



R3	0											
R4	0											
R5	0											
R6	0											
R7	0											

**Question 2 {5 pts}**

In a given C program the variables x, y, z and sum are all declared as doubles. Can you assume that these two C statements:

sum = (x + y) + z;

and

sum = x + (y + z);

always yield the same value for sum? Explain your answer, just saying yes or no won't earn you many points.

**Answer**

Not always, these two statements could yield different results because of the **rounding** inherent in floating point operations. This would typically be implemented with two floating point additions in the first case you add x and y first then z in the second you add y and z first then x. Consider the following examples

$(1e200 + (-1e200)) + 1e-30 =$  This would probably produce a result around  $1e-30$   
 Since the first addition would result in a zero.

This sequence

$1e200 + ((-1e200) + 1e-30)$  would probably produce a result of 0 since the inner addition would produce a result of around  $1e-200$  because of rounding effects.

**Question 3 {5 pts}**

True or false, can the absolute value every n-bit 2C number be contained in an n-bit unsigned number? Please explain your answer, simply answering true or false won't get you many points. (Remember the absolute value of a signed number is simply it's magnitude, egs.  $\text{abs}(-7) = 7$ ,  $\text{abs}(23) = 23$ )

**Answer**


True, the largest magnitude of an n-bit 2C number is  $2^{(n-1)}$  this is achieved by the most negative possible value. This number can readily be represented as an n bit unsigned number. It is simply a 1 followed by (n-1) zeros in binary.

#### Question 4 {10 pts}

In the LC4 single cycle implementation that we have studied the Decoder block is responsible for generating all of the control signals required to execute the current instruction. For this question you are asked to design a small portion of this circuit. Specifically, you are asked to design a circuit that takes bits from the current instruction as input and generates the two bit Privilege.CTL signal as output. Please indicate which of your 2 output bits is the MSB and which the LSB. Please use the convention I15, I14, ... ,I0 to refer to bits in the instruction word where I15 is the MSB and I0 the LSB. More points will be given for simpler solutions.
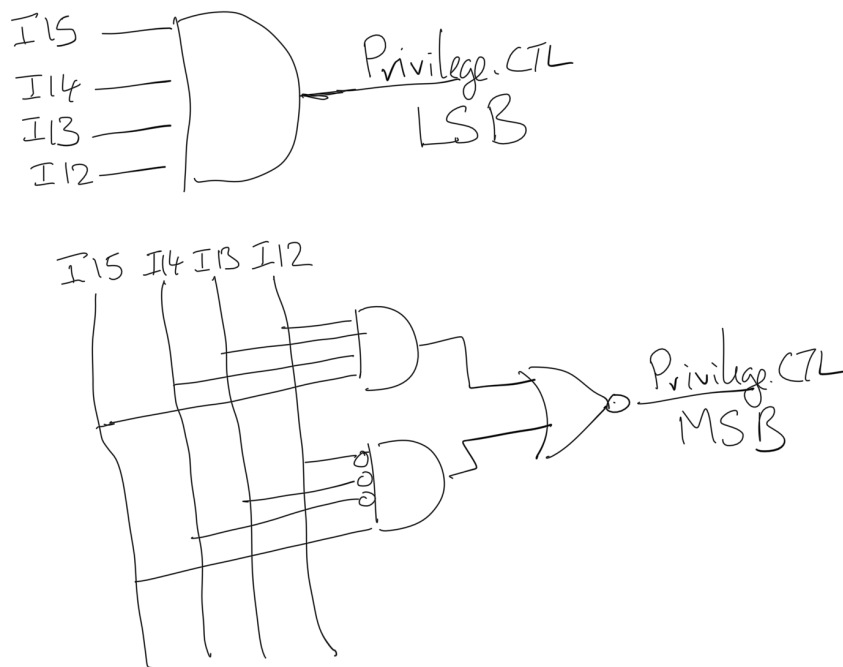
#### Answer

Here we observe that the Privilege.CTL signal should be  $10_2$  for all instructions except TRAP and RTI where it should be  $01_2$  and  $00_2$  respectively. We can conclude then that the MSB should be 1 unless the insn is TRAP or RTI and the LSB should be 0 unless the instruction is TRAP. That leads to the following solution which examines the opcode bits I15..I12. You could use the output of the LSB logic as an input to the MSB logic.



**Question 5 {10 pts}**

Design a **PLA** circuit that takes as input a 4 bit 2C value and returns a logical 1 when that input is a **non-zero** multiple of 4. Label your input bits I3 thru I0 where I3 is the MSB and I0 is the LSB


**Extra Credit {2 pts}.**

If you are not constrained to a PLA structure you can actually implement this function using no more than 3 two input gates (AND, OR, NAND, NOR, XOR, XNOR). Can you find such a solution?

 
**Answer**

First we should consider in which cases the output should be 1. The three values are 4, -4 and -8. The corresponding bit patterns are 0100, 1100, 1000. From there you can synthesize the requisite PLA.

The extra credit solution looks for situations where the lower 2 bits are both 0 and either of the upper two bits is on. Note we can check for situations where both lower bits are 0. by employing DeMorgan's law and using a NOR gate which is on the list of legal gates that was provided.



Extra Credit

 

### Question 6 {10 pts}

One of the great things about 2C representation is that we are able to use exactly the same circuit to add both unsigned and 2C values. In effect the addition circuit does not know or care whether the user thinks of the inputs as unsigned or 2C since the same algorithm is applied in both cases. Is it possible to design a single circuit that would be able to correctly detect **arithmetic** overflow for both 2C and unsigned addition in a similar manner? That is a circuit that would be able to properly detect arithmetic overflow when we perform 2C or unsigned addition without any additional inputs. Explain your answer, just saying yes or no won't earn many points. Remember that arithmetic overflow refers to a situation where the output value of the addition circuit is incorrect.

#### Answer:


This is not possible because arithmetic overflow means different things for 2C and unsigned addition. For unsigned arithmetic any operation that causes a CarryOut from the most significant position is a problem. For 2C addition this isn't always a problem, for example you may well add two 2C values like -1 and +2 which will generate a CarryOut but the answer is still correct. Basically this is not possible because unlike addition, the overflow detection function is different for unsigned and 2C so you can't have one circuit that can handle both cases.

### Question 7 {10 pts}

Design a proper CMOS circuit that takes a 4 bit unsigned number as input and produces a High(1) output if the number is a **non-zero** multiple of 5. You should refer to the bits of the input as I3 thru I0 where I3 is the MSB and I0 is the LSB. You can assume that you are also provided with the negated versions of all of these inputs. Please produce a neat, well-labeled diagram – we can't grade what we can't read. Your circuit should only have one pull down and one pull up network – you should not be cascading multiple gates to get the desired behavior.
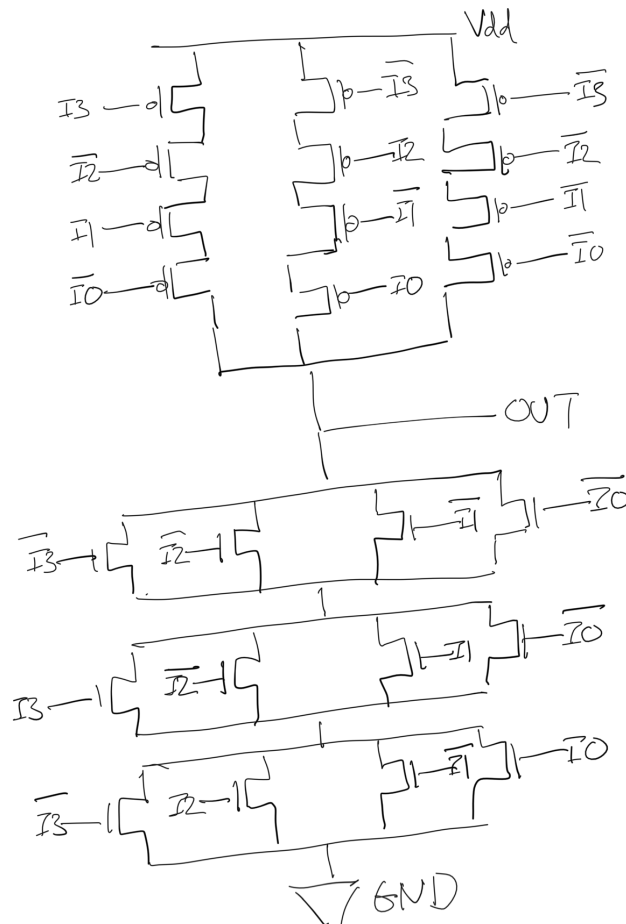
#### Answer:

We want the output of the circuit to be high if the input value is 5, 10 or 15. One way to approach the design is by designing the pull up network first but to do this we should remember that the pmos transistors are active if the input is LOW which means we need to use the inverted versions of the inputs as shown below. Once you have the pull up network you just need to make sure that the pull down network is complementary to that.



**Question 8 {10 pts}**

Attached to this exam you will find a diagram depicting an implementation of the LC4 ISA. You will also find another sheet listing all of the control signals in that implementation and what happens when they are set to different values.

Your job is to fill in the table below to show precisely how those control signals should be set to execute each of the following LC4 instructions. You must use X's to denote situations where you don't care what the control signal is.

	PCMux.CTL	rsMux.CTL	rtMux.CTL	rdMux.CTL	regFile.WE	regInputMux.CTL	NZP.WE	DATA.WE	Privilege.CTL	ALUInputMux.CTL	ALU.CTL
TRAP	4	X	X	1	1	2	1	0	1	X	X
CMPU	1	2	0	X	0	0	1	0	2	0	17
JMPR	3	0	X	X	0	X	0	0	2	X	X