

# CMOS Transistor Circuits

## Introduction to Computer Systems, Fall 2024

**Instructors:** Joel Ramirez    Travis McGaha

**Head TAs:** Adam Gorka    Daniel Gearhardt  
Ash Fujiyama    Emily Shen

### TAs:

Ahmed Abdellah

Ethan Weisberg

Maya Huizar

Angie Cao

Garrett O'Malley Kirsch

Meghana Vasireddy

August Fu

Hassan Rizwan

Perrie Quek

Caroline Begg

Iain Li

Sidharth Roy

Cathy Cao

Jerry Wang

Sydnie-Shea Cohen

Claire Lu

Juan Lopez

Vivi Li

Eric Sungwon Lee

Keith Mathe

Yousef AlRabiah



[pollev.com/tqm](https://pollev.com/tqm)


❖ How are you? Any Questions from last lecture?

# Upcoming Due Dates

- ❖ HW03 (RPN):
  - Due Friday
  - Demo in beginning of lecture today
  
- ❖ HW04 will release on Friday, will be due before Fall break.
  - **THIS IS A WRITTEN HW, AT MAX 72 HOURS LATE**
  - It should be pretty short.
  - We want to give you some practice on hardware that we are sure we can get graded and back to you before the midterm.
  - Will try to get HW05 back to you before midterm as well, but aren't certain about it.
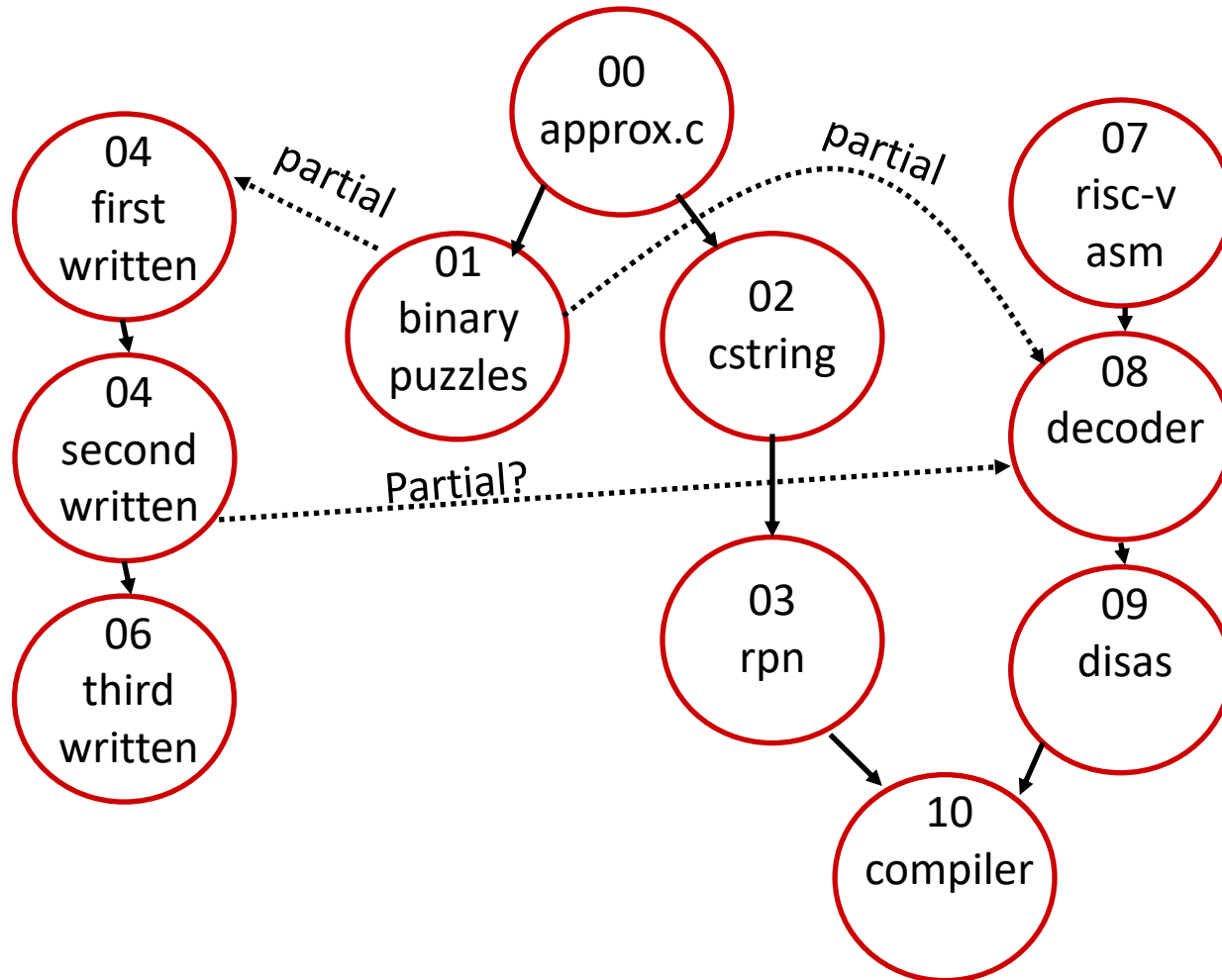
# HW DAG

- ❖ We suggest you doing HW's sequentially, but if you need to put one off till later, it is not the end of the world.



# Recitation

- ❖ Wednesday's 4PM – 5PM
  - DRL 3C6
- ❖ Super useful if you need any extra help or want to review topics.
- ❖ Slides are posted and it is recorded

# HW03 Demo


❖ rpn 😊

# Lecture Outline

- ❖ **CMOS Circuit Design**
- ❖ Gates & PLAs
- ❖ Transistors in the Real World

 
# The NAND (NOT-AND) Circuit

Note: parallel structure on top,  
series on bottom



NAND Transistor Level

Sample Input:  $A=0, B=1$

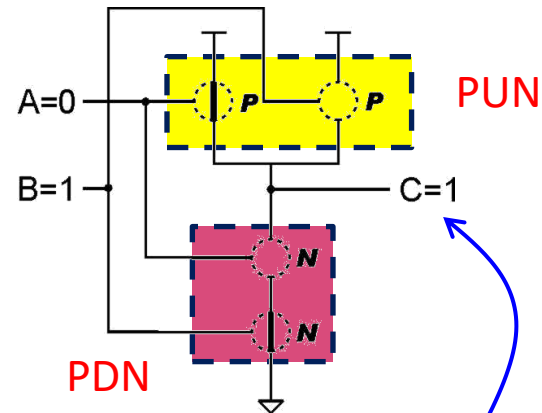

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

NAND Gate  
Truth Table



# Rules & Suggestions For Design

## ❖ Rules:

- You cannot have pMOS transistors in the PDN
- You cannot have nMOS in the PUN
- Exactly one of PDN/PUN must be “on” at a time
  - Cannot have neither connected to output
  - Cannot have both connected to output
- Every transistor in the PDN must have a complimentary transistor in the PUN
  - When any transistor in PDN is ON, its complement transistor is OFF

## ❖ Suggestions

- Start with the PDN and then do the PUN (most find it easier)
- Simplify logic before you design any part of the circuit


# NOR Circuit Design Walkthrough

- ❖ First, start with the Boolean Expression
  - NOR is NOT-OR, which is
$$\sim(A \mid B) \leftarrow \text{statement for when output is 1 (True)}$$
- ❖ Since I like to start with PDN, find the cases when output is FALSE (output connected to GND), then simplify
  - This can be done by negating the original expression
  - $\sim\sim(A \mid B) \leftarrow \text{statement for when output is 0 (False)}$
  - $(A \mid B) \leftarrow \text{simplified by identity property}$

# NOR Circuit Design Walkthrough

- ❖ With the expression for the PDN (when output is 0), translate it to a circuit diagram for the PDN
  - OR's become transistors in parallel
  - AND's become transistors in series

$(A \mid B)$  becomes

 


# NOR Circuit PUN (Strategy 1)

- ❖ With the simplified expression for PDN, negate it to get the expression for PUN
    - $(A \mid B)$  becomes  $\sim(A \mid B)$
    - Simplify
      - $\sim(A \mid B)$
      - $(\sim A \ \& \ \sim B)$  // by De Morgan's Law
  - ❖ From here, we can convert  $(\sim A \ \& \ \sim B)$  into a PUN
- In this example, initial PUN expression is the same as the original expression. This is not always the case*
 
# NOR Circuit PUN (Strategy 1)

- ❖ From here, we can convert ( $\sim A$  &  $\sim B$ ) into a PUN
  - OR's become transistors in parallel
  - AND's become transistors in series
  - pMOS transistors have an implicit "NOT"
    - pMOS only turns on when input is low (0)





The reason for the circle in pMOS:  
 Circle represents a "Not" or negation
 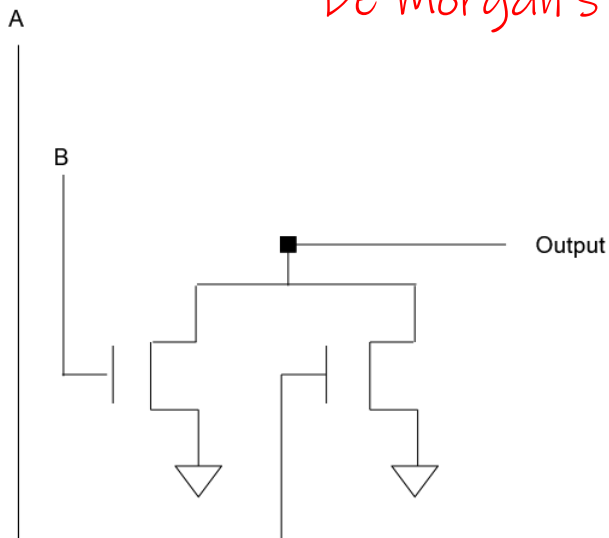
# NOR Circuit PUN (Strategy 2)


- ❖ Alternative way to get the PUN from the PDN
  - Series relations in PDN become Parallel relations in PUN
  - Parallel relations in PDN become Series relations in PUN
  - nMOS transistors become pMOS transistors

*This is just a "short-cut" for applying De Morgan's to the PDN*


 
# Completed NOR Circuit

- ❖ Finally, all you have to do is combine the PDN and PUN
  - To be safe, check your work and create a truth table



A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

# Complex Practice

- ❖ Let's Practice, create the CMOS circuit that takes in 3 inputs (A, B, C) and has a high output (1) if C is 0 and at least one of A or B is 0.
- ❖ First, what is the expression?
  - $\sim C \& (\sim A \mid \sim B)$  *Take some time to figure this out.*
- ❖ Second, what is the expression for the PDN?




# Complex Practice

- ❖ Second, what is the expression for the PDN?
  - $\sim C \& (\sim A \mid \sim B)$  // original overall expression
  - $\sim(\sim C \& (\sim A \mid \sim B))$  // Negate for PDN expression
  - $\sim\sim C \mid \sim(\sim A \mid \sim B)$  // by De Morgan's
  - $C \mid \sim(\sim A \mid \sim B)$  // By identity property
  - $C \mid (\sim\sim A \& \sim\sim B)$  // by De Morgan's
  - $C \mid (A \& B)$  // by identity property
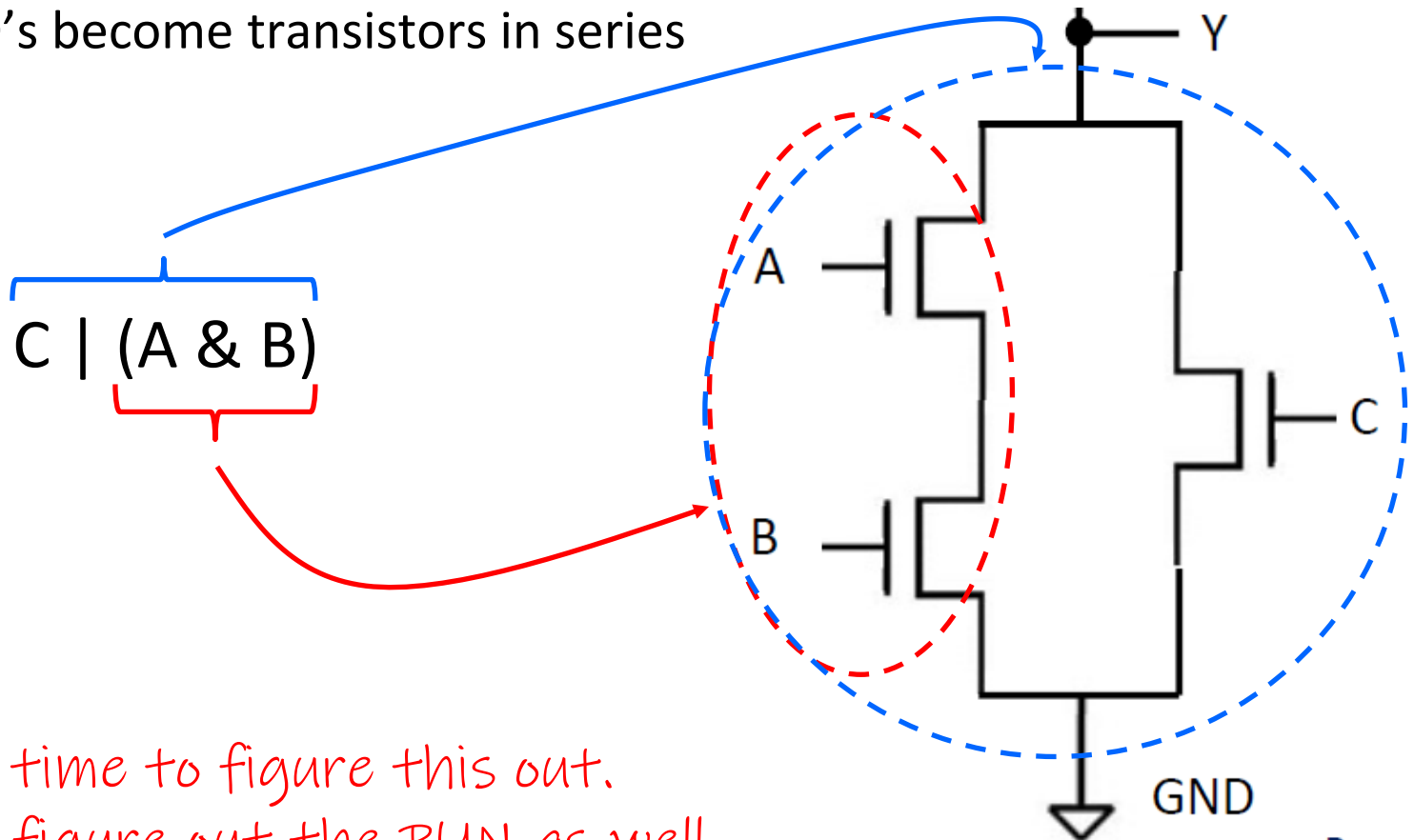
# Complex Practice



- ❖ Third, convert the PDN expression into a circuit
  - OR's become transistors in parallel
  - AND's become transistors in series



Take some time to figure this out.  
If you can, figure out the PUN as well

  
# Complex Practice

- ❖ Fourth get the PUN from the PDN (I'll use the short-cut)
  - Series relations in PDN become Parallel relations in PUN
  - Parallel relations in PDN become Series relations in PUN
  - nMOS transistors become pMOS transistors


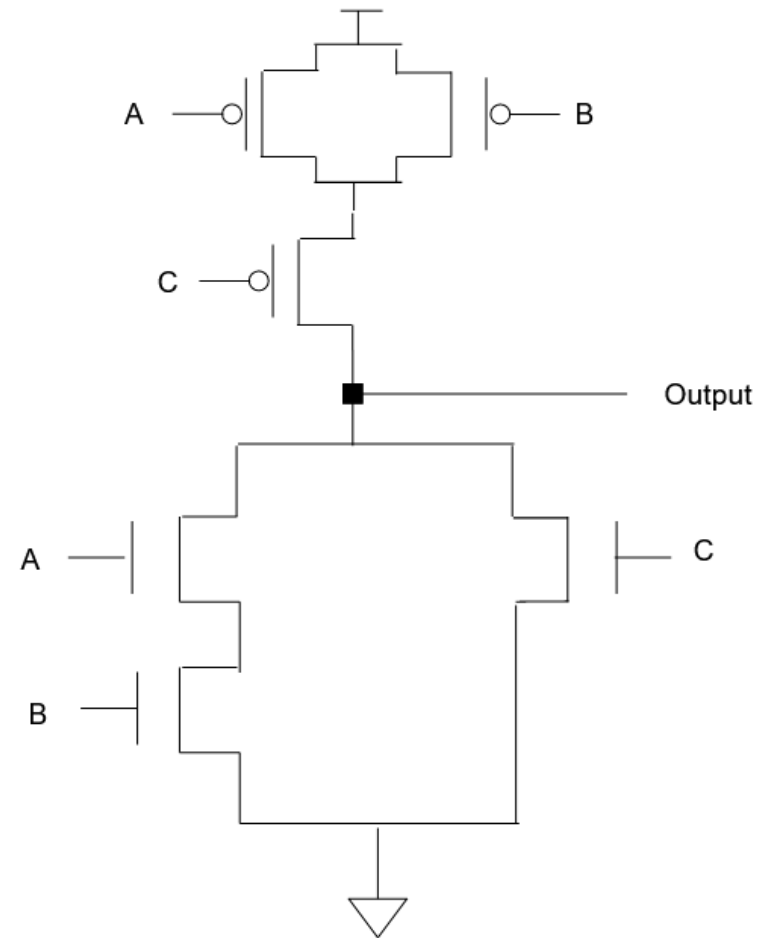
# Complex Practice


- ❖ Last step:  
combine PDN and PUN
- ❖ Suggested:  
Check your work



# Closing Details on CMOS

- ❖ Sometimes, there will be 3 or more inputs (A, B, C)
- ❖ Sometimes you will also have the complements of the inputs ( $\sim A$ ,  $\sim B$ ,  $\sim C$ ) that you can use as inputs in a circuit

- Example AND circuit:

 


- ❖ Highly suggest you simplify before creating circuits
  - More practice available in recitation

# Lecture Outline

- ❖ CMOS Circuit Design
- ❖ **Gates & PLAs**
- ❖ Transistors in the Real World

# Logic Gates

## ❖ Basic Logic Gates

 


## ❖ Moving an Abstraction layer “up”

- + Abstracting away messy details of CMOS Circuits!
  - + Technology independent at this level, doesn't have to be CMOS
  - - Designing only at this level can be less efficient than CMOS
- 
- ❖ Gates of more complex operations exist (e.g. an XOR gate)
  - ❖ Gates can be combined to make more complex functions

# Logic to Gates Practice

- ❖ Let's Practice, create a Gate-level circuit that takes in 3 inputs (A, B, C) and has a high output (1) if C is 0 and at least one of A or B is 0.
- ❖ First, what is the expression?
  - $\sim C \ \& \ (\sim A \ | \ \sim B)$
- ❖ Second, translate it to gates:

 




# Logic to Gates Practice 2

- ❖ Create a gate-level circuit that takes two inputs (A and B) and output 1 if and only if A and B are the same.
  - Use only the basic logic gates I've shown you so far

- ❖ First, what is the expression?

 - $(A \& B) \mid (\sim A \& \sim B)$  *Take some time to figure this out. If you can, figure out the circuit as well*




# Poll Everywhere

[pollev.com/tqm](https://pollev.com/tqm)

❖ What is the equivalent expression of this gate circuit

- A.  $(A \& B) | C$
- B.  $C \& (B | A)$
- C.  $(C | B) \& A$
- D.  $(B \& C) | A$
- E. I'm not sure

 

 **Poll Everywhere**[pollev.com/tqm](https://pollev.com/tqm)

❖ What is the equivalent expression of this gate circuit


**A.  $(A \& B) \mid C$**

B.  $C \& (B \mid A)$

C.  $(C \mid B) \& A$




D.  $(B \& C) \mid A$

E. I'm not sure

 

  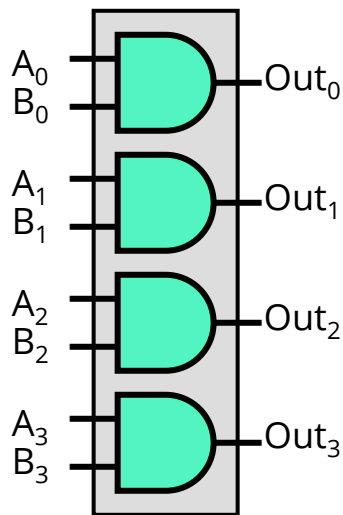
# Shortcuts: Multi-Bit Gates


- ❖ Use a cross-hatch mark groups of wires:
  - Example, Say we had two 4-bit integers we wanted to AND
  - $A_3$  is the most-significant bit,  $A_0$  is the least significant bit



This is still a 2-input NAND,  
Except each input is 4-bits wide!
 
# Shortcuts: Inverting Signals


- ❖ Instead of always drawing out a NOT gate
  - A  represents a negation/inversion of a signal



# Boolean algebra rules on gates

- ❖ Boolean rules still apply to gate-level circuits

- ❖ Associative Example:

 

- ❖ De Morgan's law Example:



- ❖ **NOTE:** There are actual differences between these circuits, but “logically” they are the same. More on this later in lecture.

# PLA's

- ❖ What if we only had a truth table to create a gate circuit?
- ❖ PLA: **P**rogrammable **L**ogic **A**rray
  - A device where we can configure AND, OR and NOT gates to implement a function


A	B	C	OUT
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1



GATES
 
# Implementing a PLA From a Truth Table

- ❖ NOT, AND, OR can implement any truth table function



*IN a PLA, this structure is always followed*

Notice, 5 rows that cause a "1" in the output...5 AND gates  
 Notice, 1 output, only 1 OR gate  
 Notice, negations always happen before the AND gates




# PLAs Pros & Cons

- ❖ A PLA can be used to implement ANY logical function
  - Provides you with an incredibly easy tool to use
  - If you can generate a truth table to model desired behavior
    - PLA gives you a way generate the gate level implementation
  - *However, PLAs don't give the most efficient solution*
    - *In terms of "run-time" and transistor cost*

Logic Function  
 $F = (A \text{ AND } B) \text{ OR } C$

Truth Table

A	B	C	OUT
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

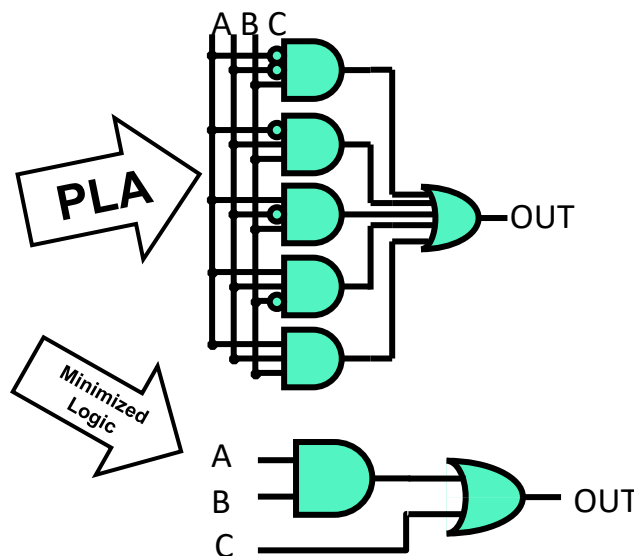

# Lecture Outline


- ❖ CMOS Circuit Design
- ❖ Gates & PLAs
- ❖ **Transistors in the Real World**

# Moore's Law

- ❖ Observation that number of transistors that can be put in an integrated circuit doubles every 18 months-ish

Intel 15-core Xeon IvyBridge-EX (2014):  
4.3 billion  
(not pictured)

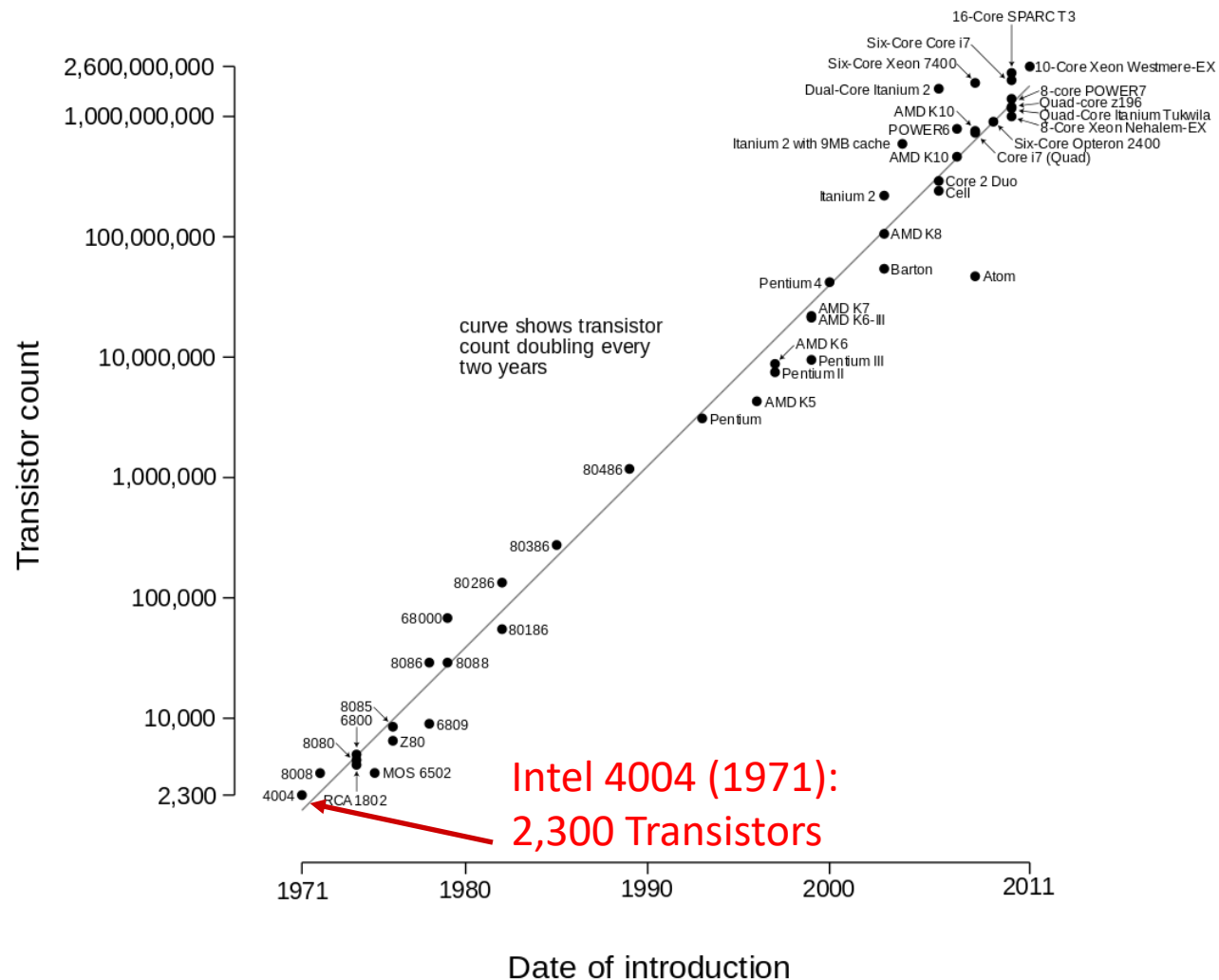Microprocessor Transistor Counts 1971-2011 & Moore's Law



# Transistors are Small



- ❖ The Intel Skylake chip uses transistors that are 60 times smaller than the wavelength of light.
  - Skylake transistor size 14nm.
  - Wavelength of visible light 400-700nm
  
- ❖ There are now more transistors at work in the world (15 quintillion : 15,000,000,000,000,000,000) than there are leaves on all the trees in the world
  - From (The Perfectionists, Simon Winchester)

# Transistors limitations

- ❖ After switching an input, it takes time for current to flow, and output to match changed output
- ❖ The faster you switch the circuit, the more current flows, the more heat is generated, the hotter your laptop gets.
  - This has proven to be an important barrier to speeding up CMOS circuitry

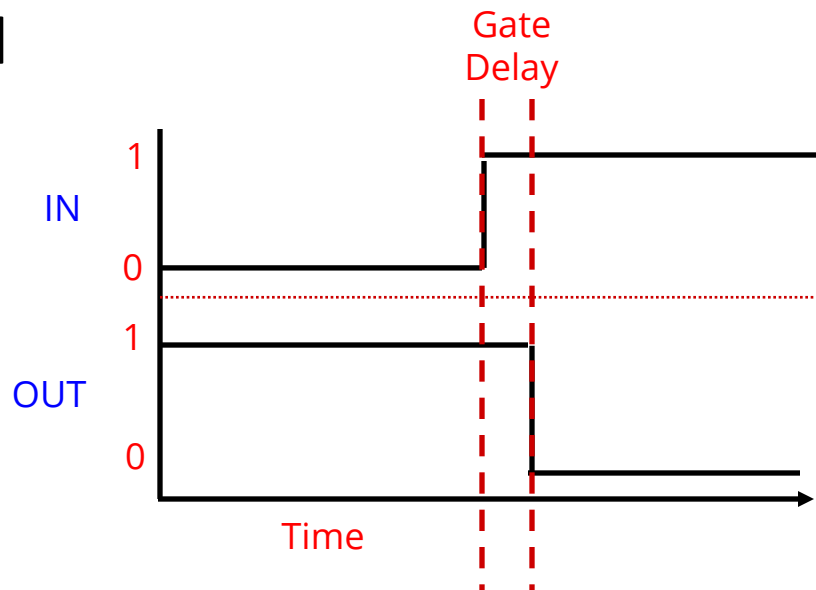 
# Gate Delays

- ❖ With any logic circuit there will be a short delay between when an input changes and when the output updates to it
  - This time is referred to as the gate delay
- ❖ For modern circuitry, gate delays are on the order of nanoseconds ( $10^{-9}$  seconds) or picoseconds ( $10^{-12}$  seconds)
- ❖ These delays ultimately limit the number of operations you can perform per second




 **Poll Everywhere**[pollev.com/tqm](https://pollev.com/tqm)

 - ❖ Consider the following logically equivalent circuits:



Circuit A

 


Circuit B

Which is the better implementation of 4-input AND?

 
- A. Circuit A**
- B. Circuit B**
- C. They are equally good**
- D. I'm not sure**

 **Poll Everywhere**[pollev.com/tqm](https://pollev.com/tqm)

- ❖ Consider the following logically equivalent circuits:



Circuit A

 

Circuit B

Which is the better implementation of 4-input AND?

**A. Circuit A**

Circuit A is better:

Why? It's faster, 2 "gate delays" instead of 3

**B. Circuit B**

**C. They are  
equally good**

- ❖ **Gate delays: longest path (in gates) through a circuit**

- Grossly over-simplified, ignores gate differences, wires
- Good enough for our purposes

**D. I'm not sure**



# Abstraction

- ❖ Moving from CMOS to Gates is going to a higher abstraction level.
  
- ❖ Transistor Level:
  - More control over how many transistors there are and how they are oriented (orientation could affect how much delay there is)
  - More hardware details that must be worried about (PDN vs PUN, pMOS vs nMOS, etc)
  
- ❖ Gate level:
  - Abstract away the hardware details, focus only on logic.
  - Multiple gates -> longer delay

# Multiple Approaches to things

- ❖ Lots of ways to implement things. Implementation choice depends on many factors:
  - Ease of Implementation (Readability, dev time, ...)
  - Kinds of gates available
  - Number of transistors available
  - Energy Consumption
  - Circuit delay
  - ...

# Lecture Schedule

## ❖ This Lecture

- CMOS
- Gates
- PLAs
- Gate Delays

## ❖ Next Lecture:

- Use Gates & PLAs to start building more complex circuits and components of a computer