

Sequential Logic & Memory

Introduction to Computer Systems, Fall 2024

Instructors: Joel Ramirez Travis McGaha

Head TAs: Adam Gorka Daniel Gearhardt
Ash Fujiyama Emily Shen

TAs:

Ahmed Abdellah

Ethan Weisberg

Maya Huizar

Angie Cao

Garrett O'Malley Kirsch

Meghana Vasireddy

August Fu

Hassan Rizwan

Perrie Quek

Caroline Begg

Iain Li

Sidharth Roy

Cathy Cao

Jerry Wang

Sydney-Shea Cohen

Claire Lu

Juan Lopez

Vivi Li

Eric Sungwon Lee

Keith Mathe

Yousef AlRabiah



pollev.com/cis2400

❖ How are you? Any Questions?

Logistics

- ❖ Midterm
 - ❖ Covers material all the up to Lecture 10!
 - ❖ Double Sided Cheat Sheet of Paper is permissible
- ❖ HW 5 is Due Tomorrow!
 - ❖ Ask for an extension before hand if you already know you need it.
 - ❖ Easier to respond at 6PM than it is at 2AM.



pollev.com/cis2400

Question for Everyone

- ❖ If recitation next week was a Midterm Review Session, would you prefer that?


Lecture Outline

- ❖ Review
 - D Latch & Clock
 - D Flip Flops
- ❖ Registers
- ❖ Memory at a high level
- ❖ Memory using flip flops
- ❖ Memory Hierarchy


D Latch

WE is "Write Enabled".

 If WE is set to 0, the value of D isn't Saved.



A	B	Output
0	0	1
1	0	1
0	1	1
1	1	0

 


D is the data we are trying to "Save" in the Latch.

Q is the value stored in the Latch.


In D Latch terms, *Q is set to the value of D when WE is 1.*

Some Verbiage

NAND

 

A	B	Output
0	0	1
1	0	1
0	1	1
1	1	0

 


D is 1 equivalent to "D is High"

D is 0 equivalent to "D is Low"


Timing Diagrams Revisited

 - ❖ Diagram to represent how signals (outputs) change



 **Poll Everywhere**pollev.com/cis2400

 ❖ How many times is Q set to be 1 (i.e. High)?



A. 4

B. 5


C. 6

D. 7

 E. I can't tell

 **Poll Everywhere**pollev.com/cis2400

❖ How many times is Q set to be 1 (i.e. High)?



A. 4

B. 5


C. 6

D. 7

 E. I can't tell

 **Poll Everywhere**pollev.com/cis2400

❖ How many times is Q set to be 1 (i.e. High)?



A. 6

B. 7


C. 8

D. 9

 E. I can't tell

 **Poll Everywhere**pollev.com/cis2400

❖ How many times is Q set to be 1 (i.e. High)?



A. 6

B. 7


C. 8

D. 9

 E. I can't tell

Transparency


- ❖ WE being 1 sets Q equal to D every time!



If **WE** were to be held at a high signal indefinitely, this would be a Fully Transparent D-Latch.

The Clock Revisted

 
- ❖ A regular up & down signal with constant Period



- ❖ A **clock** in tandem with **WE** can change when the D-Latch is *Transparent*.


The Clock & Transparency

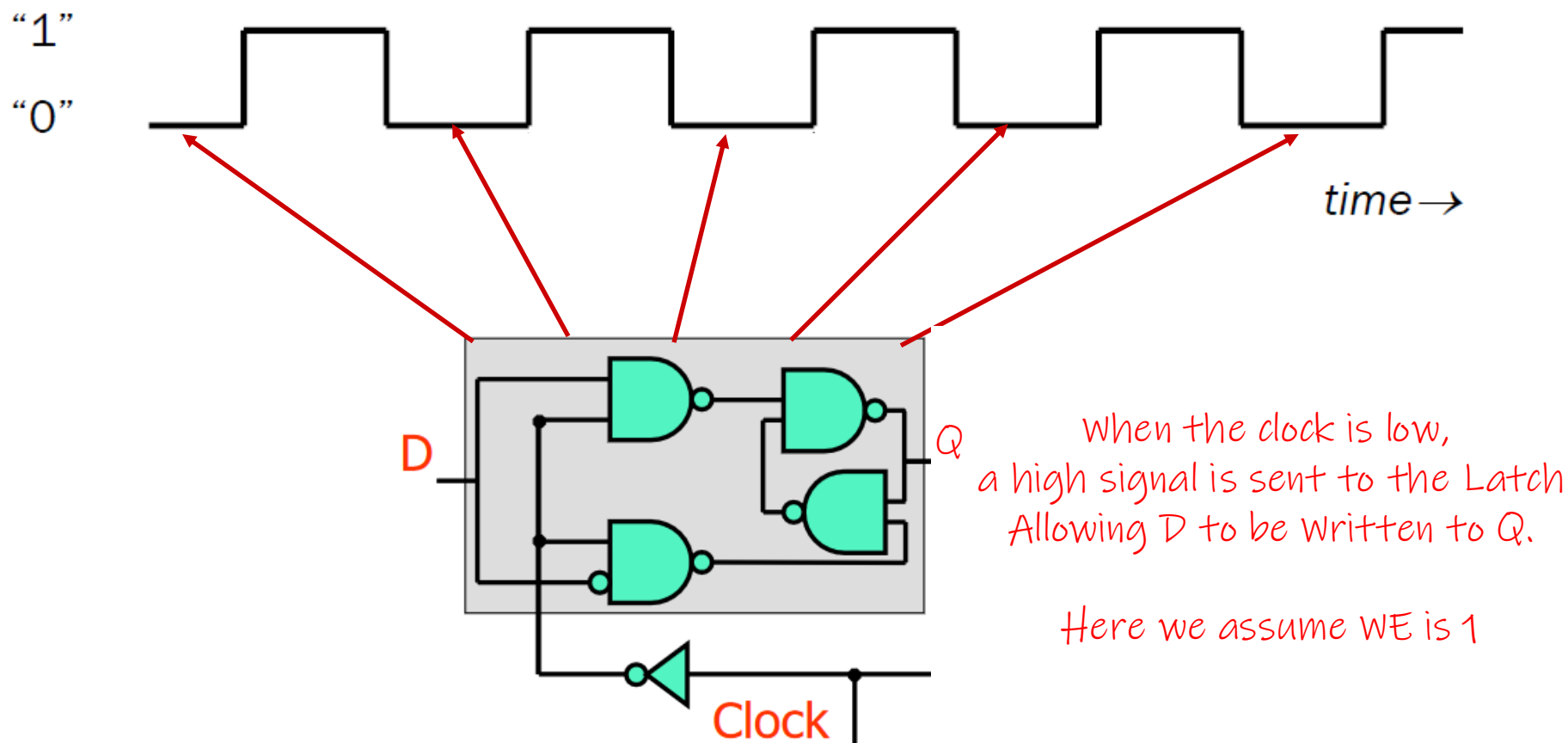- ❖ A regular up & down signal with constant Period



D Flip Flop

Transparent
Low

 

Transparent
high




When the clock is LOW, Q_{inter} is set to D
When the clock is High, Q is set to Q_{inter}

Lecture Outline

- ❖ Review
 - D Latch & Clock
 - D Flip Flops
- ❖ **Registers**
- ❖ Memory at a high level
- ❖ Memory using flip flops
- ❖ Memory Hierarchy

Register Made of Flip Flops

  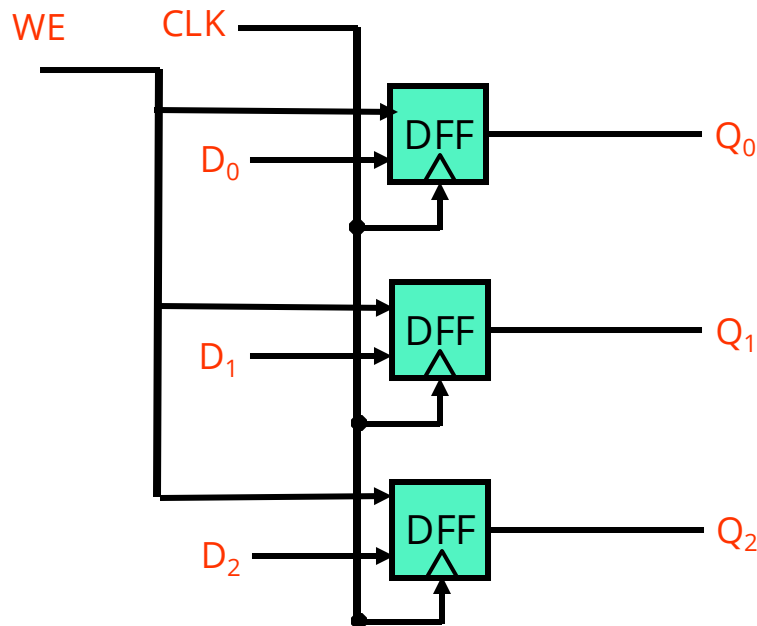
- ❖ A collection of D Flip-Flops, controlled by a common CLK signal can be called a register
 - A register is a fixed size multi-bit fast storage location used by a Processor. (More on this over the next few weeks)
 - Many different implementations; but made of same stuff



This device can store 3-bits!

Register Made of Flip Flops

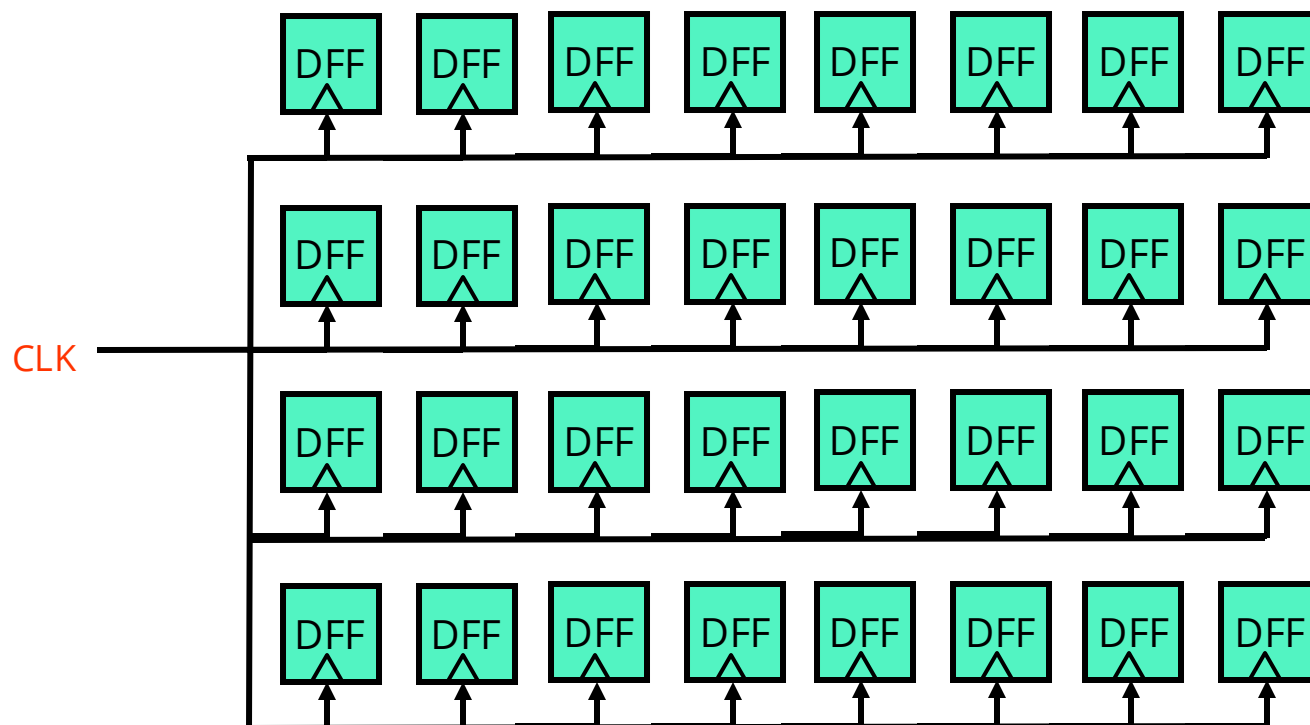- ❖ A collection of D Flip-Flops, controlled by a common CLK signal can be called a register
 - Here is a 32 bit register connected by CMN CLK



Lecture Outline

- ❖ Review
 - D Latch & Clock
 - D Flip Flops
- ❖ Registers
- ❖ **Memory at a high level**
- ❖ Memory using flip flops
- ❖ Memory Hierarchy

Memory as an array

- ❖ Memory is like a huge array...
 - Stores ***almost all*** the information needed to run a program (Code, variables, strings, ...)
 - In a 64-bit machine, this array has **18,446,744,073,709,551,616** indexes
 - Pointers are 8 bytes (64 bits)
 - That's 2^{64} possible values
 - 0xFFFFFFFFFFFF0020 would be a *Full Address*.
 - An index corresponds to a location in memory that contains data
 - (An index in this context is called an **address**)

Memory as an array

- ❖ Memory is like a huge array...
 - A location in memory is of fixed size bits
 - Usually 8-bits.
 - RISC-V, x86, and Arm64
 - Previous Version of CIS2400 used LC4
 - **USED 16 bits**
 - These addresses could be storing variables

```
int a = 0;  
int b = 9;
```

Index # (Address)	Information (Data)
0	0xFFEC
1	0x000A
2	0xFFF1
3	0x0008
4	0xFFFF
5	0x0000
6	0x0102
7	0x0000
8	0xFF32
9	0x2400
10	0x0000
11	0x0009
12	0xF308
13	0x0000
14	0x0000

Memory as an array

- ❖ Address Space: The range of possible addresses. Usually, some power of 2.
 - In RISC-V, we can have either 2^{32} or 2^{64} addresses depending on the width of the registers.
 - (i.e. Is the Machine 32 or 64 bits?)
- ❖ Addressability: number of bits per location
 - 8-bits on modern computers
 - 8-bits for RISC-V

Index # (Address)	Information (Data)
0	0xFFEC
1	0x000A
2	0xFFF1
3	0x0008
4	0xFFFF
5	0x0000
6	0x0102
7	0x0000
8	0xFF32
9	0x2400
10	0x0000
11	0x0009
12	0xF308
13	0x0000
14	0x0000

Basic Memory Usage

- ❖ There are two basic memory operations
 - Selecting a location to read from
 - Selecting a location to write to
- ❖ Consider our example from before

```
int a = 0;
int b = 9;
```

- ❖ What if we did

```
b = a;
```

- ❖ Done in **two steps**:

- Read the value stored in a
- Store the value in b

Index # (Address)	Information (Data)
0	0xFFEC
1	0x000A
2	0xFFF1
3	0x0008
4	0xFFFF
5	0x0000
6	0x0102
7	0x0000
8	0xFF32
9	0x2400
10	0x0000
11	0x0000
12	0xF308
13	0x0000
14	0x0000



pollev.com/cis2400

- ❖ If we wanted to use memory that contains 128 different locations, how many bits do we need at minimum to represent an address?
 - A. 5
 - B. 7
 - C. 8
 - D. 6
 - E. I'm not sure

 **Poll Everywhere**pollev.com/cis2400

- ❖ If we wanted to use memory that contains 128 different locations, how many bits do we need at minimum to represent an address?

A. 5

B. 7

C. 8

D. 6

E. I'm not sure


7 bits is = 2^7 different values
 2^7 is 128

Lecture Outline

- ❖ Review
 - D Latch & Clock
 - D Flip Flops
- ❖ Registers
- ❖ Memory at a high level
- ❖ **Memory using flip flops**
- ❖ Memory Hierarchy


Let's build a simple 2^2 by 3-bit memory

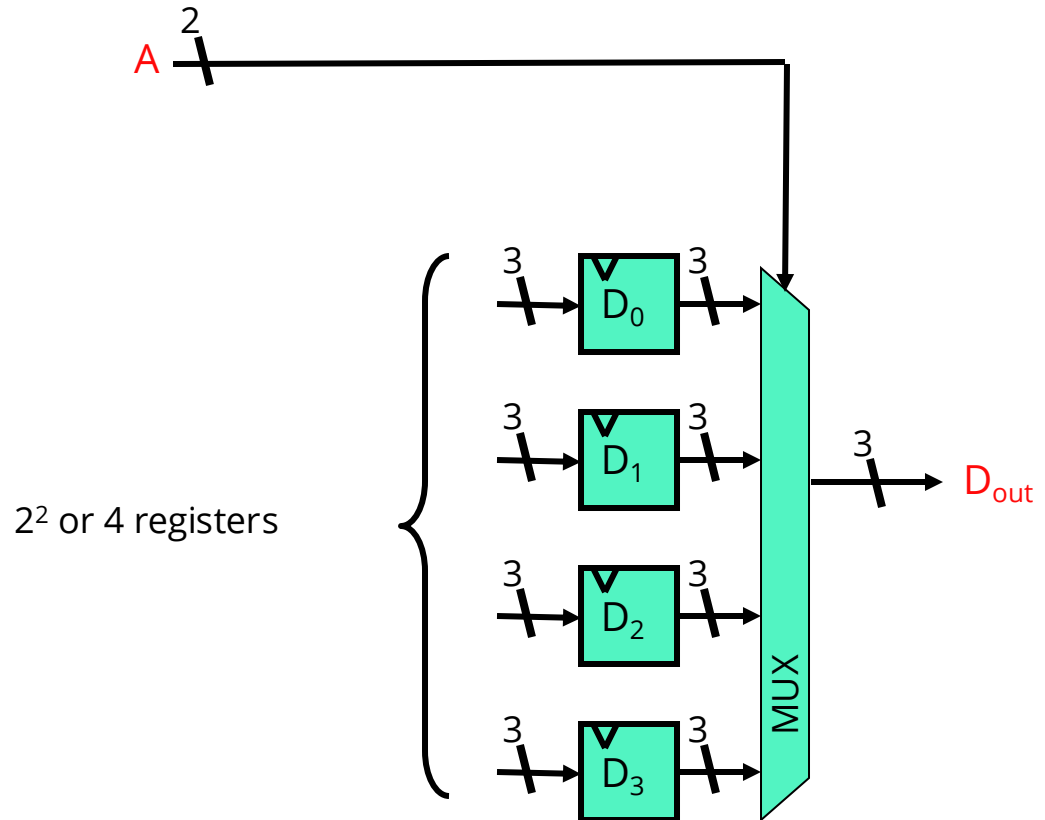- ❖ 2^2 is the amount of locations
- ❖ 3-bit is the size of the memory at the location.
- ❖ We can implement memory as a collection of registers
- ❖ Read operation:



Aside: Decoder

 - ❖ n inputs, 2^n outputs
 - $n = 2$ for this example
inputs are A and B
- ❖ A single output will be 1,
the rest will be 0
 - Putting in a binary number
will have the corresponding
output wire “turn on”
- ❖ Sort of a “reverse MUX”
 - Instead of 4-to-1 we are
sort of doing 1-to-4




2^2 by 3-bit writeable memory

Write operation

Limitation:

You can only read or write
at any given time

This is called "single port" memory

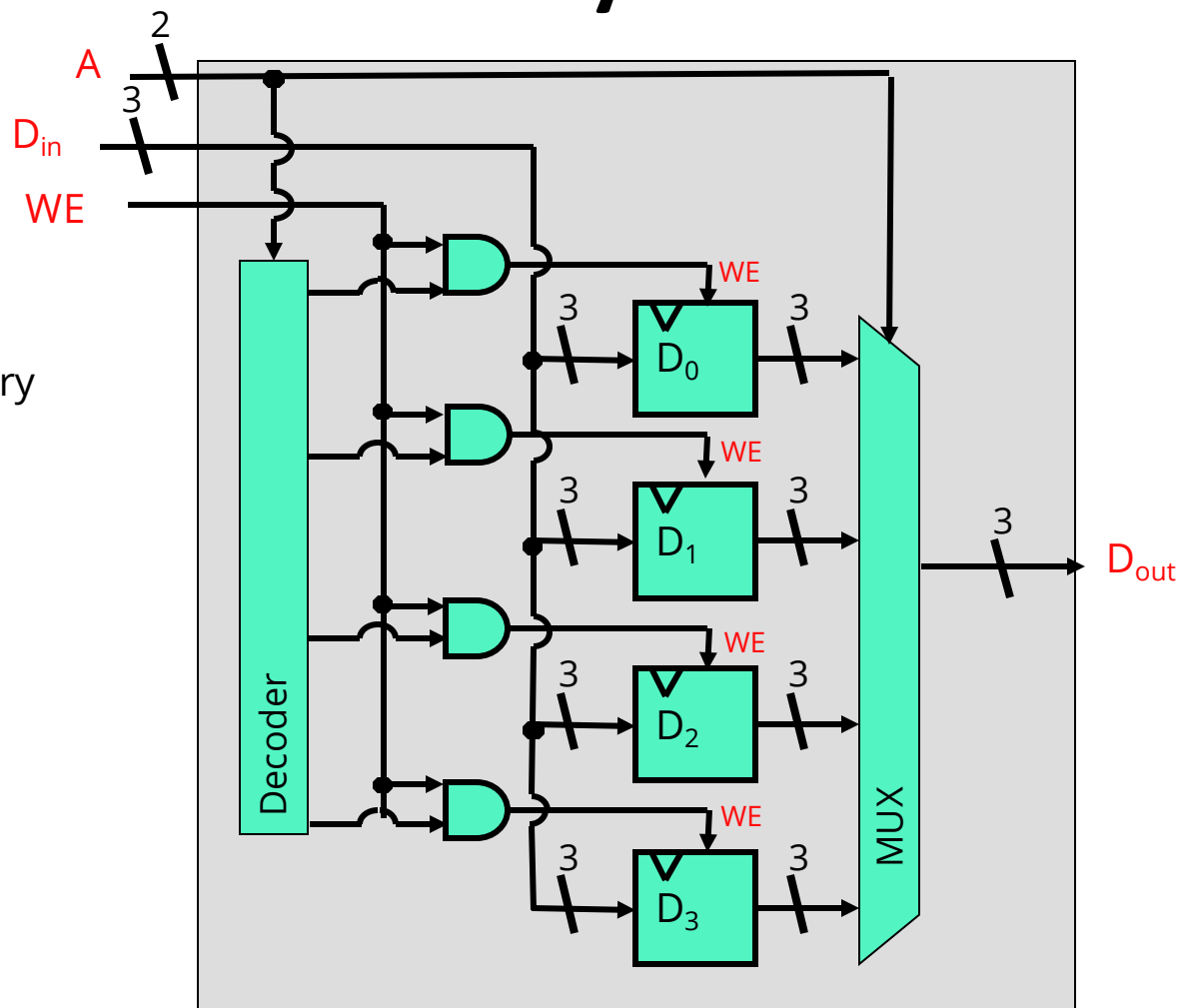

2^2 by 3-bit writeable memory

Write operation

Limitation:

You can only read or write at any given time

This is called "single port" memory

Let's go through an example:


$A = 01$

$WE = 0$

$D = ?$

WE makes these output 0

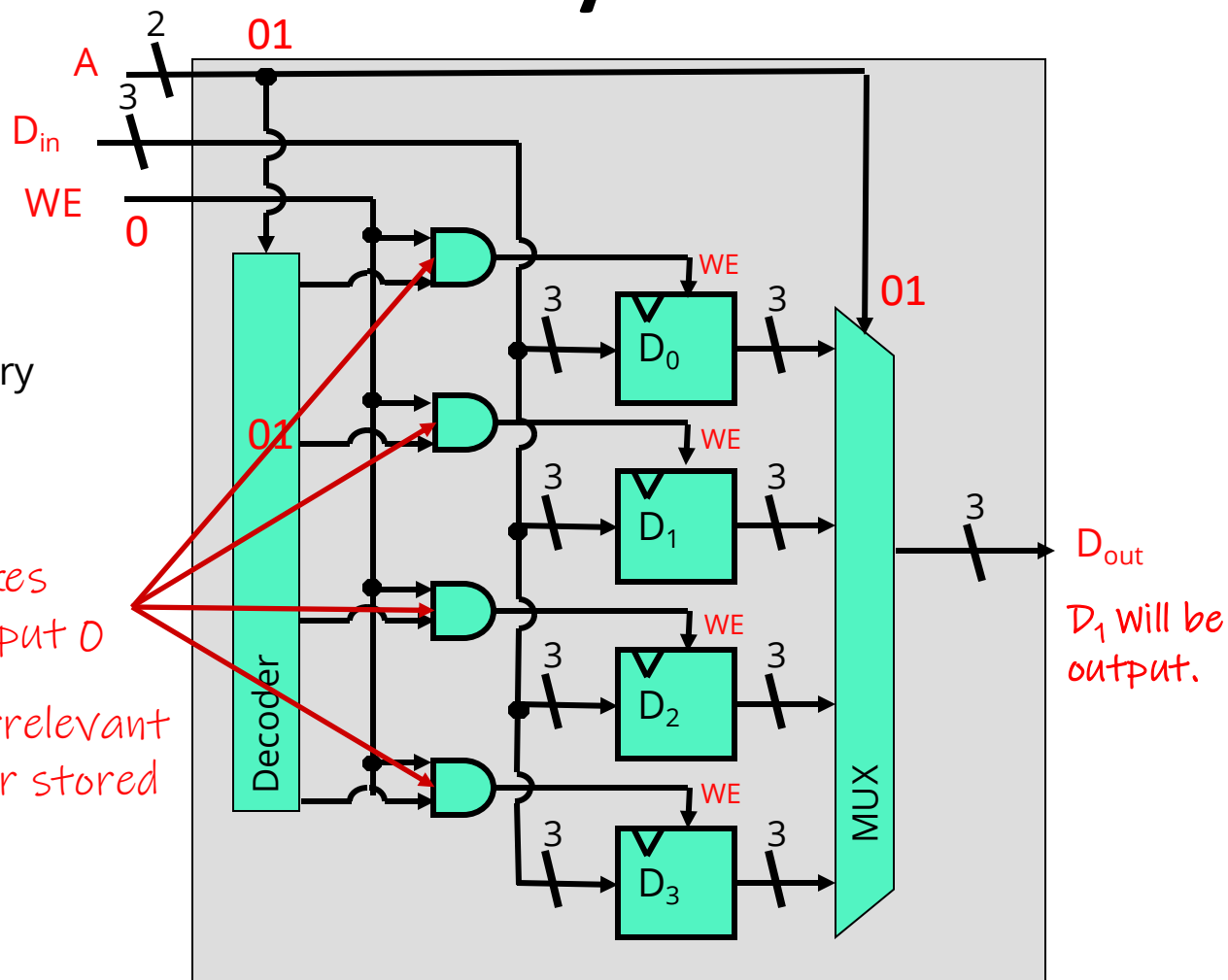D_{in} is then irrelevant as it is never stored





pollev.com/cis2400


Which is true?

$A = 10$

$WE = 1$

$D_{in} = 001$

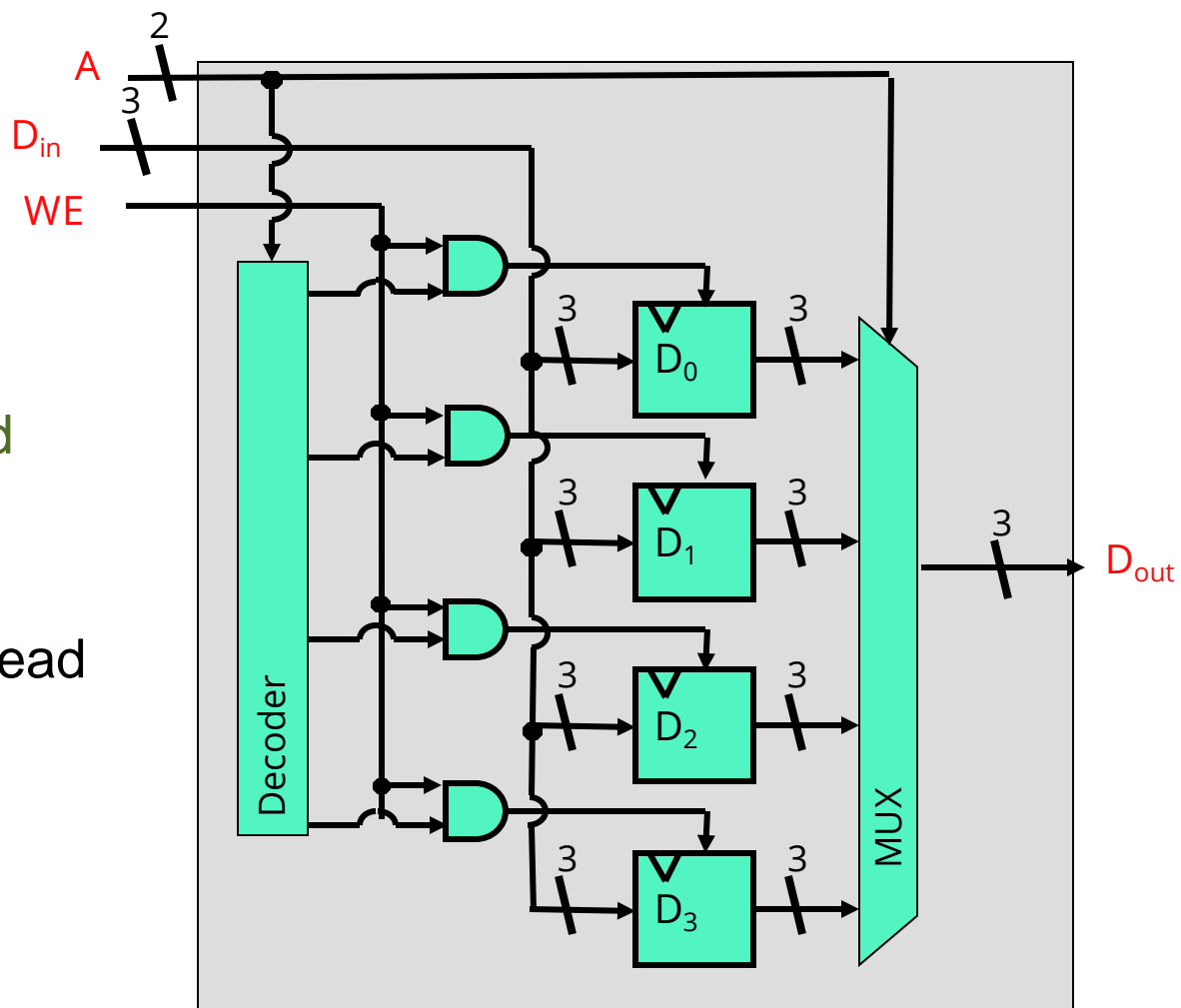- A. D_3 is read only
- B. D_2 is set to 001 and read
- C. D_1 is read
- D. D_2 is set to 001 but not read





pollev.com/cis2400


Let's see what happens

$A = 10$

$WE = 1$

$D = 001$

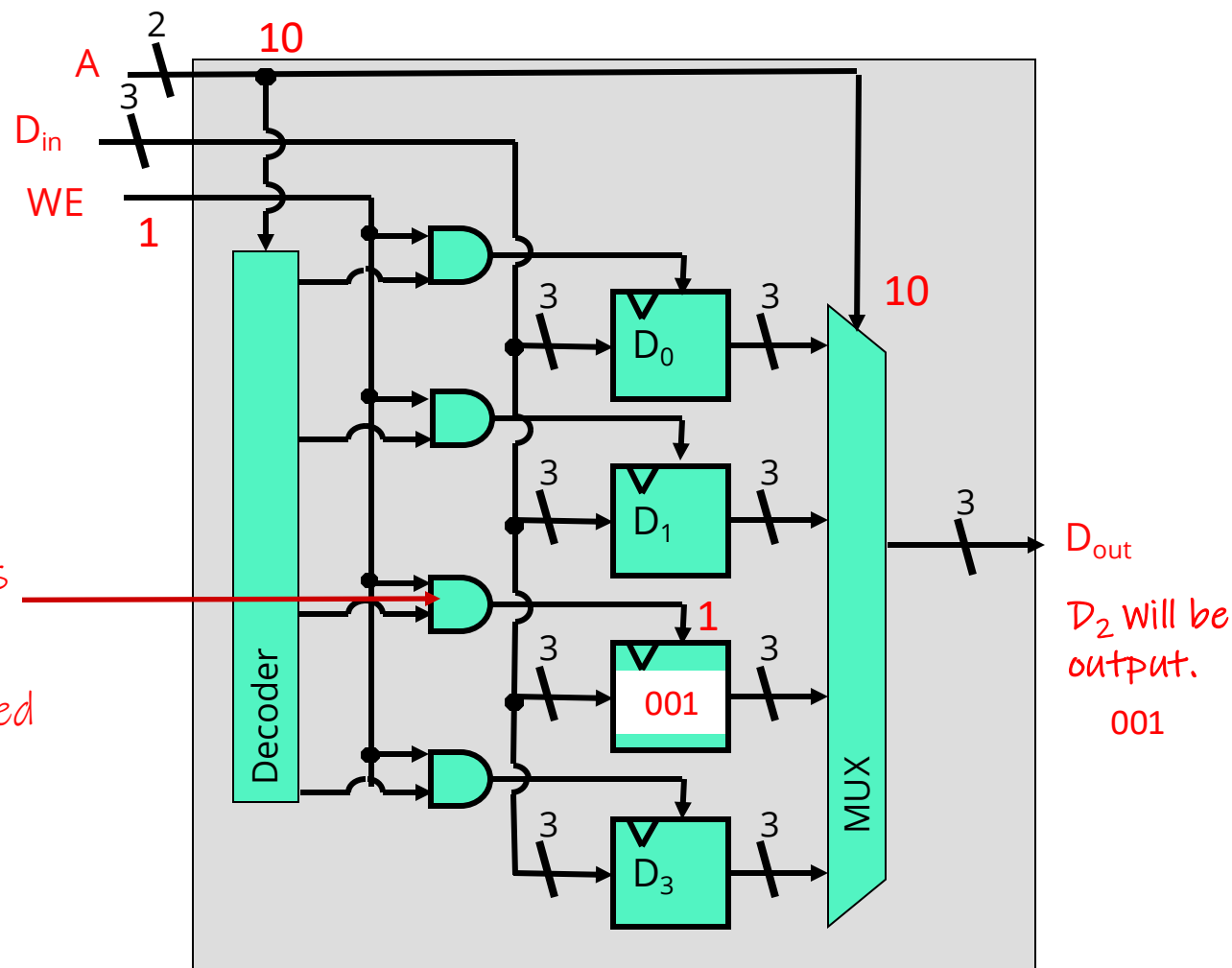Decoder makes
this output 1
 D_{in} is then stored
in D_2 .





pollev.com/cis2400

Which is true?

$A = 10$

$WE = 1$


$D = 001$

A. D_3 is read only

B. D_2 is set to 001 and read

C. D_1 is read

D. D_4 is set to 001 and read

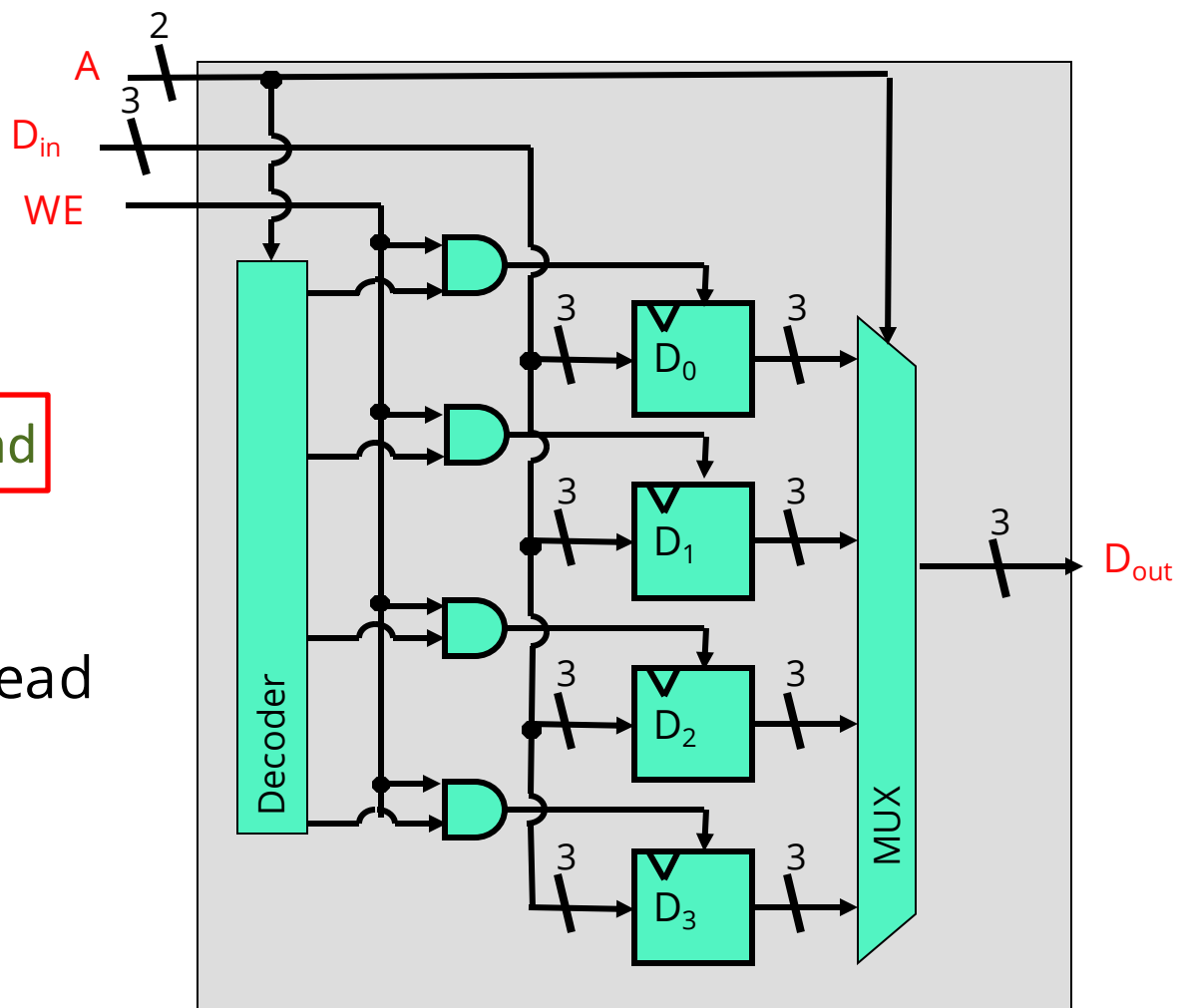


2^2 by 3-bit memory – independent R/W

- ❖ Can have independent read/write operations if we take in separate addresses for each.


You can read from one address and write to another with this arrangement

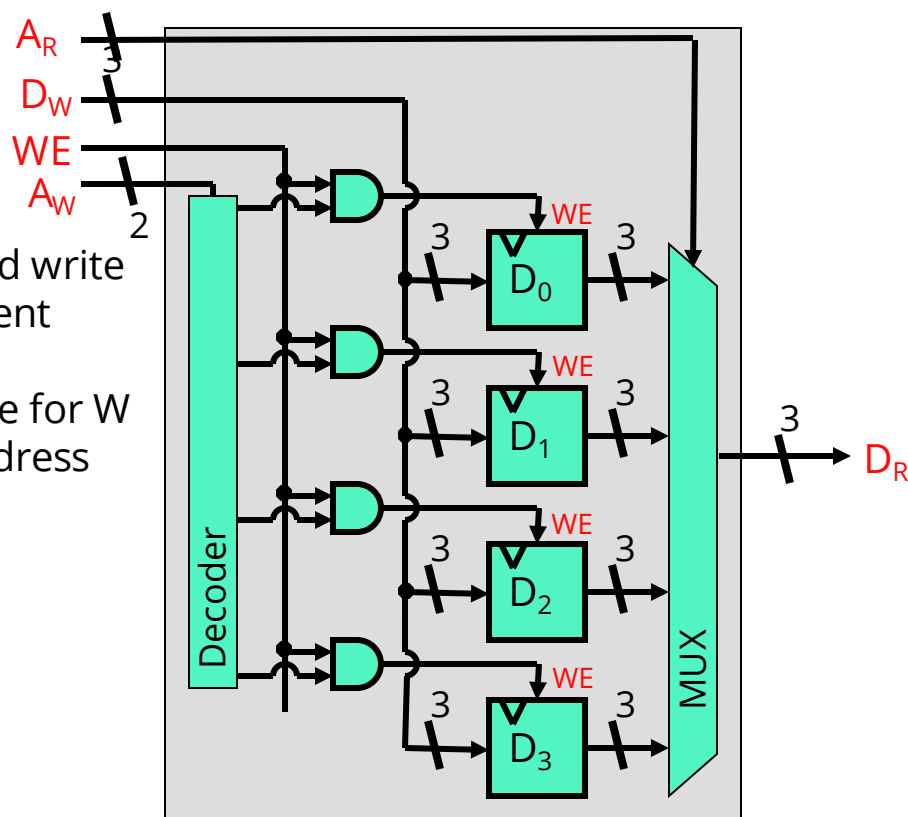1 address line for R & 1 address line for W
Previously we used the same address



2^2 by 3-bit memory – Multiple Reads

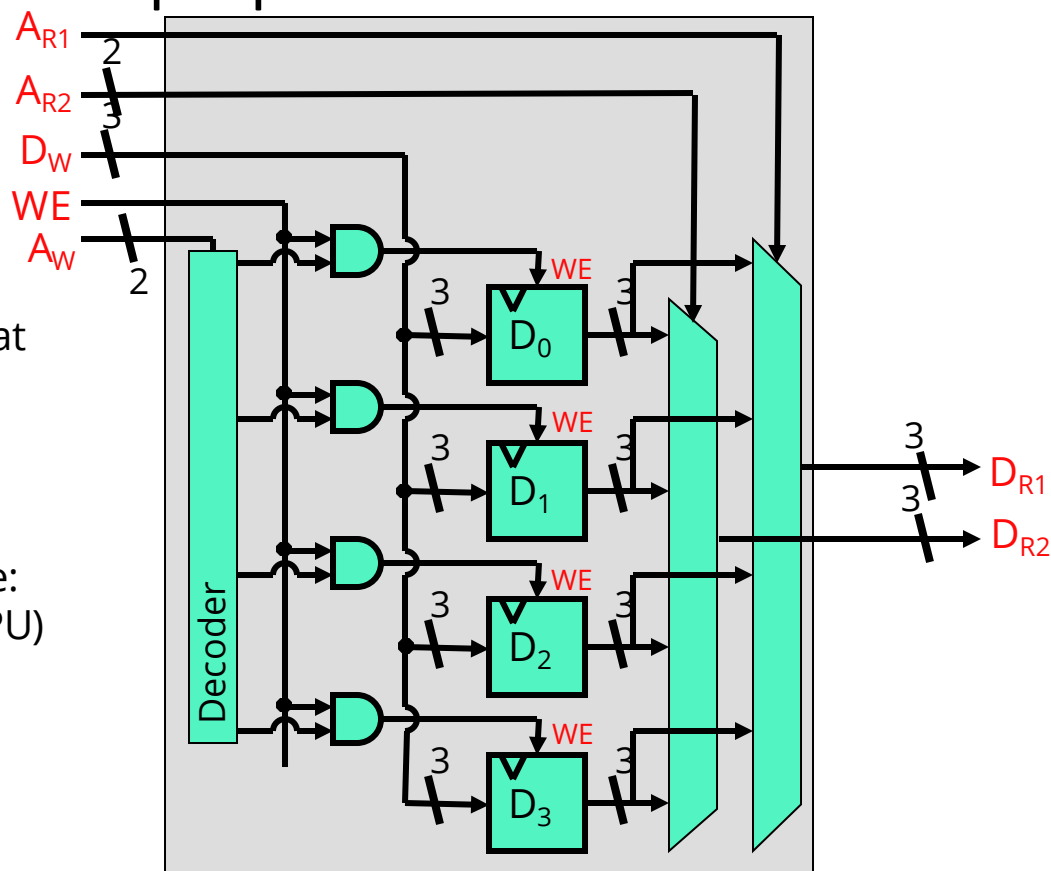- ❖ Can read from multiple places at once!



Read from 2 locations at once, write to a third!
(notice 3 address lines)

(We will use this later
In something called the:
"register file" for the CPU)


More Memory Details

- ❖ The Memory We've Created Would need many transistors, but is a good starting place to understand how it works!
 - Real memory: fewer transistors, denser, relies on analog properties
- ❖ The logical structure of all memory is similar
 - Address decoder
 - “Word select line”, word write enable
 - “Bit line”
- ❖ Two basic kinds of **RAM** (Random Access Memory)
- ❖ **Static RAM** (SRAM) - 6 transistors per bit
 - We've created a type of SRAM in this presentation, we can do better (6 transistors!)
 - Fast, maintains data as long as power applied
- ❖ **Dynamic RAM** (DRAM) - 1 transistor per bit
 - Denser but slower, relies on “capacitance” to store data, needs constant “refreshing” of data to hold charge on capacitor

Also, non-volatile memories: ROM, PROM, flash, ...


Dynamic RAM

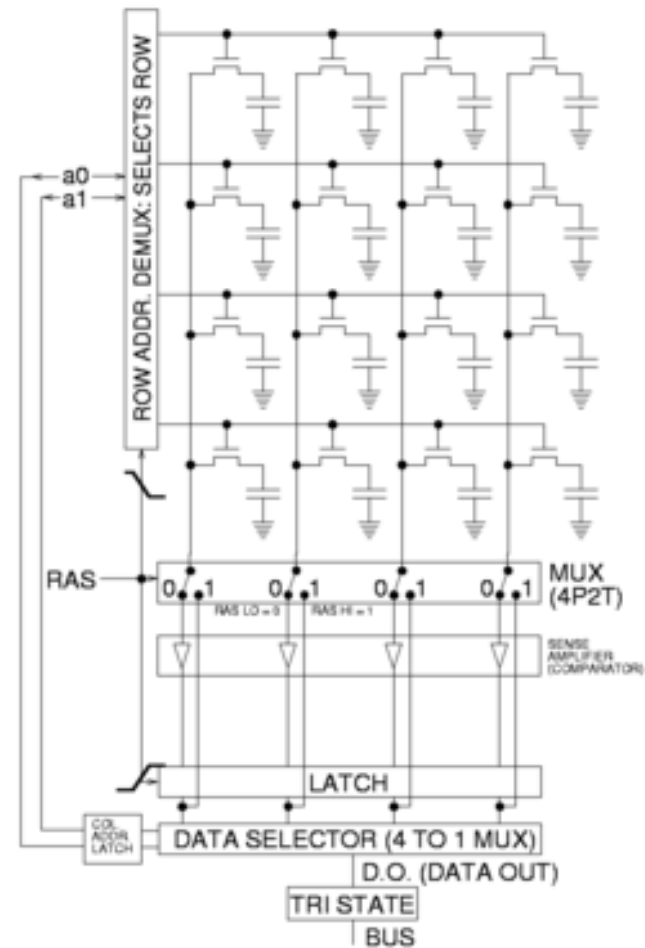- Information stored as charge on capacitors
- Capacitors *leak* so values have to be 'refreshed' continually
- As memory chips get larger, access times tend to increase. The processor spends more time waiting for data.
 - This is a major issue limiting computer systems performance



Dynamic RAM

 An Efficient 2^2 by 3-bit Memory - Single Port




What is different?

D-latch


(instead of D-FF)
Makes this memory writeable when clock is HIGH, instead of on positive edge of CLK

Also uses less transistors per bit!

 Efficient 2^2 by 3-bit Memory - Single Port - SRAM Cell



A 6 Transistor D-Latch!

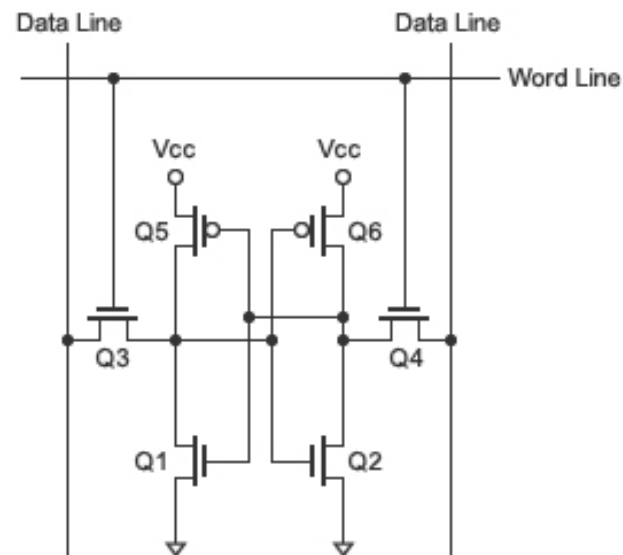


Lecture Outline

- ❖ Review
 - D Latch & Clock
 - D Flip Flops
- ❖ Registers
- ❖ Memory at a high level
- ❖ Memory using flip flops
- ❖ **Memory Hierarchy**

Data Access Time

- ❖ Data is stored on a physical piece of hardware
- ❖ The distance data must travel on hardware affects how long it takes for that data to be processed
- ❖ Example: data stored closer to the CPU is quicker to access
 - We will see this as we discuss memory vs registers in RISC-V programming
 - As we go further from the CPU, storage space goes up, but access times increase

Processor-Memory Gap

 

- ❖ Processor speed kept growing ~55% per year
- ❖ Time to access memory didn't grow as fast ~7% per year
- ❖ Memory access would create a bottleneck on performance

Cache


- ❖ Pronounced “cash”
- ❖ English: A hidden storage space for equipment, weapons, valuables, supplies, etc.
- ❖ Computer: Memory with shorter access time used for the storage of data for increased performance. Data is usually either something frequently and/or recently used.

Principle of Locality

- ❖ The tendency for the CPU to access the same set of memory locations over a short period of time
- ❖ Two main types:
 - **Temporal Locality:** If we access a portion of memory, we will likely reference it again soon
 - **Spatial Locality:** If we access a portion of memory, we will likely reference memory close to it in the near future.
- ❖ Caches take advantage of these tendencies with the cache policies to decide what data is stored in the cache.

Memory Hierarchy

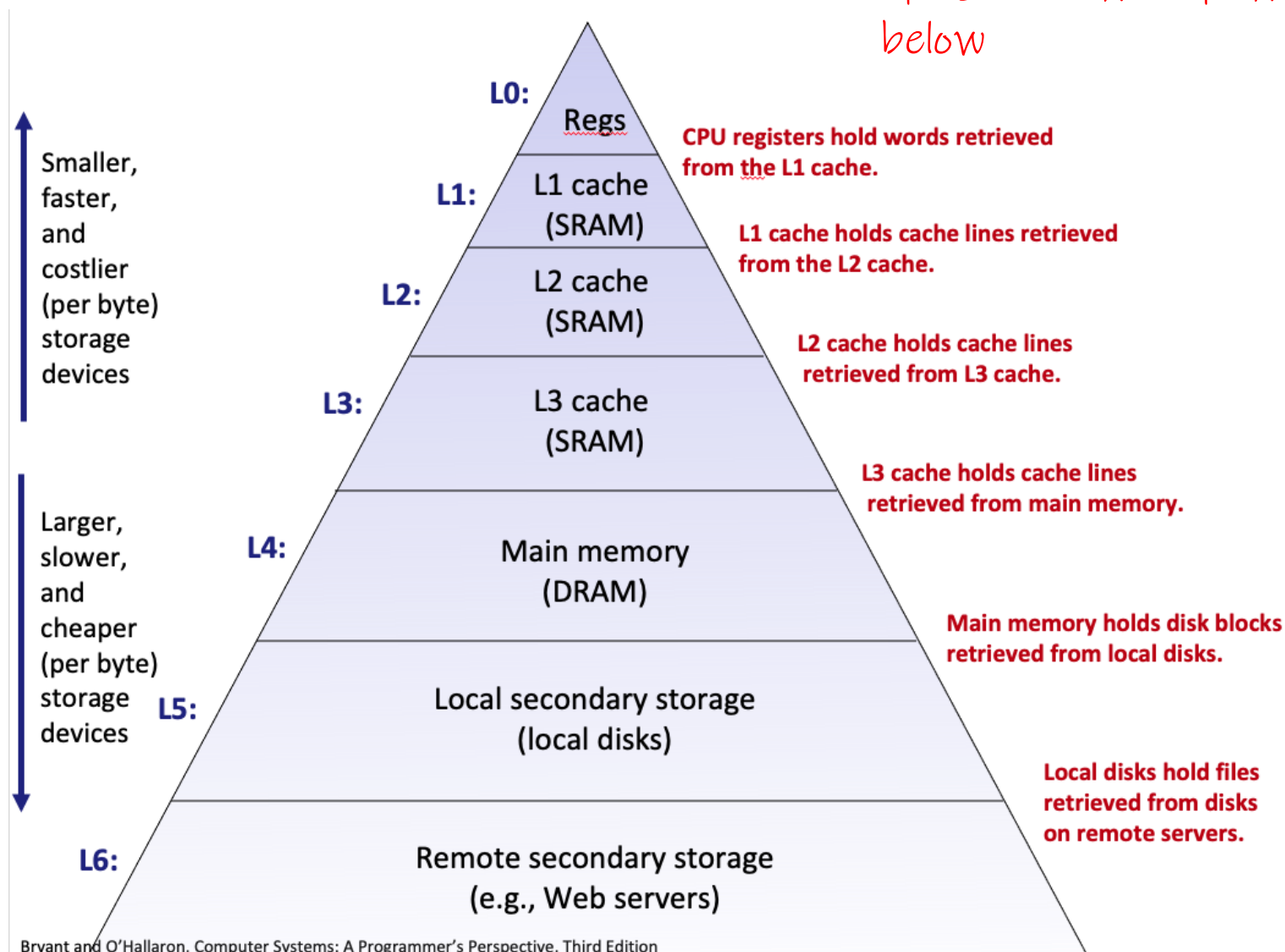Each layer can be thought of as a "cache" of the layer below



And that's it; enjoy your weekend and see you on Tuesday for the Midterm Review!

