

Midterm Review

Introduction to Computer Systems, Fall 2024

Instructors: Joel Ramirez Travis McGaha

Head TAs: Adam Gorka Daniel Gearhardt
Ash Fujiyama Emily Shen

TAs:

Ahmed Abdellah

Ethan Weisberg

Maya Huizar

Angie Cao

Garrett O'Malley Kirsch

Meghana Vasireddy

August Fu

Hassan Rizwan

Perrie Quek

Caroline Begg

Iain Li

Sidharth Roy

Cathy Cao

Jerry Wang

Sydney-Shea Cohen

Claire Lu

Juan Lopez

Vivi Li

Eric Sungwon Lee

Keith Mathe

Yousef AlRabiah

Midterm Review: Which Topic Next?

- ❖ Binary & 2C
- ❖ Binary C Programming
- ❖ C: Memory Diagrams
- ❖ C Programming: Strings & Output Parameters
- ❖ C Programming: Malloc & Double Pointers
- ❖ CMOS, PLA, Gates
- ❖ Gate Delay
- ❖ Combinatorial Logic: Mux

Logistics

- ❖ Midterm Exam: **This Thursday “in lecture”**
 - Details released on the course website
- ❖ Midterm Review in recitation
 - @4pm tomorrow (DRL 3C6)
 - Extra Recitation offering at 7:30 tomorrow (Towne 100)
- ❖ HW04 Sample solutions and grades posted yesterday
- ❖ HW05 Sample Solutions (and grades probably) posted tonight

Binary & 2C

- ❖ There are about 236 students in the class and 27 staff. If we wanted to assign each of these individuals a unique numerical ID, how many bits would each ID need to be?

- ❖ Translate:
 - -1 into 4-bit 2C

 - 7 into 4-bit 2c

 - 7 into 8-bit 2c

 - 5 into 3bit unsigned

Binary C Programming

- ❖ Write the function `reverse_bits()` which takes an unsigned integer and returns a new unsigned integer but with the bits reversed
 - Assume `unsigned int` is 32 bits long
 - Input: `0000 ... 0001` returns `1000 ... 0000` (only 1 bit is a 1)
 - Input: `1111 ... 1111` returns `1111 ... 1111` (all bits are 1)

```
unsigned int reverse_bits(unsigned int num) {
```

```
}
```

C: Memory Diagrams

```
typedef struct {  
    int x;  
    int y;  
} pair;
```

```
typedef struct {  
    pair* data;  
    size_t len;  
} pair_arr;
```

```
pair_arr make_pair_arr(size_t len, pair p) {  
    pair_arr result;  
    result.len = len;  
    result.data = malloc(sizeof(pair) * len);  
    for (size_t i = 0; i < len; i++) {  
        p.x += i;  
        p.y += i;  
        result.data[i] = p;  
    }  
    return result;  
}
```

```
int main() {  
    pair p = (pair) {0, 1};  
    pair_arr a = make_pair_arr(3, p);  
    printf("%d %d\n", p.x, p.y);  
    for (size_t i = 0; i < a.len; i++) {  
        p = a.data[i];  
        printf("%d %d\n", p.x, p.y);  
    }  
}
```

What does this print?
What memory errors are there?
How do we fix them?

C Strings & Output Params

- ❖ Complete the following function (on Codio)

```
// given a string, allocates and creates a new duplicate  
// of it and returns it through the output parameter "out".  
// Returns false on error, returns true otherwise
```

```
bool str_duplicate(char* str, char** out) {
```

```
}
```

C Strings & Output Params

❖ Complete the main function

```

// given a string, duplicates it and returns it through
// the output parameter "out". Returns false on error
// returns true otherwise
bool str_duplicate(char* str, char** out);

// duplicates a string literal,
// prints the duplicate, and runs without errors
int main(int argc, char** argv) {
    char* sample = "Hello World!";

}
    
```


This problem may be on the harder side.

If space would have given you a memory diagram of the output

C Programming: Malloc & Double Pointers

- ❖ We want to make a module that implements 2d matrices in C. We define the following struct which holds a dynamically allocated 2-dimensional array.

```
typedef struct {
    int** data;
    int rows;
    int cols;
} matrix;
```

- ❖ Implement the `create_matrix()` function which creates a matrix on the heap with the specified rows and cols. Assume malloc does not fail.
- ❖ Example: `create_matrix(2, 3)` should create a 2x3 matrix. data points to 2 `int*`, each of those point to 3 `ints`.

```
matrix* create_matrix(int rows, int cols) {
    // Implement this function. You need more than 1 line.
}
```

C Programming: Malloc & Double Pointers

- ❖ We want to make a module that implements 2d matrices in C. We define the following struct which holds a dynamically allocated 2-dimensional array.

```
typedef struct {
    int** data;
    int rows;
    int cols;
} matrix;
```

- ❖ Implement the `free_matrix()` function which deallocates the matrix allocated in `create_matrix()`
- ❖ Example: `create_matrix(2, 3)` should create a 2x3 matrix. data points to 2 `int*`, each of those point to 3 `ints`.

```
void free_matrix(matrix* m) {
    // Implement this function.
}
```

CMOS, PLAS, GATES

- ❖ Create a circuit that takes in an unsigned 4-bit input I ($I_3I_2I_1I_0$), and outputs a 1 if and only if the 4-bit input is a non-zero multiple of 7
 - List the outputs that result in a 1 for the output
 - Create a corresponding CMOS circuit
 - Can assume you have the inverses of the Input bits
 - Create a corresponding PLA circuit
 - Create a corresponding gate level non-PLA circuit

CMOS, PLAS, GATES


- ❖ Create a circuit that takes in an unsigned 4-bit input I ($I_3I_2I_1I_0$), and outputs a 1 if and only if the 4-bit input is a non-zero multiple of 7
 - List the outputs that result in a 1 for the output
 - 7 (0b0111) and 14 (0b1110)

CMOS

- ❖ Create a circuit that takes in an unsigned 4-bit input I ($I_3I_2I_1I_0$), and outputs a 1 if and only if the 4-bit input is a non-zero multiple of 7. You can assume you have inverse of the input signals.
 - Overall Expression: $(\sim I_3 \& I_2 \& I_1 \& I_0) \mid (I_3 \& I_2 \& I_1 \& \sim I_0)$


CMOS Strategy 1 (Starting with PDN)

- ❖ Overall Expression: $(\sim I_3 \& I_2 \& I_1 \& I_0) \mid (I_3 \& I_2 \& I_1 \& \sim I_0)$
- ❖ PDN Expression:
 - $\sim((\sim I_3 \& I_2 \& I_1 \& I_0) \mid (I_3 \& I_2 \& I_1 \& \sim I_0))$ // negate
 - $\sim(\sim I_3 \& I_2 \& I_1 \& I_0) \& \sim(I_3 \& I_2 \& I_1 \& \sim I_0)$ // De Morgan's
 - $(I_3 \mid \sim I_2 \mid \sim I_1 \mid \sim I_0) \& (\sim I_3 \mid \sim I_2 \mid \sim I_1 \mid I_0)$ // De Morgan's
- ❖ Translated to PDN:

 

CMOS Strategy 1 (Starting with PDN)


- ❖ Flip PDN into PUN:

 

CMOS Strategy 1 (Starting with PDN)


- ❖ Connect PDN and PUN:

Not the only possible answer

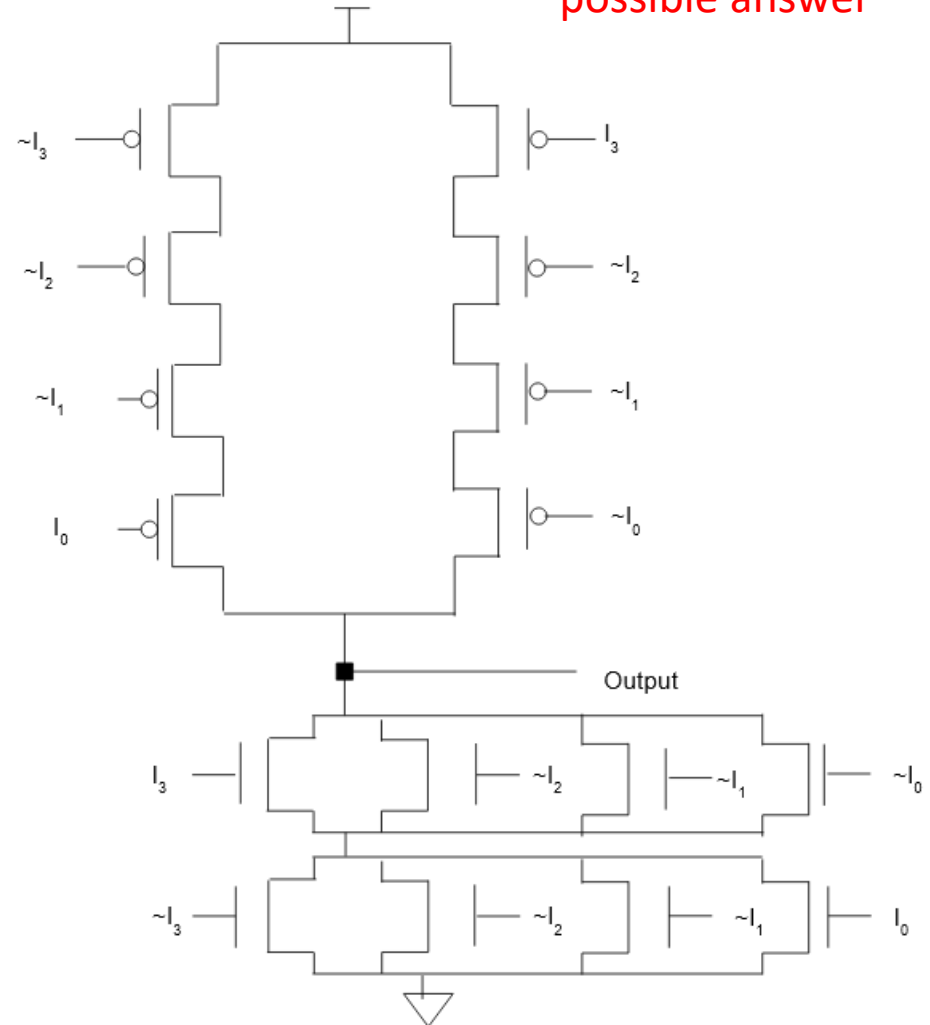



CMOS Strategy 2 (Starting with PUN)

 - ❖ Take the original expression:
 - $(I_3 \& I_2 \& I_1 \& \sim I_0) \mid (\sim I_3 \& I_2 \& I_1 \& I_0)$
- ❖ Translate it directly into PDN but add a negation to each input
 - This is because PMOS transistors are “naturally negating”
 - E.g., $\sim I_3$ becomes $\sim\sim I_3 == I_3$



CMOS Strategy 2 (Starting with PUN)

- ❖ Flip PUN to get PDN

  

PLA



- ❖ Create a circuit that takes in an unsigned 4-bit input I ($I_3I_2I_1I_0$), and outputs a 1 if and only if the 4-bit input is a non-zero multiple of 7

Non-PLA

- ❖ Create a circuit that takes in an unsigned 4-bit input I ($I_3I_2I_1I_0$), and outputs a 1 if and only if the 4-bit input is a non-zero multiple of 7

Gate delay pt.1

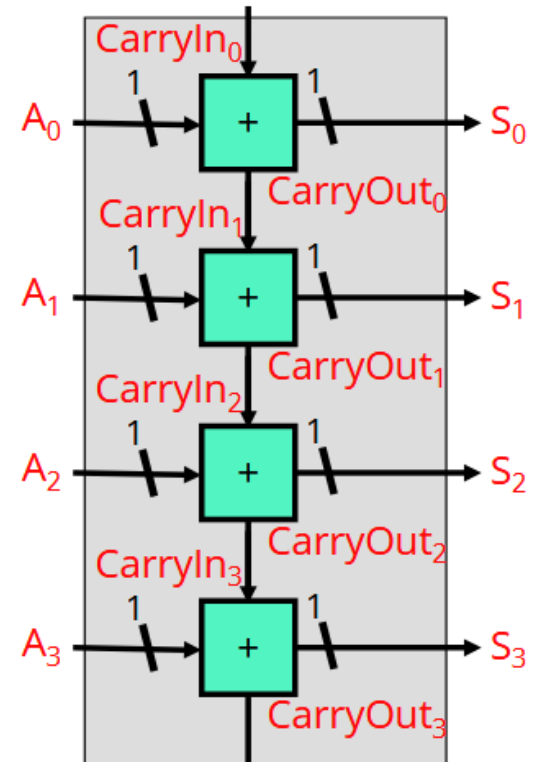
 
- ❖ Given the 4-bit incrementor that we created in lecture, how long do we have to wait to make sure that the output of the incrementor matches the input?
 - Assume that each gate has a 1ns delay
 - You can ignore delay from inverters



Gate delay pt.2

- ❖ The 4-bit incrementor that we created in lecture is currently in a stable state showing the output of $1 + 0110$. If the A input signals were to simultaneously flip to 0111 , what would all signals be after $2ns$

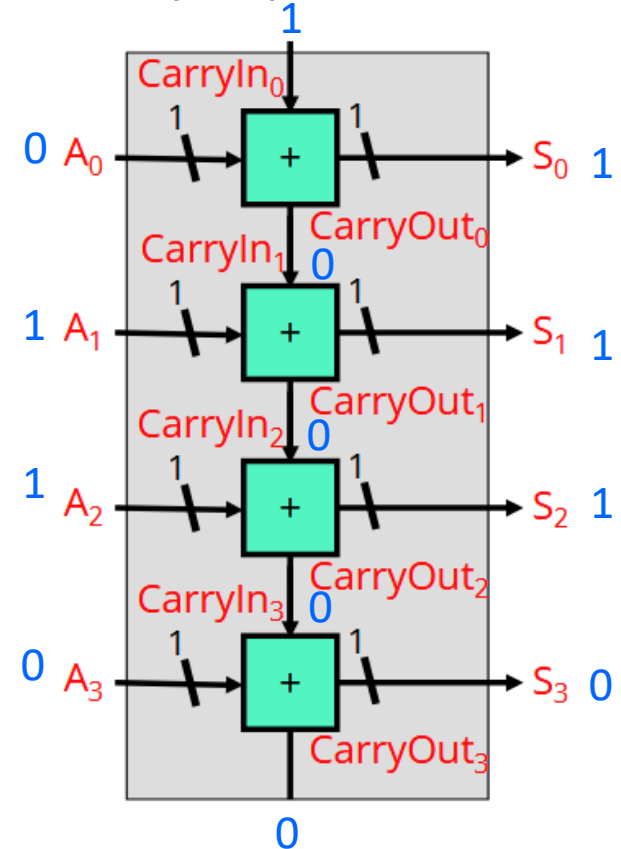 - Assume that each gate has a $1ns$ delay
- Ignore delays from inverters
- $CarryIn_n$ stays the same



Combinatorial Logic: Mux

- ❖ Given inputs I_0 I_1 I_2 I_3 and selector bits S_1 and S_0 draw a logic circuit using 2-to-1 muxes to implement the 4-to-1 MUX. You can assume you have access to each bit/wire.
- ❖ Requirements:
 - If $S_1S_0 == 00$, the output should be I_0
 - If $S_1S_0 == 01$, the output should be I_1
 - If $S_1S_0 == 10$, the output should be I_2
 - If $S_1S_0 == 11$, the output should be I_3
 - Clearly label the inputs, select lines, and output
- ❖ Yes, you are allowed to use more than one 2-to-1 mux

General Questions & Answers

- ❖ Take questions/requests from students