

RISC-V Single Cycle

Introduction to Computer Systems, Fall 2024

Instructors: Joel Ramirez Travis McGaha

Head TAs: Adam Gorka Daniel Gearhardt
Ash Fujiyama Emily Shen

TAs:

Ahmed Abdellah

Ethan Weisberg

Maya Huizar

Angie Cao

Garrett O'Malley Kirsch

Meghana Vasireddy

August Fu

Hassan Rizwan

Perrie Quek

Caroline Begg

Iain Li

Sidharth Roy

Cathy Cao

Jerry Wang

Sydnie-Shea Cohen

Claire Lu

Juan Lopez

Vivi Li

Eric Sungwon Lee

Keith Mathe

Yousef AlRabiah



pollev.com/tqm

❖ Any Questions?

Logistics

- ❖ Midterm: Soontm
 - Edge cases need to be looked at, and a few files need to be rescanned
 - I hope tonight

- ❖ HW07 is out and due this Friday at midnight
 - Should have everything you need after this lecture
 - Autograder is out
 - Simulator is out

- ❖ HW08 comes out this Friday/weekend

Logistics Pt. 2

- ❖ Office Hours this week
 - No Office Hours on Halloween (Thursday)
 - Reduced TA presence at office hours the day after (Friday)

- ❖ Check-in06 out later this week

- ❖ Election happening soon
 - No lecture on Tuesday next week.

Lecture Outline

- ❖ **Von Neuman & Processor Start**
- ❖ RISC-V Single Cycle Processor
 - Decoder
 - Register File
 - ALU
 - Branch unit
 - The Rest
 - “Single Cycle”

This Lecture: Hardware/Software Interface

- ❖ We've looked at some hardware topics and some software topics (C & RISC-V)
- ❖ Today we are looking at the hardware/software interface for the RISC-V ISA
 - How does assembly run on hardware?
 - How do we create hardware that runs assembly code?
- ❖ Hardware details abstracted, uses a lot of the components previously talked about (Mux, Adders, Incrementors, etc.)
 - You will implement something like this in CIS 4710

HW/SW Interface

- ❖ Assembly is a middle ground between software and hardware

- ❖ Software:
 - It can still be very hard to read assembly code
 - More complex coding languages translates into assembly

- ❖ Hardware:
 - Hardware only needs to implement these “simple” instructions.
 - Hardware does not *need* to implement a custom “calculate the Fibonacci sequence” piece of hardware.
 - Instructions translate directly into binary that hardware can read.

Reminder: Instructions are bits

- ❖ An instruction fits in 32-bits (4-bytes, 4 memory locations)
- ❖ These instructions are stored in memory and accessed sequentially
 - When we trace through the code, we are just accessing the next instruction in memory

```
li x0, #32
li x1, #16
li x2, #64

div x1, x2, x1
add x3, x3, x0
sub x0, x2, x3
```

Index # (Address)	Information (Data)
x00	0x.....
x04	0x.....
x08	0x.....
x0C	0x.....
x10	0x.....
x14	0x.....
x18	0x.....


The Von Neumann Loop

- ❖ Von Neumann Processor essentially does:
 - Fetch instruction at Program Counter
 - Decode instruction
 - Execute instruction & Update PC
 - Repeat

- ❖ Critical Requirement
 - Each iteration of this loop must appear **atomic** (All or nothing)
 - Key word from programmer perspective: atomic
 - Maintains sanity
 - Key word from hardware perspective: appear
 - Enables hardware to perform various tricks for performance >:]

An Idea of what we are doing :

 Single Cycle Implementation of the RISC-V ISA (RV32IM)



More RISC-V References!

- ❖ More RISC-V References added to the course website
- ❖ Highly recommend you print out a copy of the “Control Signals Description” handout
- ❖ RISC-V Single Cycle Processor is the diagram on the previous slide, may also want to print this

Lecture Outline

- ❖ Von Neuman & Processor Start
- ❖ **RISCV Single Cycle Processor**
 - **Decoder**
 - **Register File**
 - **ALU**
 - **Branch unit**
 - **The Rest**
 - **“Single Cycle”**

Aside: bit selecting syntax

- ❖ Assume we have a 32-bit pattern called X


- X: `00000000000101010000001010010011`

- ❖ We can refer to a specific subsection of X with the syntax $X[n:m]$


- `X[31:0]` // all 31 bits
 - `X[2:0]` // 3 least most significant bits
 - `X[19:15]` // 5 bits in the middle

Fetch & Decode

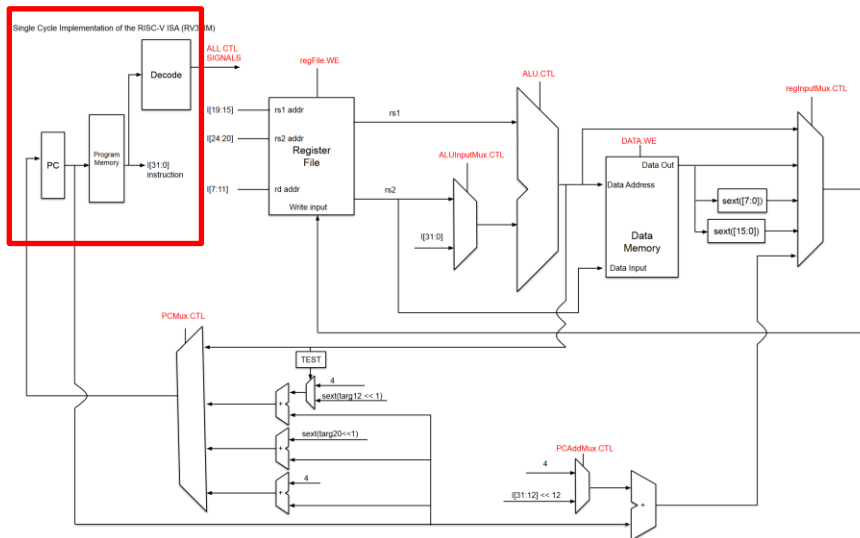- ❖ First & second step: Fetch an instruction and decode it
 - Read instruction at PC in memory (stored as 32 bits)
 - **From those 32-bits, outputs signals to control the processor to execute the instruction.**
 - Common exam question: implement part of the decoder with logic gates.



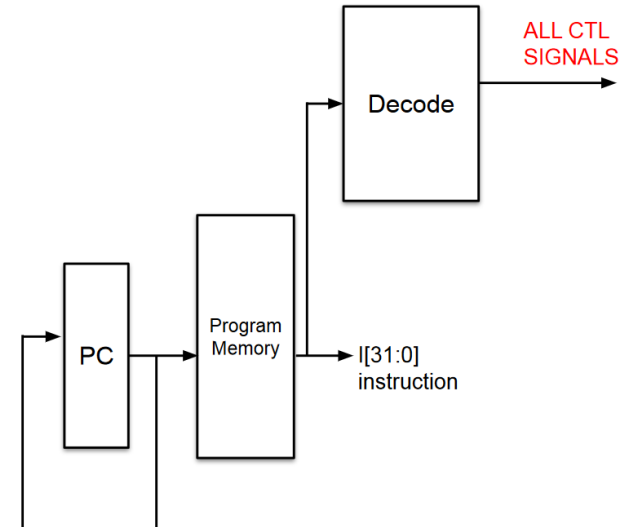
Single Cycle Implementation of the RISC-V ISA (RV32IM)



Fetch & Decode: ADDI x5, x10, 1



- ❖ Throughout this lecture, we will assume we just fetched the instruction `ADDI x5, x10, 1` and decide what the control signals for this should be
- ❖ We have fetched and decoded the instruction, now we must execute it

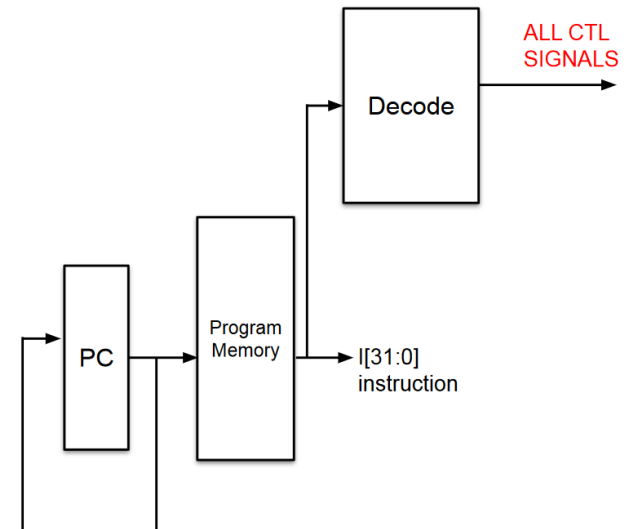Single Cycle Implementation of the RISC-V ISA (RV32IM)





Register File

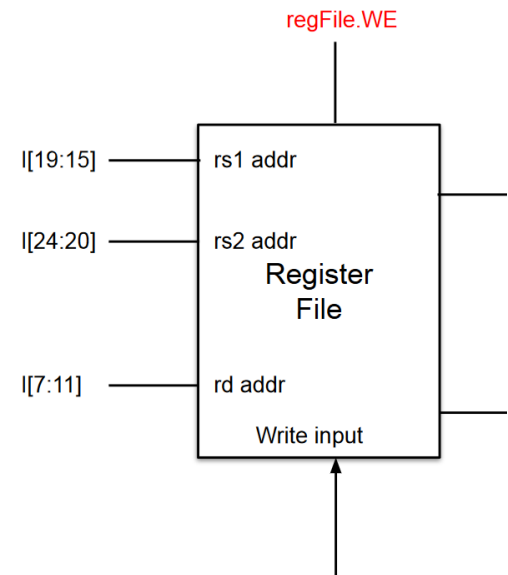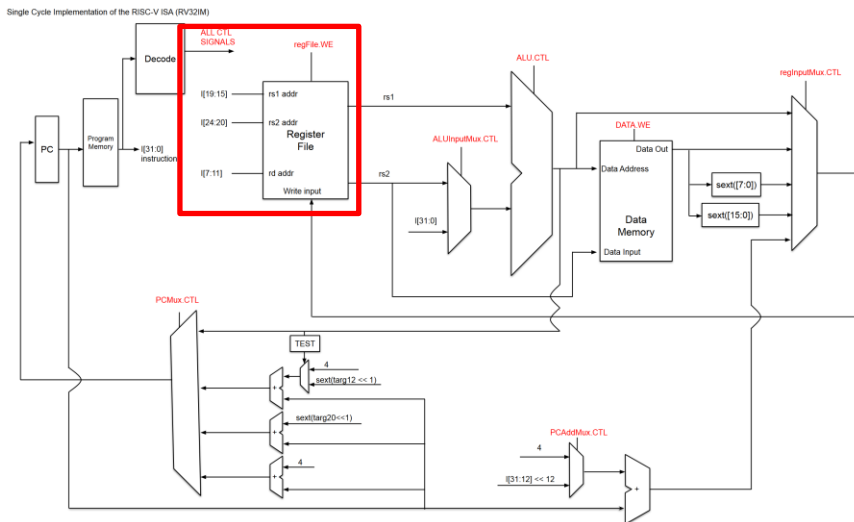- ❖ Array of the 32 general purpose processor registers x0 - x32
- ❖ The registers used are always at the same position in the instruction encoding.
- ❖ Not a typical “File” on a computer
 - (We will talk about regFile.WE later this lecture)



ALU: Arithmetic Logic Unit

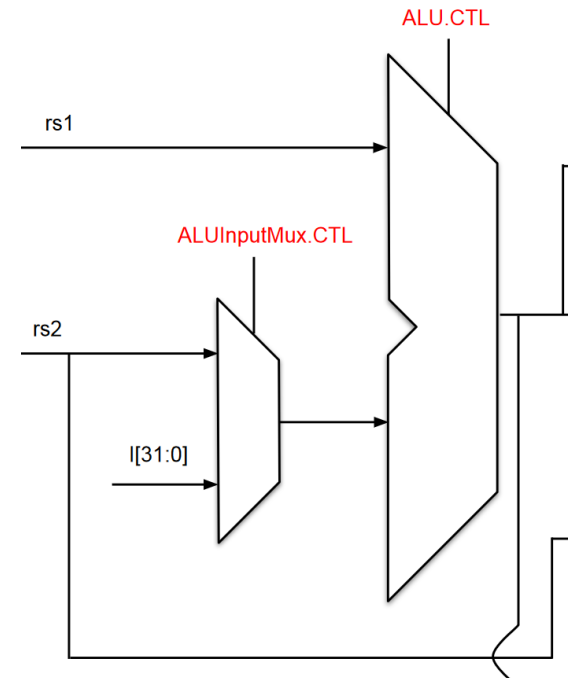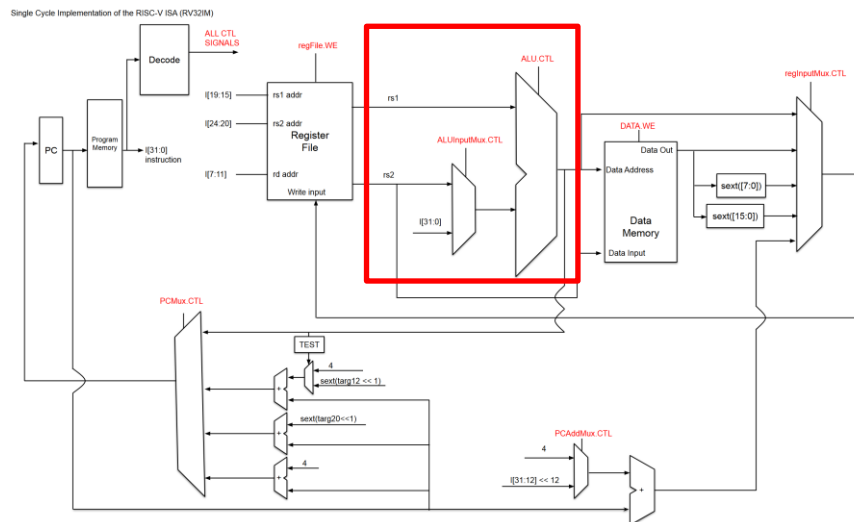- ❖ Performs Arithmetic and Logical operations
 - Where most instructions perform their “work”
- ❖ Use Control Signals to decide
 - what operation is performed
 - what the inputs are



ALU Input Mux: ADDI x5, x10, 1

- ❖ ALUInputMux.CTL
 - This signals decide what should be used as input for the ALU (thing that does most arithmetic / logical operations)
- ❖ How to decide signals generally:
 - Look at the options available for this control signal (Single Cycle handout or Control Signal Description handout)
 - Determine which signal matches up for the current instruction


❖ ADDI Example:

- Do we use an rs2 or an immediate for ADDI?

`iiii iiiii iiiii ssss s000 dddd d001 0011`


iiii iiiii iiiii

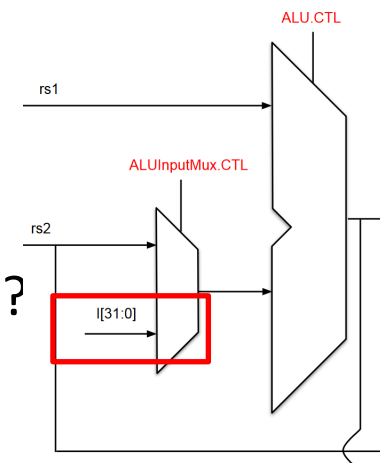- From the encoding directly
- so AluInputMux CTL is 1



Control Signals Description Handout

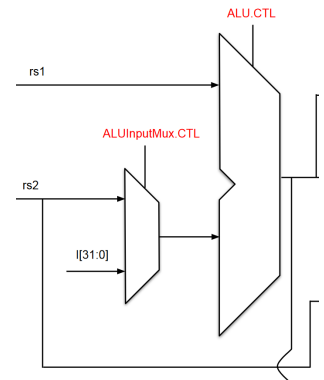- ❖ Can use the Control Signals Description Handout to look up signals
- ❖ ADDI: Do we use an rs2 or do we use the bits from the instruction encoding?



Signal Name	# of bits	value	action
ALUInputMux.CTL	2	0	Second input to ALU is rs2
		1	Second input to ALU is the 32 bits of the instruction


- ❖ Then ALUInputMux.CTL should be 1

ALU: ADDI x5, x10, 1

- ❖ ALU.CTL decides which arithmetic/logical operation to perform.
 - 36 different options: look at the control signals description sheet
- ❖ ADDI operation is $C = A + B$, but B is sign extended from the immediate, So ALU.CTL is 0



Signal Name	# of bits	value	action
ALU.CTL	6		
Arithmetic Ops (I)	0		$C = A + \text{se}(B[31:20])$
	1		$C = A < \text{se}(B[31:20]) ? 1 : 0$
	2		$C = A < \text{unsigned se}(B[31:20]) ? 1 : 0$
	3		$C = A \wedge \text{se}(B[31:20])$
	4		$C = A \mid \text{se}(B[31:20])$

	5		$C = A \& \text{se}(B[31:20])$
	6		$C = A \ll \text{se}(B[24:20])$
	7		$C = A \gg \text{se}(B[24:20])$
	8		$C = A \gg \gg \text{se}(B[24:20])$

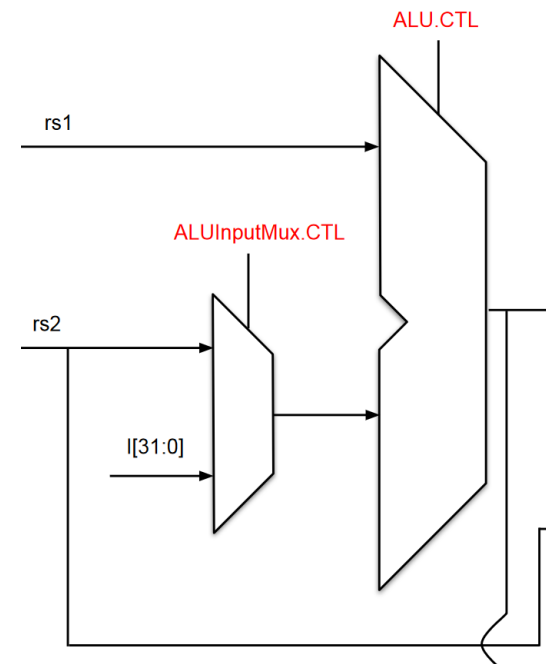


Branch Unit

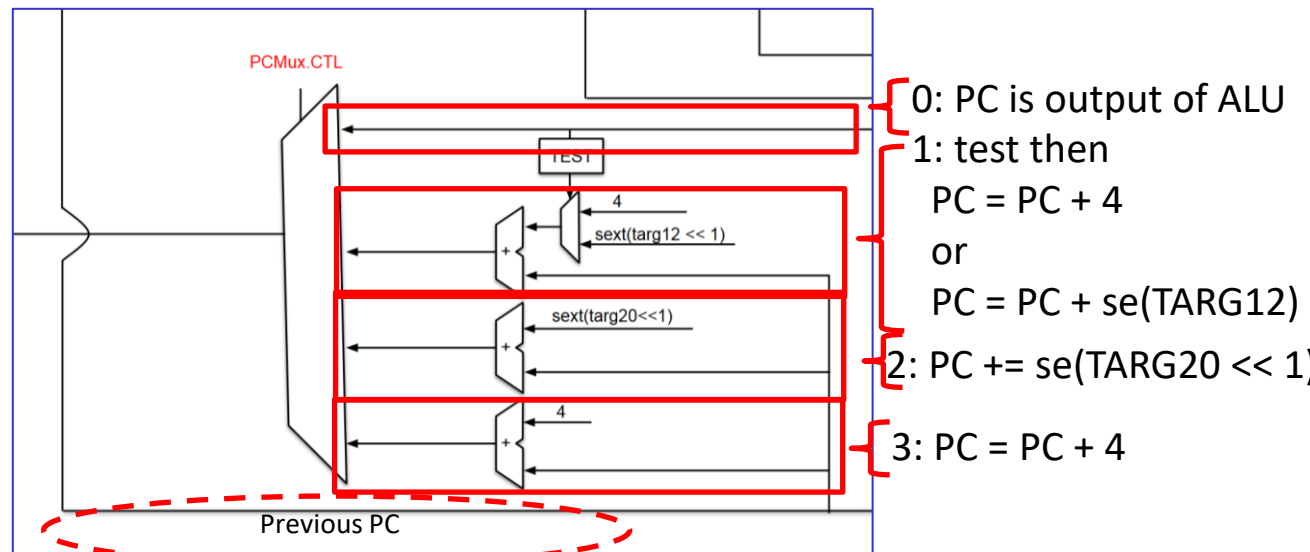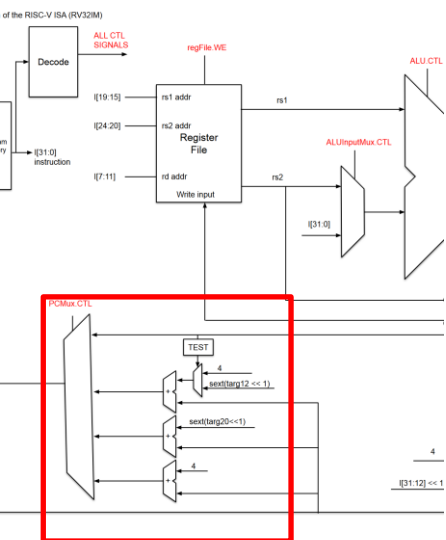- ❖ Updates PC
- ❖ PCMux.CTL: decides how PC is updated




Branch Unit: ADDI x5, x10, 1

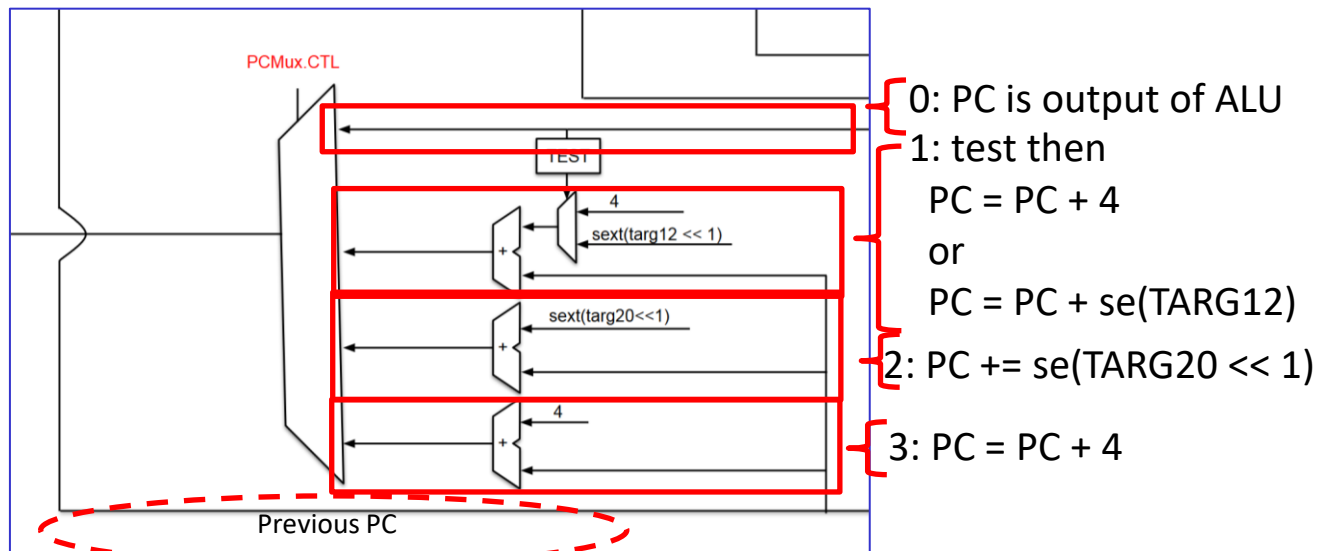- ❖ How does ADDI x5, x10, 1 update the PC?
 - $PC = PC + 4$ so, PCMux.CTL is 3



Data Memory

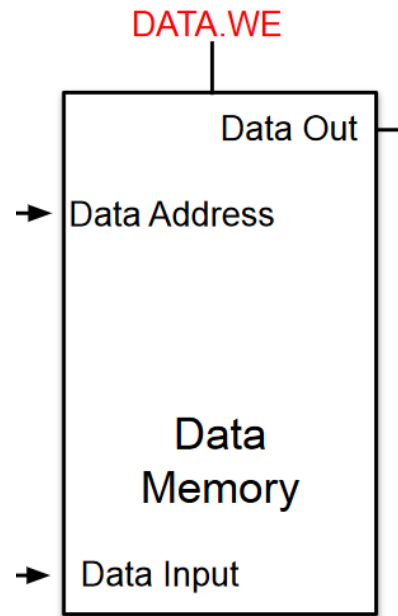
- ❖ Contains the data memory of our program
- ❖ Takes in the:
 - Address of the data to access
 - What data to write at that address
- ❖ Outputs the data at the specified address
- ❖ DATA.WE decides if we are updating any data in memory.
 - Does ADDI update any data in memory?
 - No, so DATA.WE for ADD is 0



Data Memory (cont.)


- ❖ DATA.WE decides if we are updating any data in memory.
 - Not shown with ADDI instruction: DATA.WE is 4 bits.

 - ❖ Why is DATA.WE 4-bits?
 - We can write 0, 1, 2, or 4-bytes to data memory.
 - Each byte we could write will have “its” own WE bit to determine if we write that byte.
 - E.g. if we wanted to write all 4-bytes of data input, then DATA.WE would be 0b1111 (15)



Register File: regFile.WE

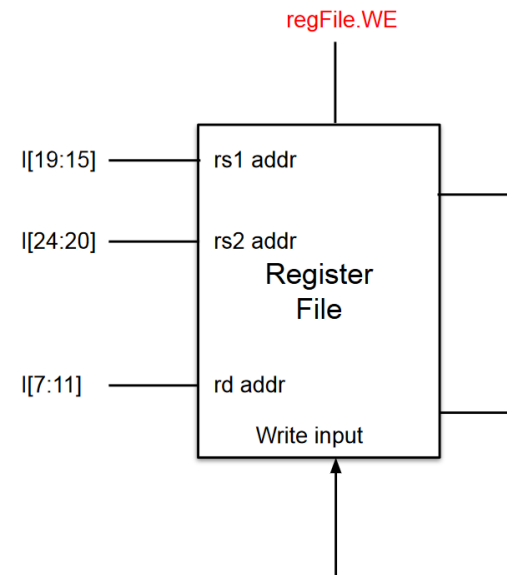
- ❖ regFile.WE: write-enable for the register file. If we are writing to a register it should be 1, 0 otherwise
 - ADD writes to a register, so regFile.WE is 1



regInputMux.CTL



- ❖ Decides what gets written back to the register file
 - 0 = output of ALU
 - 1 = 4-bytes of data memory
 - 2 = 1-byte of data memory
 - 3 = 2-bytes of data memory
 - 4 = PC + <something>

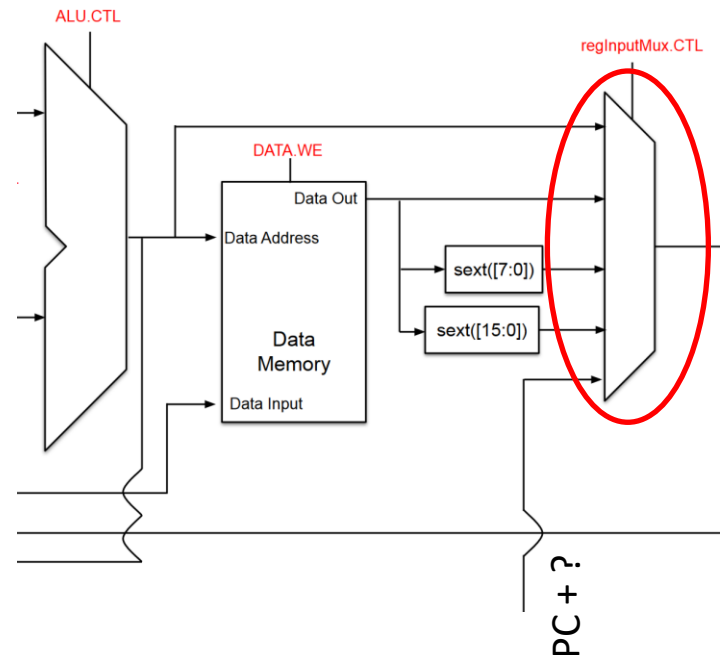- ❖ What does ADDI store into a register?
 - Output of ALU, so for ADDI `regInputMux.CTL = 0`




PCAddMux.CTL

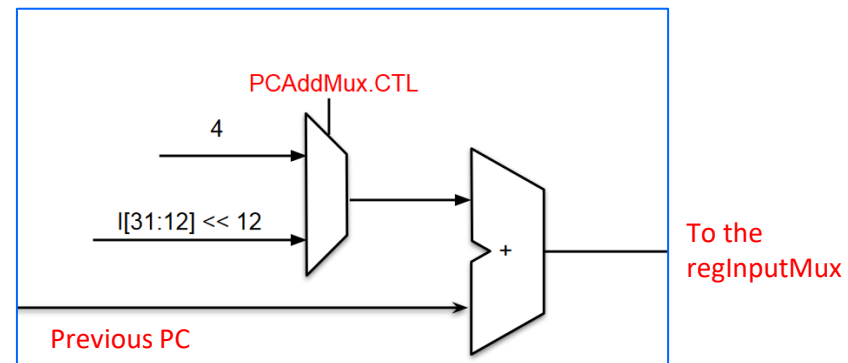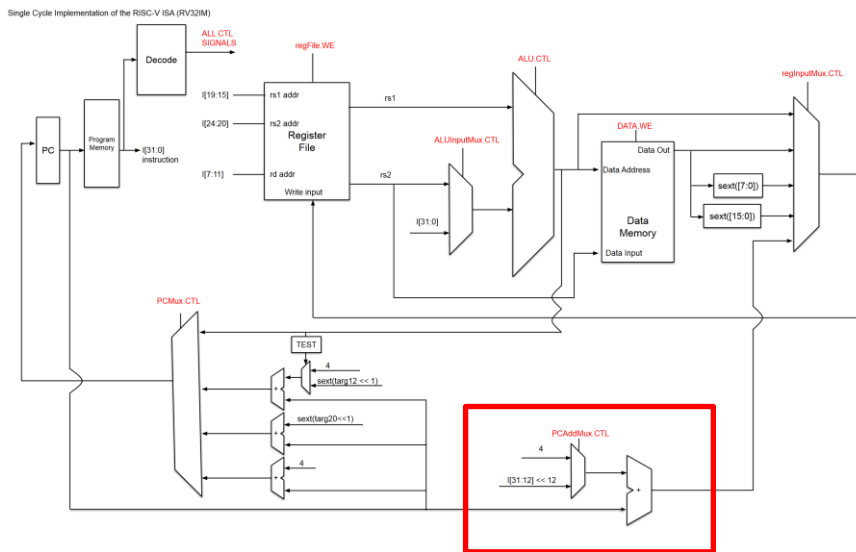- ❖ When we store the PC to the register file, we also have to add something to it. This decides what we add to the PC value that would get written back to the register file




PCAddMux.CTL

- ❖ When we store the PC to the register file, we also have to add something to it. This decides what we add to the PC value that would get written back to the register file
- ❖ What does ADDI do with the PC value stored to register file?
 - **It doesn't store the PC into the register file.**
 - **If we look at the diagram given our other signals, the output of this is unused.**
 - **We can mark this signal as X (unused) for the ADD instruction**
 - **Will not always be X, sometimes it will be 0 or 1.**
 - **Other signals can be X too**

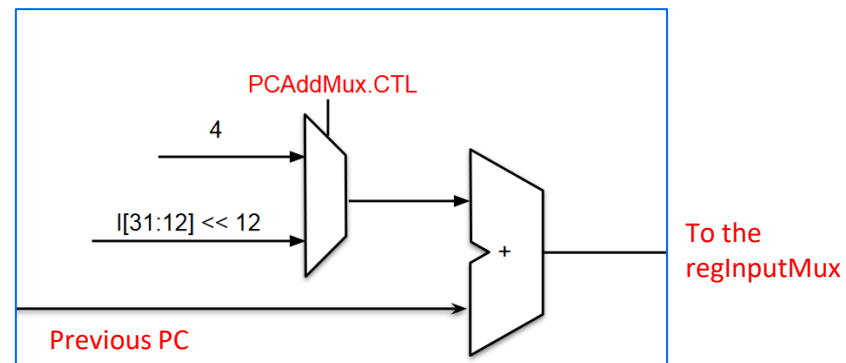


The Complete Picture

 Single Cycle Implementation of the RISC-V ISA (RV32IM)



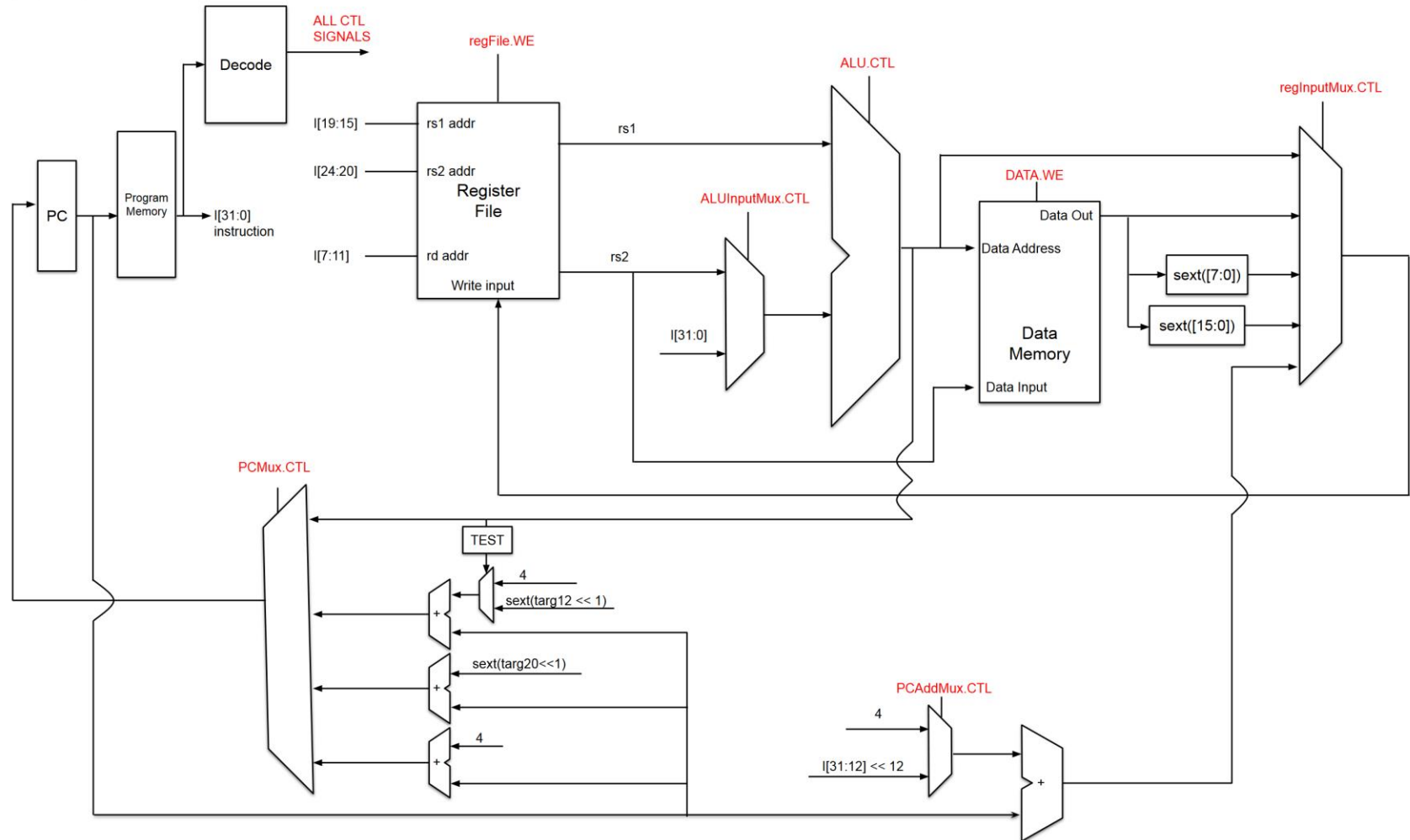
Questions?

Single Cycle Implementation of the RISC-V ISA (RV32IM)



Reminder: Circuits are not Code

- ❖ We are dealing with circuits, not software
 - All components are “working” all the time.
 - We may not be using their output all the time though.
- ❖ WE Signals always matter, we never “don’t care” about them
 - Example: ADDI and DATA.WE
 - ADDI doesn’t use data memory at all, but the data address and data input will still be some value (which may be garbage)
 - We do NOT want to write garbage to memory so DATA.WE should be 0

 



Poll Everywhere

pollev.com/tqm

- ❖ What are the control signals for the LUI instruction?
 - 7 different control signals questions on PollEv
- ❖ Probably want to pull up the Control Signals Description, RISC-V Encoding, and Single Cycle Sheet
- ❖ If you are reading the slides after lecture and want to go over this, should probably watch the lecture recording

“Single Cycle”

- ❖ This whole Lecture I’ve been talking about processor with the term “Single Cycle”
 - This means that one instruction is executed in one clock cycle.
 - That means the length of the program is directly proportional to the number of instructions executed
- ❖ “Single Cycle” is a convenient way for programmers to think about the processor, but most current processors are **not** like this
 - More in CIS-5710 (Or a special topic at the end of the semester)



pollev.com/tqm

❖ Any Questions On Registration?