# Recitation 9/25

Welcome back! :)

# Vote Ash, Ahmed, and Garrett for best recitation TAs

#### Schedule for Today

- Connecting circuits and boolean algebra
- Logic Gates
- CMOS
- User input demo in C (echo.c)

## **Boolean Algebra**

#### **Boolean rules**

- Identity
  - A & 1 = A
  - A & 0 = 0
  - A | 1 = 1
  - A | 0 = A
  - ~~A = NOT NOT A = A
- Associative
  - A & (B & C) = (A & B) & C
  - A | (B | C) = (A | B) | C
- Distributive
  - A & (B | C) = (A & B) | (A & C)
  - A | (B & C) = (A | B) & (A | C)

- More Identity
  - A & A = A
  - A | A = A
  - A & ~A = 0
  - A | ~A = 1
- De Morgan's Law
  - ~(A & B) = ~A | ~B
  - ~(A | B) = ~A & ~B

#### Other formats you might see:

- A & B  $\rightarrow$  A \* B or A  $\wedge$  B
- $A \mid B \rightarrow A + B \text{ or } A \lor B$
- $\sim A \rightarrow !A \text{ or } A' \text{ or } \neg A$

Intuitively, you can think of A \* B as saying "both A **and** B have to be 1 for this not to be 0" and A + B as saying "only one of these have to be 1 for this to be greater than 0".



## Simplify: $Z = A \& ((A | \sim A) | \sim B)$

## Z = A & ((A | ~A) I ~B)

## $Z = A \& (True I \sim B)$

Z = A & True = A

## **Logic Gates**

Symbols





NOR Gate



## Write a truth table for Z:



А	В	Z
0	0	0
0	1	0
1	0	1
1	1	1

#### So Z = A??????

...yes

## Write a truth table for:



## Answer: only for people who go to recitation

### **Transistor Review**

#### Label & Conditions?



#### A little Chemistry

1					1	5 ←		– Atomi	ic numbe	er							18
1 H Hydrogen	9				Phoe	P «	6									2 He Helium	
3 Li	4 Be Beryllium	[Ne] 3s <sup>2</sup> 3p <sup>3</sup> Nonmetal						Electron configuration			5 B Boron	6 C Carbon	7 <b>N</b> Nitrogen	8 O Oxygen	9 F Fluorine	10 Ne Neon	
11 Na Sodium	12 Mg <sup>Magnesium</sup>	3	4	5	6	7	8	9	10	11	12	13 Al Aluminium	14 Si Silicon	15 P Phosphorus	16 S Sulfur	17 Cl Chlorine	18 Ar Argon
19 <b>K</b> Potassium	20 Ca Calcium	21 Sc Scandium	22 Ti Titanium	23 Va Vanadium	24 Cr Chromium	25 Mn <sup>Manganese</sup>	26 Fe	27 Co Cobalt	28 <b>Ni</b> Nickel	29 Cu Copper	30 Zn <sup>Zinc</sup>	31 Ga Gallium	32 Ge Germanium	33 As Arsenic	34 Se Selenium	35 Br Bromine	36 <b>Kr</b> <sub>Krypton</sub>
37 <b>Rb</b> Rubidium	38 <b>Sr</b> Strontium	39 <b>Y</b> Yttrium	40 Zr Zirconium	41 <b>Nb</b> Niobium	42 Mo Molybdenum	43 Tc Technetium	44 <b>Ru</b> Ruthenium	45 <b>Rh</b> Rhodium	46 <b>Pd</b> Palladium	47 Ag Silver	48 Cd Cadmium	49 In Indium	50 <b>Sn</b> <sup>Tin</sup>	51 Sb Antimony	52 Te Tellurium	53 I Iodine	54 Xe <sub>Xenon</sub>
55 Cs <sup>Cesium</sup>	56 Ba Barium	57 - 71 lanthanides	72 <b>Hf</b> Hafnium	73 Ta Tantalum	74 W Tungsten	75 <b>Re</b> Rhenium	76 Os Osmium	77 Ir Iridium	78 Pt Platinum	79 Au <sub>Gold</sub>	80 Hg Mercury	81 <b>Tl</b> Thallium	82 Pb Lead	83 <b>Bi</b> Bismuth	84 Po Polonium	85 At Astatine	86 <b>Rn</b> Radon
87 <b>Fr</b> Francium	88 Ra Radium	89 - 103 Actinides	104 <b>Rf</b> Rutherfordium	105 Db Dubnium	106 <b>Sg</b> Seaborgium	107 Bh Bohrium	108 <b>Hs</b> Hassium	109 Mt Meitnerium	110 DS Darmstadtium	111 Rg Roentgenium	112 Cn Copernicium	113 <b>Nh</b> Nihonium	114 <b>Fl</b> Flerovium	115 Mc <sup>Moscovium</sup>	116 <b>Lv</b> Livermorium	117 <b>TS</b> Tennessine	118 <b>Og</b> Oganesson
		57 <b>La</b>	58 <b>Ce</b>	59 <b>Pr</b>	60 <b>Nd</b>	61 <b>Pm</b>	62 <b>Sm</b>	63 Eu	64 <b>Gd</b>	65 <b>Tb</b>	66 <b>Dy</b>	67 <b>Ho</b>	68 <b>Er</b>	69 <b>Tm</b>	70 <b>Yb</b>	71 Lu	
		89 Actinium	90 Th Thorium	Praseodymium 91 Pa Protactinium	Neodymium 92 U Uranium	Promethium 93 Np Neptunium	Samarium 94 <b>Pu</b> Plutonium	Europium 95 Am Americium	Gadolinium 96 Cun Curium	Terbium 97 <b>Bk</b> Berkelium	98 Cf Californium	Holmium 99 <b>Es</b> Einsteinium	Erbium 100 Fm Fermium	Thulium 101 Md Mendelevium	Ytterbium 102 No Nobelium	Lutetium 103 Lr Lawrencium	

hemistry Topics

#### A little Chemistry



## CMOS

#### So what is CMOS and what's its purpose?

- CMOS: Complementary Metal Oxide Semiconductor





#### Parts of a CMOS network!



#### **Pull Up Network**



#### **Pull Down Network**

A Simple Example: AND2

#### 1) Boolean function: $Y = (A^*B)$

ABY

#### 3) PUN

#### 4) PDN

#### Going from CMOS -> Function



To connect Ground to Y:  $A = B = \sim C = 1$ 

Therefore:  $GND \rightarrow Y = A \& B \& \sim C$ 

Invert this expression:  $\sim$ (A & B &  $\sim$ C)

Optional Simplify: ~A | ~B | C

# Going from Function -> CMOS Y = C' + (A'\*B')



If you're looking for this code, it's in edpost #589 titled "Recitation today!"

## Demo: echo.c

This is helpful for HW03