

University of Pennsylvania
Department of Electrical and System Engineering
Circuit-Level Modeling, Design, and Optimization for Digital Systems

ESE3700, Spring 2024

Final

Tuesday, May 7

- Problem weightings shown.
- Calculators allowed.
- Closed book = No text or notes allowed.
- Additional workspace in exam book. Note where to find work in exam book if relevant.

Name: Answers

Q1	
Q2	
Q3	
Q4	
Q5	
Total	Mean: 71.4, Stdev: 13.1

Default technology:

- 22nm Low Standby Power Process (LSTP)
- $\gamma = 1$
- $V_{dd}=800\text{mV}$
- nominal $V_{thn} = -V_{thp}=300\text{mV}$
- $C_0 = 2 \times 10^{-17}\text{F}$ (for $W = 1$ device)
- $I_{d,sat_0} = 10\mu\text{A}$ (for $W = 1$ device)
- $I_{sd,leak_0} = 0.3 \text{ pA}$ (for $W = 1$ device)
- velocity saturated operation
- $R_{wire} = 700\text{K}\Omega/\text{cm}$
- $C_{wire} = 1.7\text{pF}/\text{cm}$

Device	V_{gs}	I_{ds}
NMOS	$V_{gs} < V_{thn}$	$(1 \times 10^{-6}) W e^{\frac{V_{gs}-V_{thn}}{40\text{mV}}}$
	$V_{gs} > V_{thn}$	$2 \times 10^{-5} W (V_{gs} - V_{thn})$
PMOS	$V_{gs} > V_{thp}$	$(-1 \times 10^{-6}) W e^{-\left(\frac{V_{gs}-V_{thp}}{40\text{mV}}\right)}$
	$V_{gs} < V_{thp}$	$2 \times 10^{-5} W (V_{gs} - V_{thp})$

Timing constraints:

$$T \geq t_{clk \rightarrow q} + t_{plogic} + t_{setup} \quad (1)$$

$$t_{cdlatch} + t_{cdlogic} \geq t_{hold} \quad (2)$$

Optimal buffering:

$$L_{seg} = 2\sqrt{\frac{R_0(\gamma + 1)C_0}{R_{wire}C_{wire}}} \quad (3)$$

$$W_{buf} = \sqrt{\frac{R_0C_{wire}}{2R_{wire}C_0}} \quad (4)$$

1. (20pts) Speed and Power. Consider using CMOS nand2 gates minimum sized in the default technology. Specify units in all answers.

(a) Assume the default technology and calculate $\tau = R_0C_0$.

$$R_0 = \frac{V_{DD}}{I_{d,sat0}} = \frac{800mV}{10\mu A} = 80k\Omega$$

$$C_0 = 2 \times 10^{-17} F$$

$$\tau = R_0C_0 = 1.6ps$$

τ	1.6 ps
--------	--------

- (b) Assume the critical path in the design (including flip-flop setup time and clock-to-q delay) can be modeled as a series chain of 10 of these gates, each loaded by 4 equivalent gates. What is the maximum frequency of operation possible?

$$t_{nand2} = R_0(5\gamma + 4 \times 2)C_0 + R_0(3\gamma + 4 \times 2) = 24\tau$$

$$t_{cycle} = 10 \cdot 24\tau = 240\tau = 384ps$$

$$F_{max} = \frac{1}{t_{cycle}} = 2.6GHz$$

Max Frequency	2.6 GHz
---------------	---------

- (c) Assuming chip cooling allows a maximum dynamic power dissipation of 1W (leakage is negligible), when operating at the frequency from part (b), what is the maximum number of gates that can switch during a clock cycle, on average?

In the worst case, each nand gate switches C_{load} :

$$C_{load} = 4 \times 2C_0 + 5\gamma C_0 = 13C_0$$

$$P_{total,dyn} = \frac{1}{2} N_{gate} C_{load} V_{DD}^2 \times F_{max} \leq 1W$$

$$\frac{1}{2} \cdot N_{gate} \cdot 13 \cdot 2 \times 10^{-17} \cdot (.8)^2 \cdot 2.6 \times 10^9 \leq 1W$$

Max gate-evals/clock	4.6 M
----------------------	-------

- (d) Assuming the output of one of these gates drives a single gate input through an unbuffered wire with $R_{wire} = 700\text{K}\Omega/\text{cm}$, $C_{wire} = 1.7\text{pF}/\text{cm}$, what is the maximum distance the signal can travel in one clock cycle at the maximum clock frequency identified (part b)?

$$\begin{aligned}
 t_{cycle} &= R_0(5\gamma + C_{wire}L_{wire} + 2C_0) + R_0(3\gamma + C_{wire}L_{wire} + 2C_0) \\
 &\quad + 0.5R_{wire}C_{wire}L_{wire}^2 + R_{wire}L_{wire} \cdot 2C_0 \\
 &= R_0(12C_0 + 2C_{wire}L_{wire}) + 0.5R_{wire}C_{wire}L_{wire}^2 + R_{wire}L_{wire} \cdot 2C_0 \\
 384ps &= 19.2ps \\
 &\quad + 80 \times 10^3 \cdot 2 \cdot 1.7 \times 10^{-12} L_{wire} \\
 &\quad + 0.5 \cdot 700 \times 10^3 \cdot 1.7 \times 10^{-12} L_{wire}^2 \\
 &\quad + 700 \times 10^3 \cdot 2 \cdot 2 \times 10^{-17} L_{wire} \\
 364.8ps &= 2.72 \times 10^{-7} L_{wire} \\
 &\quad + 5.95 \times 10^{-7} L_{wire}^2 \\
 &\quad + 2.8 \times 10^{-11} L_{wire}
 \end{aligned}$$


We can clearly drop the final term since $2.8 \times 10^{-11} \ll 2.72 \times 10^{-7}$. Since L_{wire} must be less than 1 (much less than 1), the L_{wire}^2 term will be much less than the L_{wire} term. So, we can start by solving:

$$\begin{aligned}
 364.8ps &\approx 2.72 \times 10^{-7} L_{wire} \\
 L_{wire} &\approx 0.0013\text{cm} = 13\mu\text{m}
 \end{aligned}$$

Max Distance	$13\mu\text{m}$
--------------	-----------------

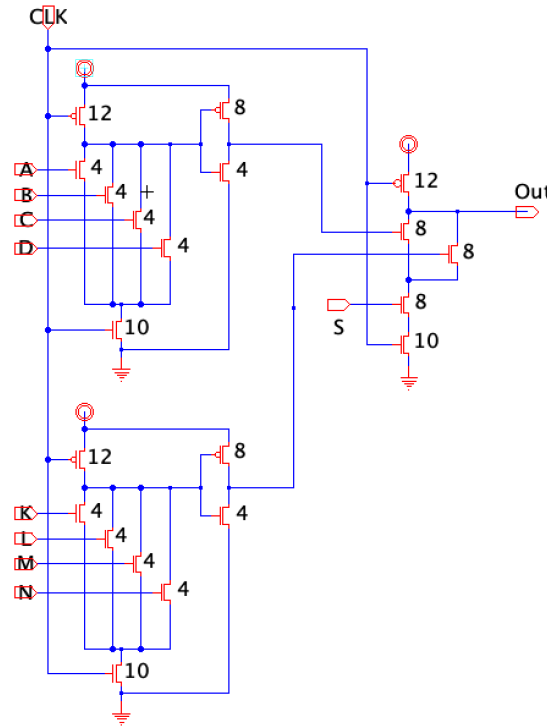
2. (20pts) Consider the following dynamic logic circuit. What logic function does it evaluate?

Assume the circuit is loaded by $7C_0$ output. Assume $C_{diff} = 0.5C_{gate}$, $\mu_n = 2\mu_p$. Assume the CLK signal is driven strongly such that the rise time on the clock is R_0C_0 . Use Elmore delay calculations where appropriate. For full credit (and partial credit consideration) show your delay components (stages, components of Elmore delay calculation).



Out as a function of the inputs?	$S \cdot (A + B + C + D + K + L + M + N)$
Evaluate Delay in units of τ (show delay components)	$\frac{\frac{10}{2} + 4 \times 4 + \frac{12}{2} + 12}{10} + \frac{2 \times 4 + \frac{12}{2} + 12}{8} + \frac{\frac{12}{2} + 8}{8}$ $\frac{12}{2} + 3 \times 8 + \frac{10}{2} + 7$ $= 24.85\tau$
Precharge Time	$\frac{\frac{12}{2} + 4 \times 4 + \frac{10}{2} + 12}{\frac{12}{2}} + \frac{2 \times 4 + \frac{10}{2}}{4} + \frac{\frac{12}{2} + 8}{4}$ $= 13.25\tau$

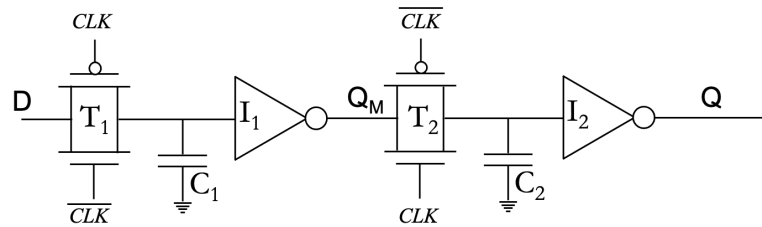3. (20pts) Below is a register built from cascading two dynamic latches. C_1 and C_2 are not explicit capacitors but just from the parasitics at each node. Assume the clocks are ideal non-overlapping clocks with a frequency of 250MHz. Each transmission gate has a delay of 100ps and each inverter has a delay of 200ps.



- (a) Is this a positive or negative edge-triggered device?

Positive


- (b) determine the register timing parameters. Include units.

i. Setup time 100ps

ii. Hold time 0 ps

iii. Worst case clock-to-q delay 500ps

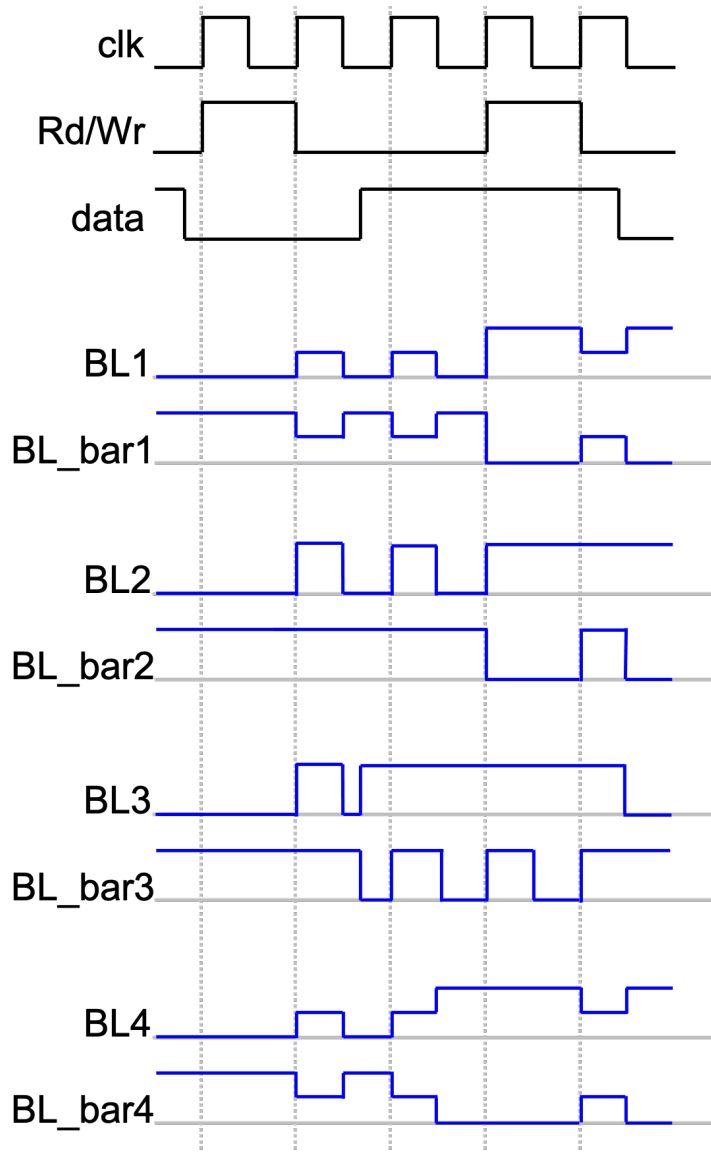4. SRAM (20 points). 4 different 6T SRAM cells are designed and tested for correct operation. There are three input test signals: clk, $\overline{\text{Rd}}/\text{Wr}$, and data. A single read or write operation occurs in a single clock period. When $\overline{\text{Rd}}/\text{Wr}$ is high a write operation should occur, and when it is low a read operation should occur. The data signal gives what data should be written into the cell when doing a write operation. Below are the test signals and BL and BL bar of all 4 cells. For each cell, indicate whether the cell is exhibiting correct operation. If not, explain what is not correct about the operation. Answer table on next page.



Bitcell 1	Correct with a precharge of $V_{dd}/2$
Bitcell 2	Correct with a precharge of V_{dd}
Bitcell 3	Not correct. There is a read upset. In the 3rd clk cycle a 1 is read instead of 0
Bitcell 4	Not correct. During the second write, BLs are not driven with complimentary data. Also in last clk cycle, reads a 0 instead of 1

5. (20pts) Short Answer Questions: Answer the questions briefly. Include diagrams and equations as needed. Be **clear** in your explanation and **handwriting**.

A Identify and describe two differences between SRAM and DRAM memory cells.

SRAM stores data in cross coupled inverter pair and is actively driven, whereas DRAM stores data dynamically on a capacitive node and must be refreshed. SRAM is larger than DRAM.

B What is a sense amplifier and why might you need it? A sense amplifier sense a small change in bitlines and amplifies it rail-to-rail. This may be needed if your bitlines are slow to charge/discharge because of a large memory size.

C What is a memory read upset and what is one way you can avoid them? A read upset is when during a read, the data in a memory cell gets flipped. One way to avoid them is to precharge to $V_{dd}/2$

D Draw a schematic of a tristate buffer and draw its truth table.

