

# ESE3700: Circuit-Level Modeling, Design, and Optimization for Digital Systems

---

Lec 13: March 24, 2025

Distributed RC Wire and Elmore Delay





# Today

---


- ❑ Estimate delay in RC Network
  - Elmore delay calculation
- ❑ Apply to wire delay
- ❑ Apply to pass transistor circuits
- ❑ Apply to CMOS gates

# Distributed RC (setup)


---




# What is response? (Preclass 1)

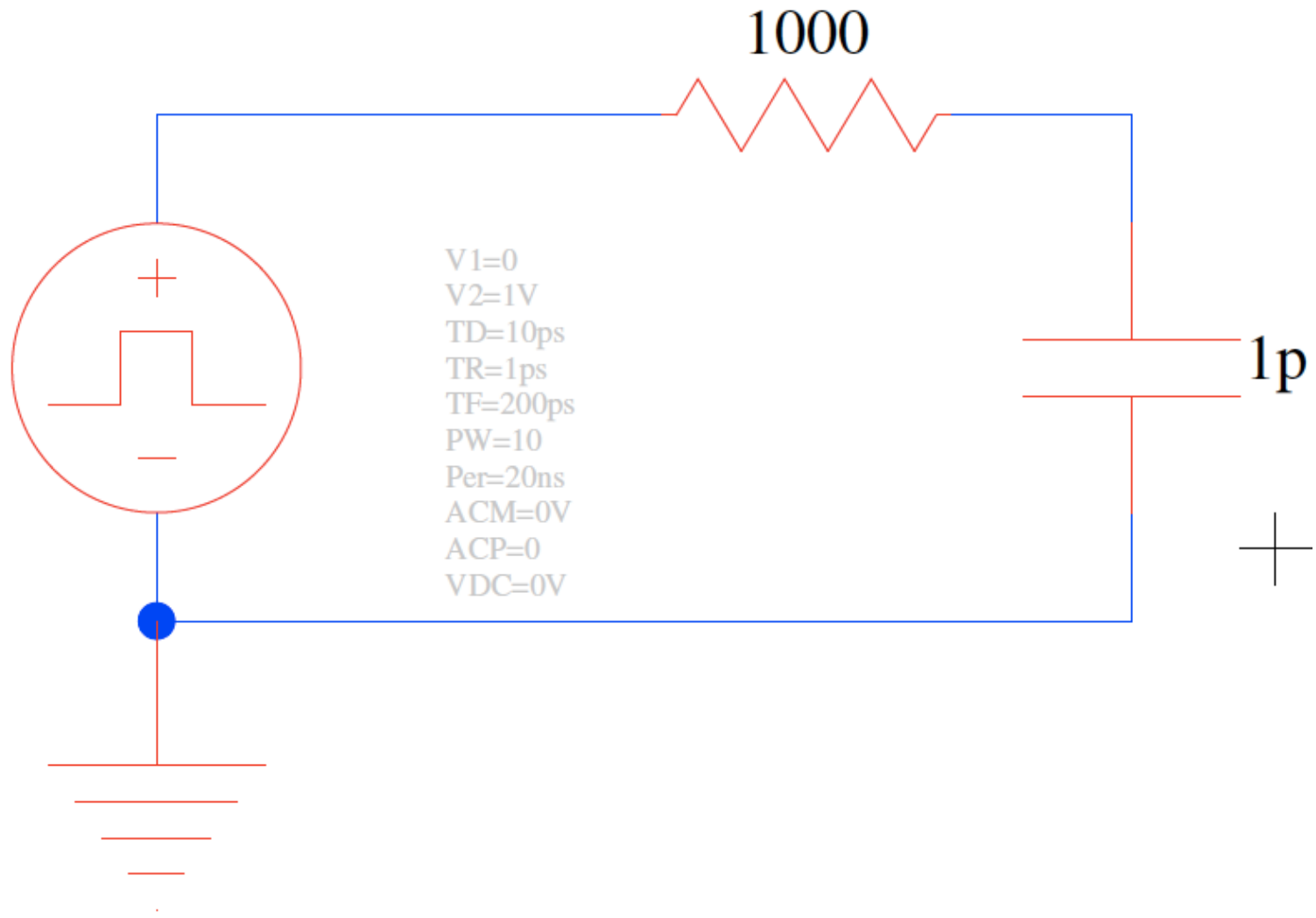

# What is response? (Preclass 1)

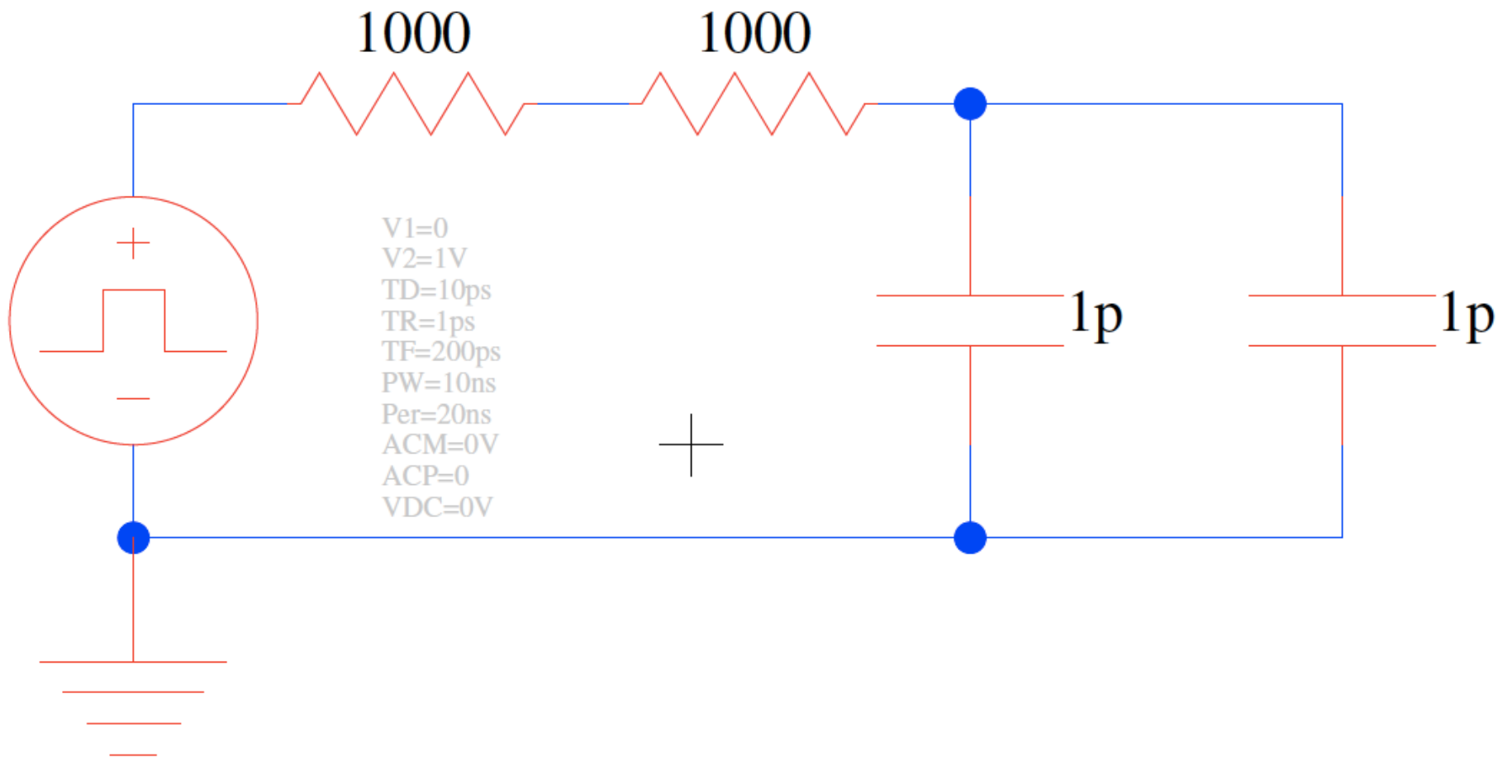


# What is response? (Preclass 1)

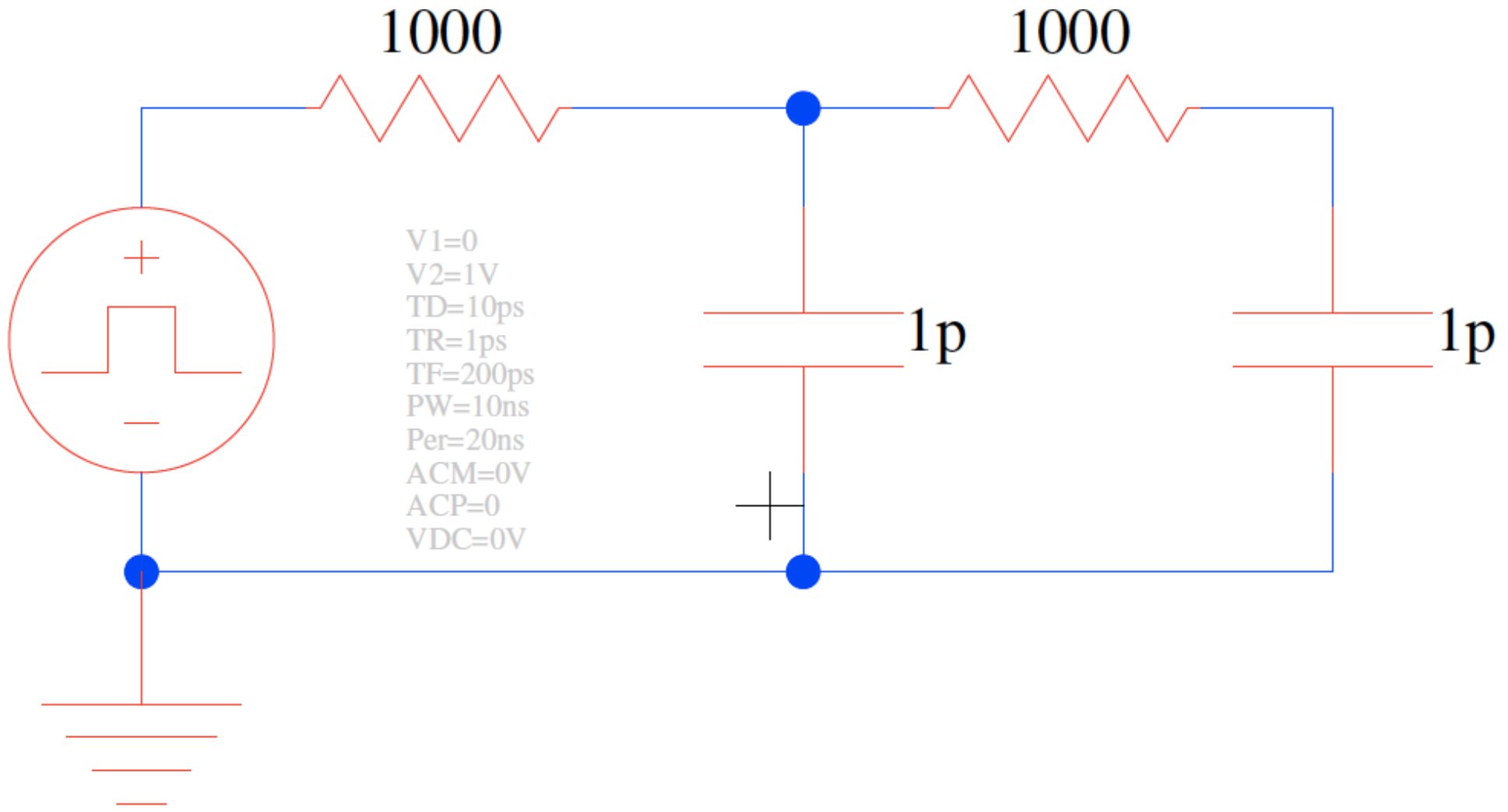




# SPICE Response

 





# SPICE Response

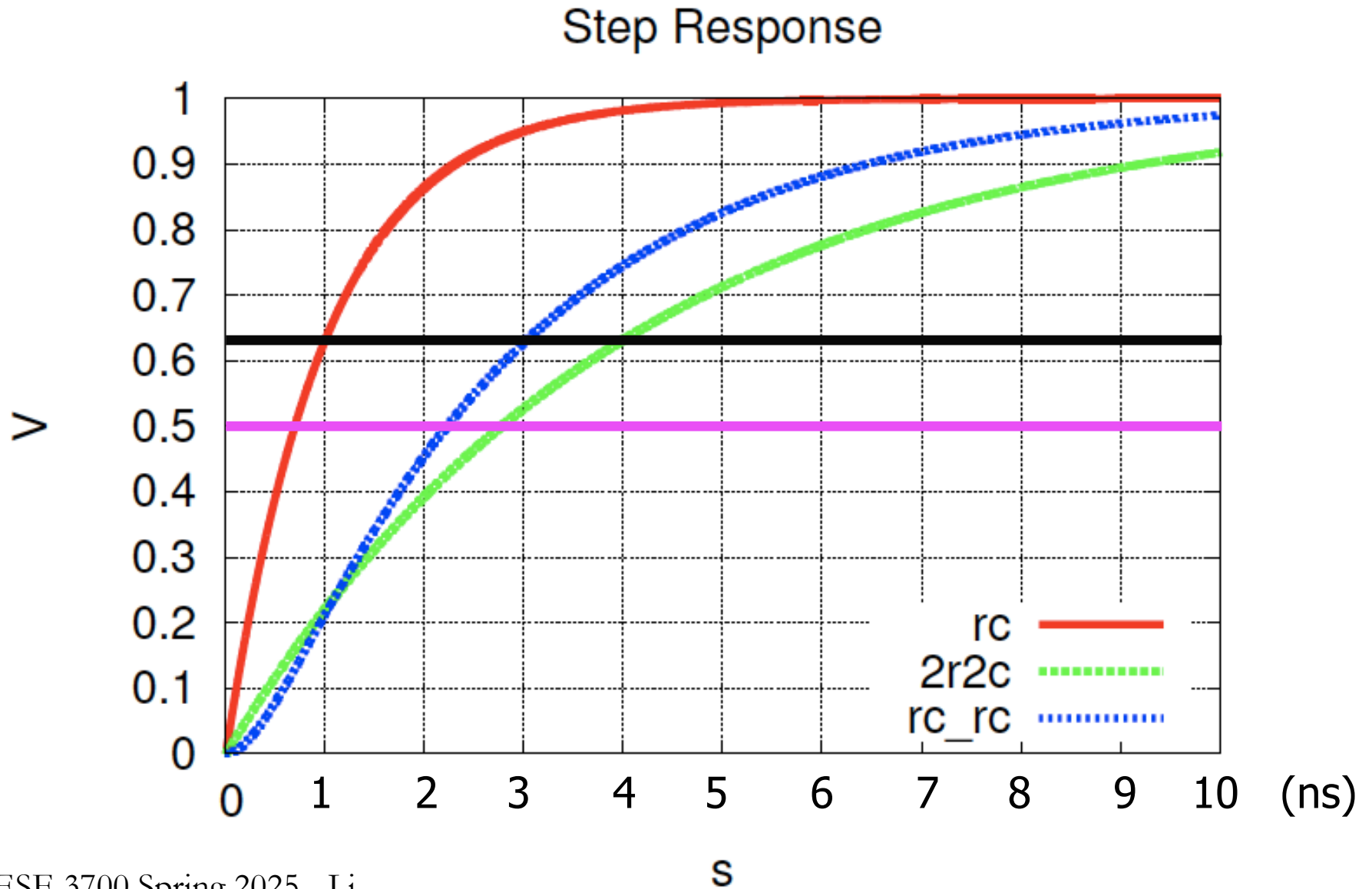



 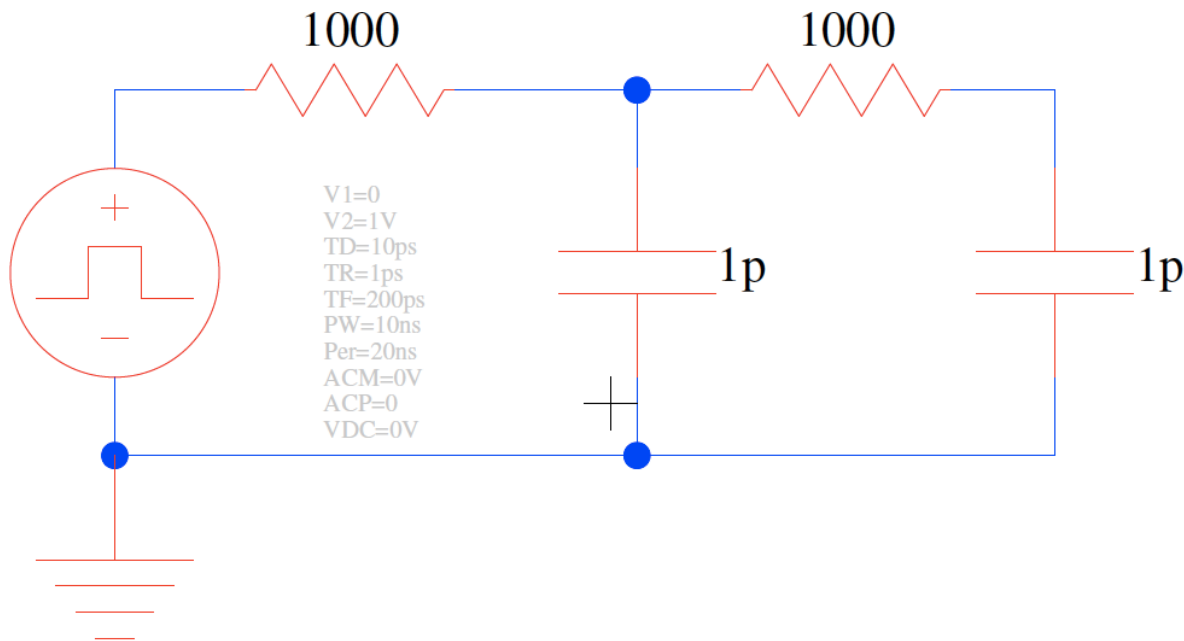
# Intuition

- Look at series of R's on path
  - Must move  $Q=V(\Sigma C)$  across each R


 
# Elmore Delay: Distributed RC network

- The delay from source  $s$  to node 5
  - $N$  = number of nodes in circuit




# Elmore Delay: Distributed RC network

- The delay from source  $s$  to node 5
  - $N$  = number of nodes in circuit

$$R_{5k} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow 5) \cap \text{path}(s \rightarrow k)])$$

$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k}$$

 


# Elmore Delay: Distributed RC network

- The delay from source  $s$  to node 5
  - $N$  = number of nodes in circuit

$$R_{5k} = \sum R_j \Rightarrow (R_j \in [path(s \rightarrow 5) \cap path(s \rightarrow k)])$$

$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k}$$

 


# Elmore Delay: Distributed RC network

□ The delay from source  $s$  to node 5

■  $N$  = number of nodes in circuit

$$R_{5k} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow 5) \cap \text{path}(s \rightarrow k)])$$

$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k}$$

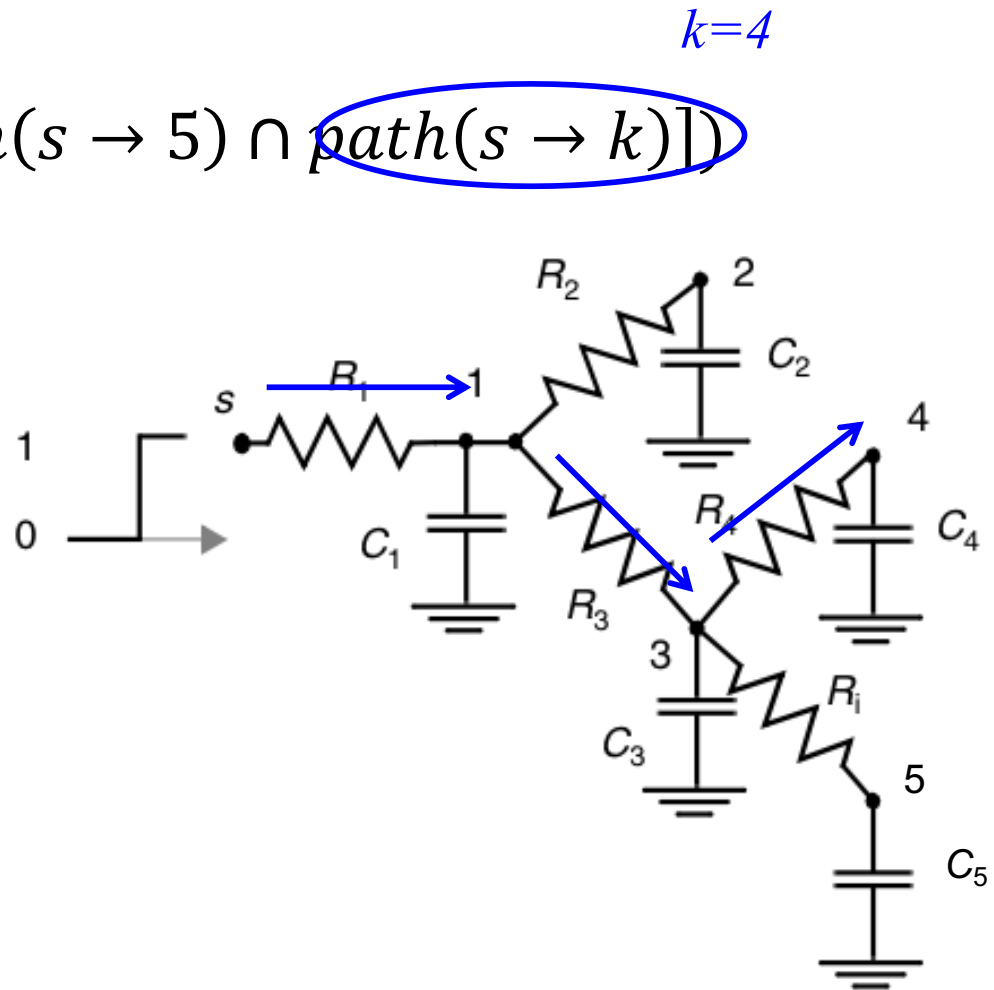


# Elmore Delay: Distributed RC network

□ The delay from source  $s$  to node 5

■  $N$  = number of nodes in circuit

$$R_{5k} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow 5) \cap \text{path}(s \rightarrow k)])$$

$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k}$$

 


# Elmore Delay: Distributed RC network

□ The delay from source  $s$  to node 5

■  $N$  = number of nodes in circuit

$$R_{5k} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow 5) \cap \text{path}(s \rightarrow k)])$$

$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k}$$

 


# Elmore Delay: Distributed RC network

- The delay from source  $s$  to node 5
  - $N$  = number of nodes in circuit

$$R_{5k} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow 5) \cap \text{path}(s \rightarrow k)])$$
 
$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k} = ?$$






# Elmore Delay: Distributed RC network

- The delay from source  $s$  to node 5
  - $N$  = number of nodes in circuit

$$R_{5k} = \sum R_j \Rightarrow (R_j \in [path(s \rightarrow 5) \cap path(s \rightarrow k)])$$
 
$$\tau_{D5} = \sum_{k=1}^N C_k R_{5k} = ?$$




# Elmore Delay: Practice



- The delay from source  $s$  to node  $O$ 
  - $N$  = number of nodes in circuit

$$R_{Ok} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow O) \cap \text{path}(s \rightarrow k)])$$


 
$$\tau_{DO} = \sum_{k=1}^N C_k R_{Ok} = ?$$



# Previously: Equivalent RC

 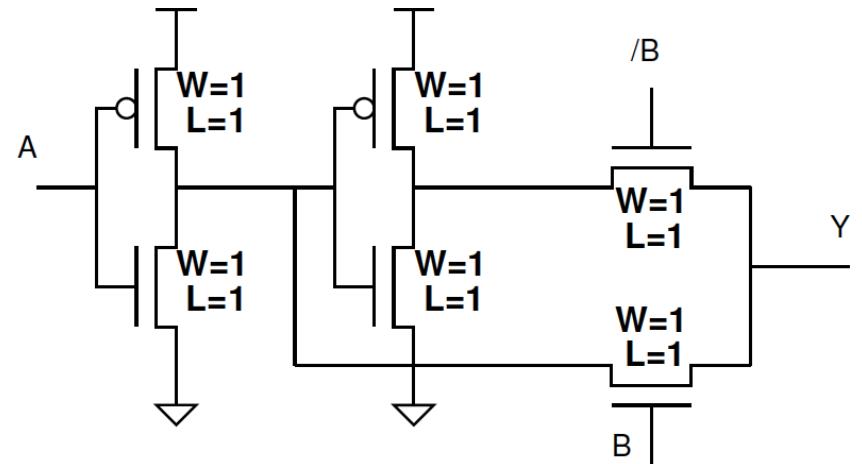

# What is response?

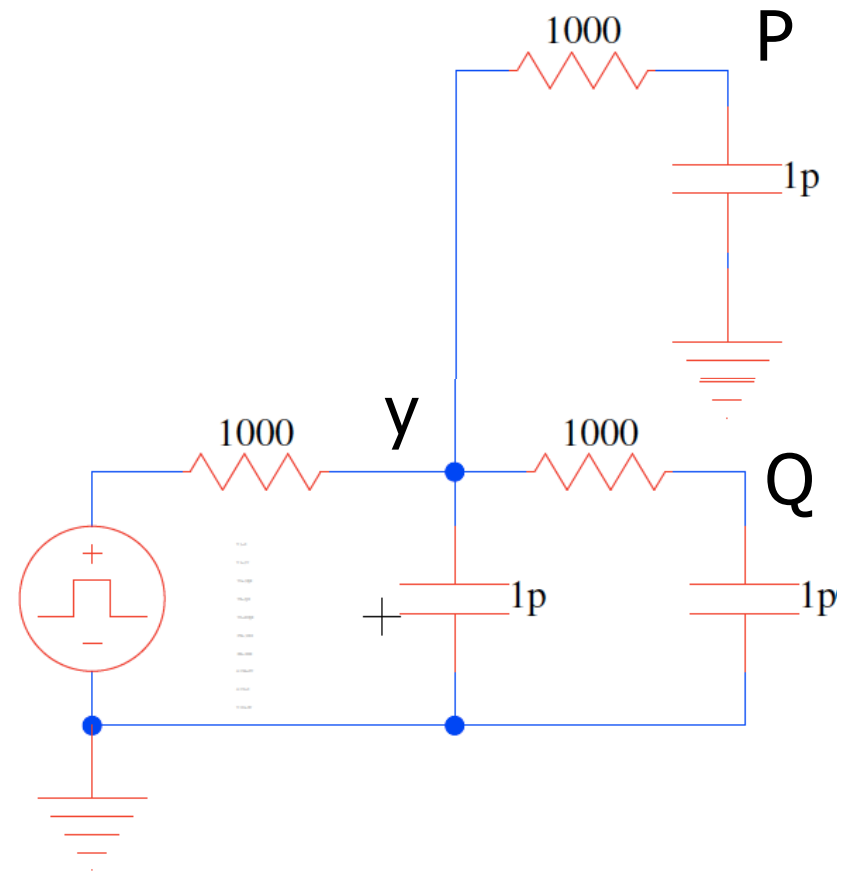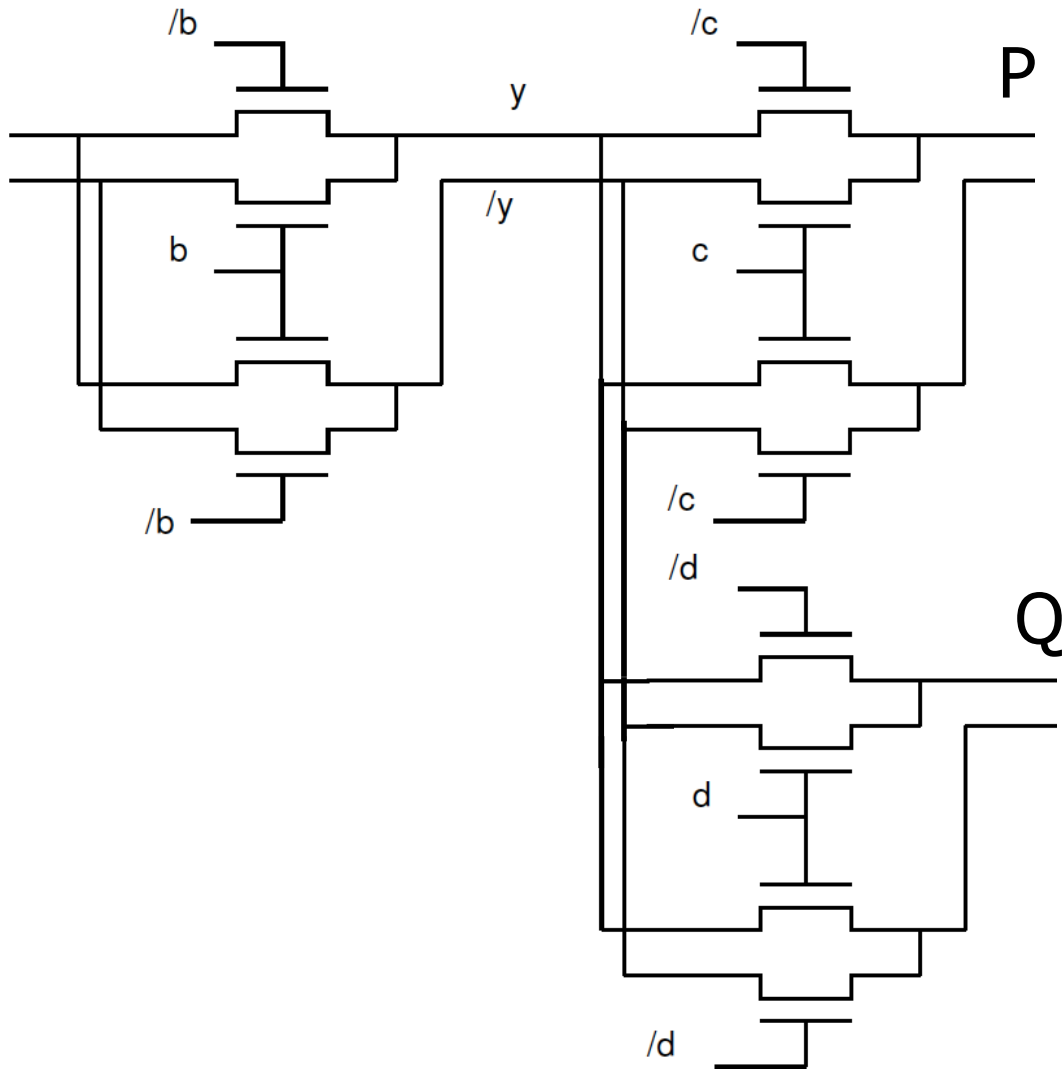


# Elmore Delay: Practice (preclass 1)

- The delay from source  $s$  to node  $i$ 
  - $N$  = number of nodes in circuit


$$R_{ik} = \sum R_j \Rightarrow (R_j \in [path(s \rightarrow i) \cap path(s \rightarrow k)])$$

$$\tau_{Di} = \sum_{k=1}^N C_k R_{ik}$$

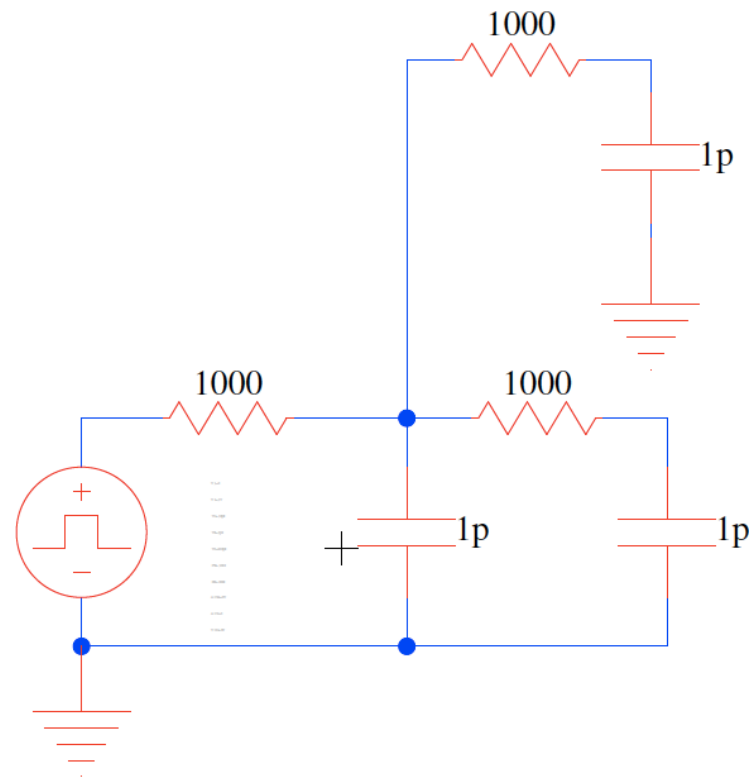


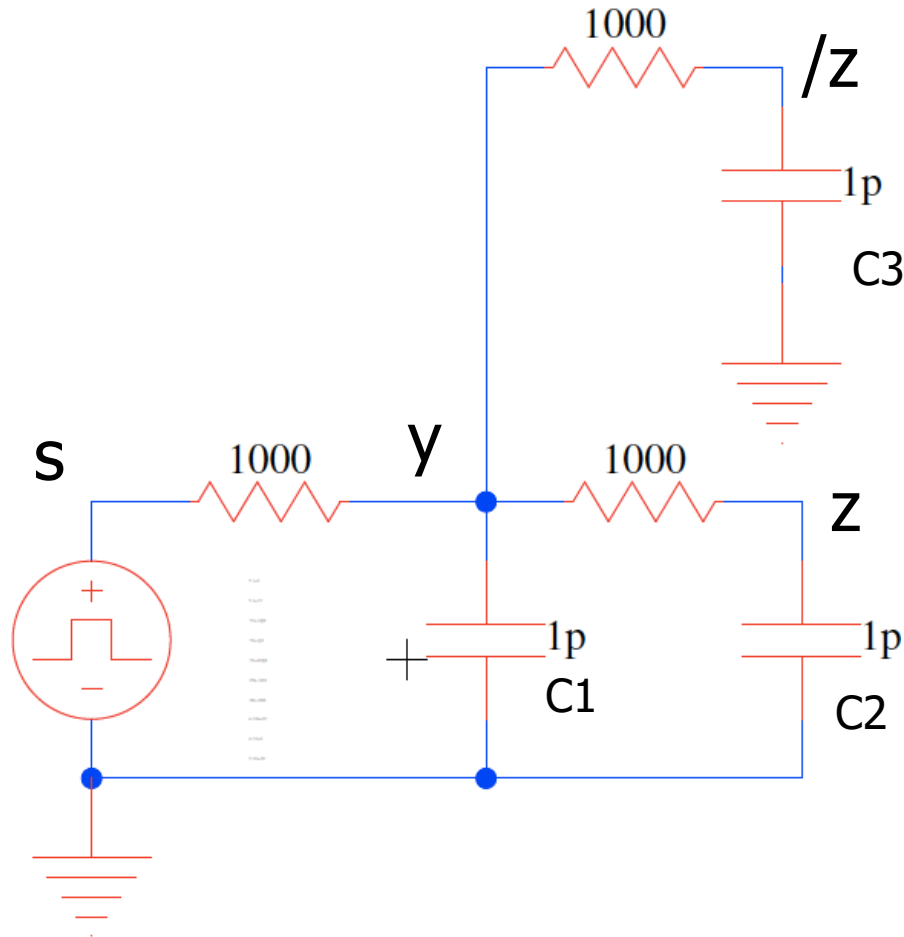
# Apply (preclass 1)

- What is Elmore delay?
  - $S \rightarrow Z$



# SPICE Response


## Step Response

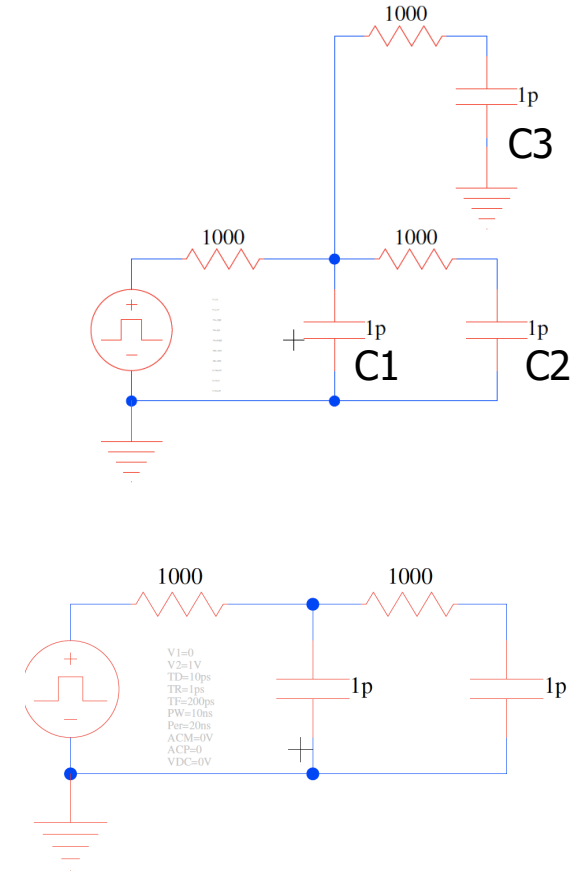 
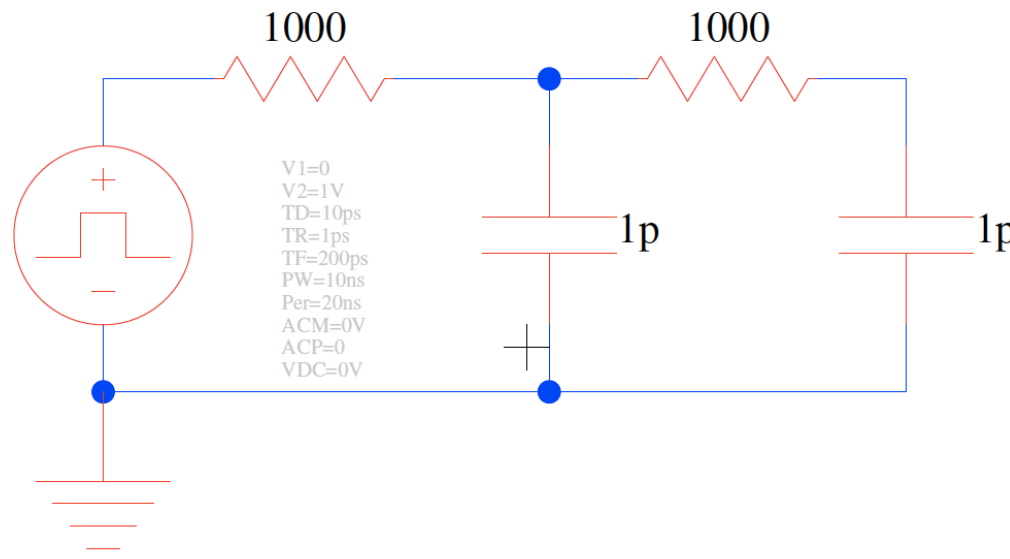
# Elmore Delay: Special Ladder Case

- For each resistor  $C_k$  in path
  - Compute  $R_{kk} =$  sum of all  $R$ s upstream of  $C_k$

$$\tau_{DN} = \sum_{k=1}^N C_k \sum_{j=1}^k R_j = \sum_{k=1}^N C_k R_{kk}$$






# Elmore Delay: Special Ladder Case

- For each resistor  $C_k$  in path
  - Compute  $R_{kk} =$  sum of all  $R$ s upstream of  $C_k$

$$\tau_{DN} = \sum_{k=1}^N C_k \sum_{j=1}^k R_j = \sum_{k=1}^N C_k R_{kk}$$

$$C_1 * (R_1) + C_2 * (R_1 + R_2)$$

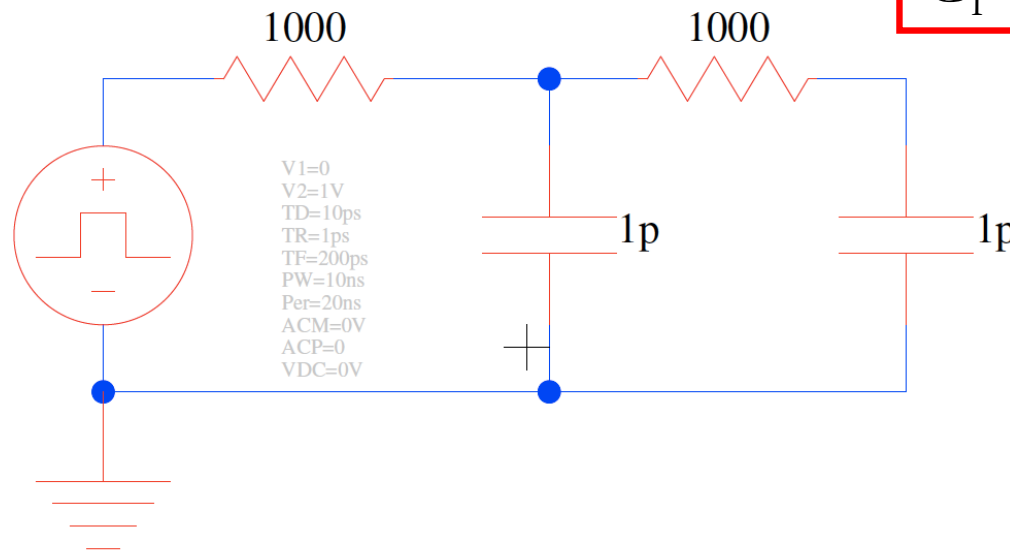


# Elmore Delay: Special Ladder Case

- For each resistor  $C_k$  in path
  - Compute  $R_{kk} = \text{sum of all } R\text{s upstream of } C_k$

$$\tau_{DN} = \sum_{k=1}^N C_k \sum_{j=1}^k R_j = \sum_{k=1}^N C_k R_{kk}$$

$$C_1 * (R_1) + C_2 * (R_1 + R_2)$$

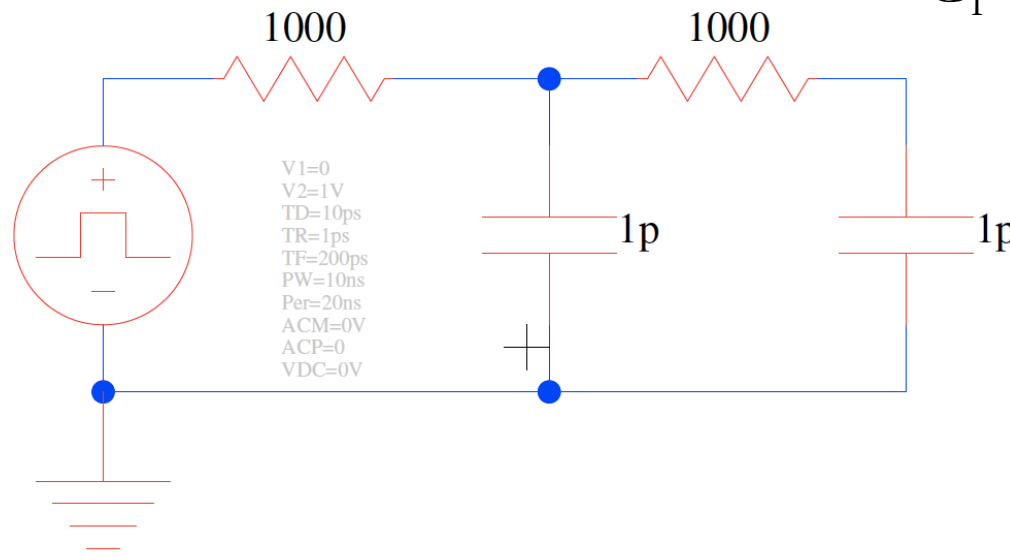

$$=3RC$$


$$=3ns$$

# Compare KCL: Setup
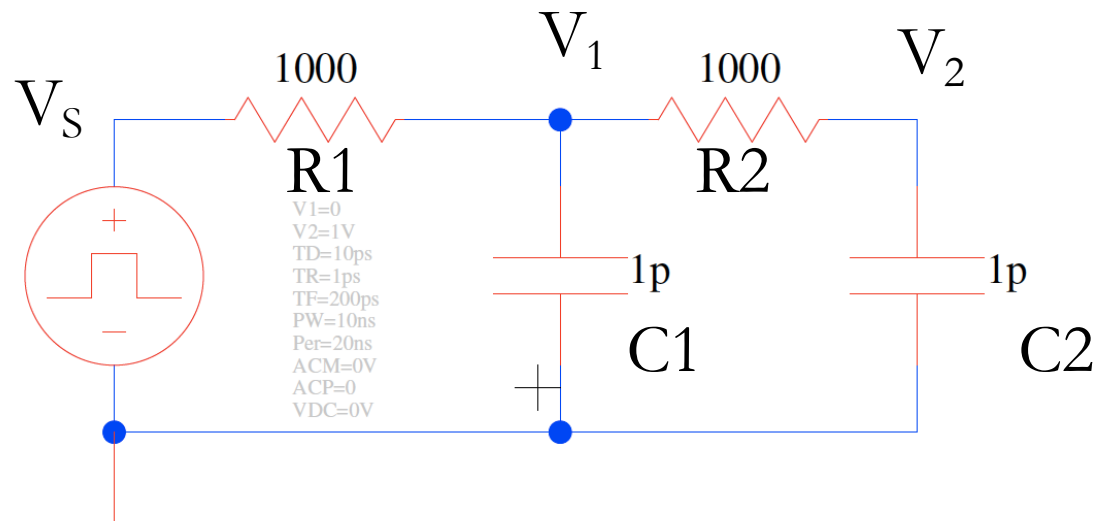
## □ Equations from KCL?

$$\text{@}V_1: \frac{V_S - V_1}{R_1} = \frac{V_1 - V_2}{R_2} + C_1 \frac{dV_1}{dt}$$

$$\text{@}V_2: \frac{V_1 - V_2}{R_2} = C_2 \frac{dV_2}{dt}$$



# Compare KCL: Math

@ $V_1$ :

$$\frac{V_S - V_1}{R_1} = \frac{V_1 - V_2}{R_2} + C_1 \frac{dV_1}{dt}$$

$$\frac{V_S}{R_1} = \frac{V_1}{R_1} + \frac{V_1}{R_2} - \frac{V_2}{R_2} + C_1 \frac{dV_1}{dt}$$

$$V_S = V_1 \left( 1 + \frac{R_1}{R_2} \right) - \frac{R_1 V_2}{R_2} + R_1 C_1 \frac{dV_1}{dt}$$

@ $V_2$ :

$$\frac{V_1 - V_2}{R_2} = C_2 \frac{dV_2}{dt}$$

$$\frac{V_1}{R_2} = \frac{V_2}{R_2} + C_2 \frac{dV_2}{dt}$$

$$V_1 = V_2 + R_2 C_2 \frac{dV_2}{dt}$$

$$\frac{dV_1}{dt} = \frac{dV_2}{dt} + R_2 C_2 \frac{d^2 V_2}{dt^2}$$

# Compare KCL: Math

$$V_S = V_1 \left( 1 + \frac{R_1}{R_2} \right) - \frac{R_1}{R_2} V_2 + R_1 C_1 \frac{dV_1}{dt}$$

$$V_S = \left( V_2 + R_2 C_2 \frac{dV_2}{dt} \right) \left( 1 + \frac{R_1}{R_2} \right) - \frac{R_1}{R_2} V_2 + R_1 C_1 \left( \frac{dV_2}{dt} + R_2 C_2 \frac{d^2 V_2}{dt^2} \right)$$

$$V_S = V_2 + \left( R_2 C_2 \left( 1 + \frac{R_1}{R_2} \right) + R_1 C_1 \right) \frac{dV_2}{dt} + R_1 C_1 R_2 C_2 \frac{d^2 V_2}{dt^2}$$

$$V_S = V_2 + (R_2 C_2 + R_1 C_2 + R_1 C_1) \frac{dV_2}{dt} + R_1 C_1 R_2 C_2 \frac{d^2 V_2}{dt^2}$$



# Compare KCL: Math

---

$$R_1 = R_2 = R$$

$$C_1 = C_2 = C$$

$$V_S = V_2 + (R_2 C_2 + R_1 C_2 + R_1 C_1) \frac{dV_2}{dt} + R_1 C_1 R_2 C_2 \frac{d^2 V_2}{dt^2}$$

$$V_S = V_2 + 3RC \frac{dV_2}{dt} + R^2 C^2 \frac{d^2 V_2}{dt^2}$$



# Compare KCL: Math

---

$$R_1 = R_2 = R$$

$$C_1 = C_2 = C$$

$$V_S = V_2 + (R_2 C_2 + R_1 C_2 + R_1 C_1) \frac{dV_2}{dt} + R_1 C_1 R_2 C_2 \frac{d^2 V_2}{dt^2}$$

$$V_S = V_2 + 3RC \frac{dV_2}{dt} + R^2 C^2 \frac{d^2 V_2}{dt^2}$$

$$V_2 = A(1 + e^{-\alpha t}) \rightarrow$$

$$V_S = A(1 + e^{-\alpha t}) - 3RC \cdot \alpha A e^{-\alpha t} + R^2 C^2 \cdot \alpha^2 A e^{-\alpha t}$$



# Compare KCL: Math

---

$$V_2 = A(1 + e^{-\alpha t}) \rightarrow$$

$$V_S = A(1 + e^{-\alpha t}) - 3RC \cdot \alpha A e^{-\alpha t} + R^2 C^2 \cdot \alpha^2 A e^{-\alpha t}$$

$$t = \infty \rightarrow V_2 = V_S = A$$





# Compare KCL: Math

---

$$V_2 = A(1 + e^{-\alpha t}) \rightarrow$$

$$V_S = A(1 + e^{-\alpha t}) - 3RC \cdot \alpha A e^{-\alpha t} + R^2 C^2 \cdot \alpha^2 A e^{-\alpha t}$$

$$t = \infty \rightarrow V_2 = V_S = A$$

$$V_S = V_S(1 + e^{-\alpha t}) - 3RC \cdot \alpha V_S e^{-\alpha t} + R^2 C^2 \cdot \alpha^2 V_S e^{-\alpha t}$$

$$0 = e^{-\alpha t} - 3RC \cdot \alpha e^{-\alpha t} + R^2 C^2 \cdot \alpha^2 e^{-\alpha t}$$

$$0 = e^{-\alpha t} (1 - 3RC\alpha + R^2 C^2 \cdot \alpha^2)$$

$$0 = 1 - 3RC\alpha + R^2 C^2 \cdot \alpha^2$$


# Compare KCL: Math

$$V_2 = V_S(1 + e^{-\alpha t})$$

$$0 = 1 - 3RC\alpha + R^2C^2 \cdot \alpha^2$$

$$\alpha = \frac{3RC \pm \sqrt{9(RC)^2 - 4(RC)^2}}{2(RC)^2} = \frac{3RC \pm \sqrt{5}RC}{2(RC)^2} = \frac{3 \pm \sqrt{5}}{2RC}$$
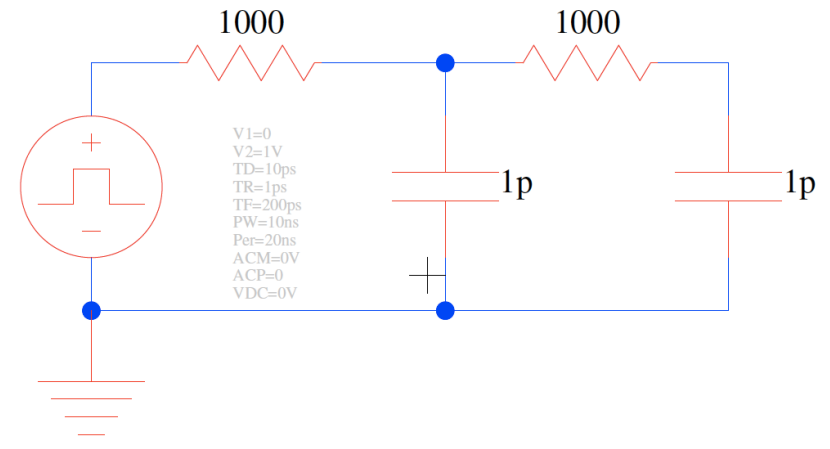
$$\rightarrow \tau = \frac{2}{3 \pm \sqrt{5}} RC \approx 2.6RC$$




# Compare KCL: Math

$$V_2 = V_S(1 + e^{-\alpha t})$$

$$0 = 1 - 3RC\alpha + R^2C^2 \cdot \alpha^2$$

$$\alpha = \frac{3RC \pm \sqrt{9(RC)^2 - 4(RC)^2}}{2(RC)^2} = \frac{3RC \pm \sqrt{5}RC}{2(RC)^2} = \frac{3 \pm \sqrt{5}}{2RC}$$
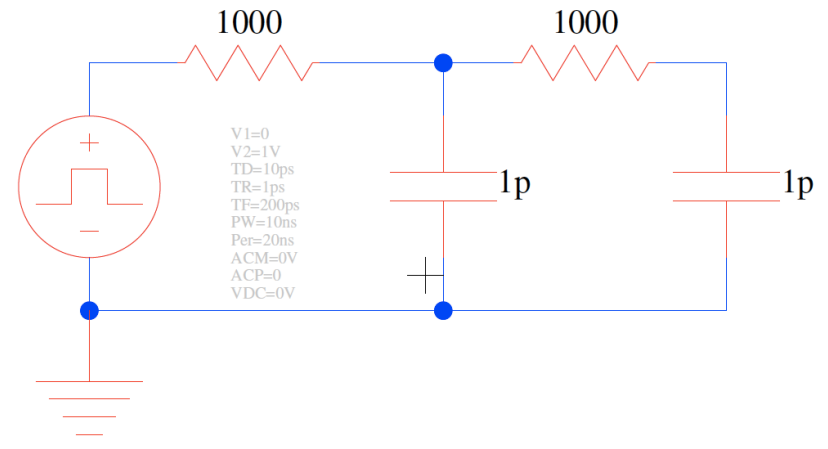
$$\rightarrow \tau = \frac{2}{3 \pm \sqrt{5}} RC \approx 2.6RC$$



$$\begin{aligned} &= 3RC \\ &= 3\text{ns} \end{aligned}$$

# Elmore Delay: Distributed RC network

- The delay from source to node  $i$ 
  - $N$  = number of nodes in circuit

$$R_{ik} = \sum R_j \Rightarrow (R_j \in [\text{path}(s \rightarrow i) \cap \text{path}(s \rightarrow k)])$$

$$\tau_{Di} = \sum_{k=1}^N C_k R_{ik}$$

- Special ladder case


$$\tau_{DN} = \sum_{k=1}^N C_k \sum_{j=1}^k R_j = \sum_{k=1}^N C_k R_{kk}$$

# Wire Delay

---



# Wire Resistance

 


$$R = \frac{\rho L}{A}$$

$$R = \frac{10^{-7} \Omega \cdot m \cdot 100 \mu m}{1 \mu m \cdot 1 \mu m} = 10 \Omega$$


# Wire Capacitance

$$C = \epsilon_d \frac{A}{d}$$

 
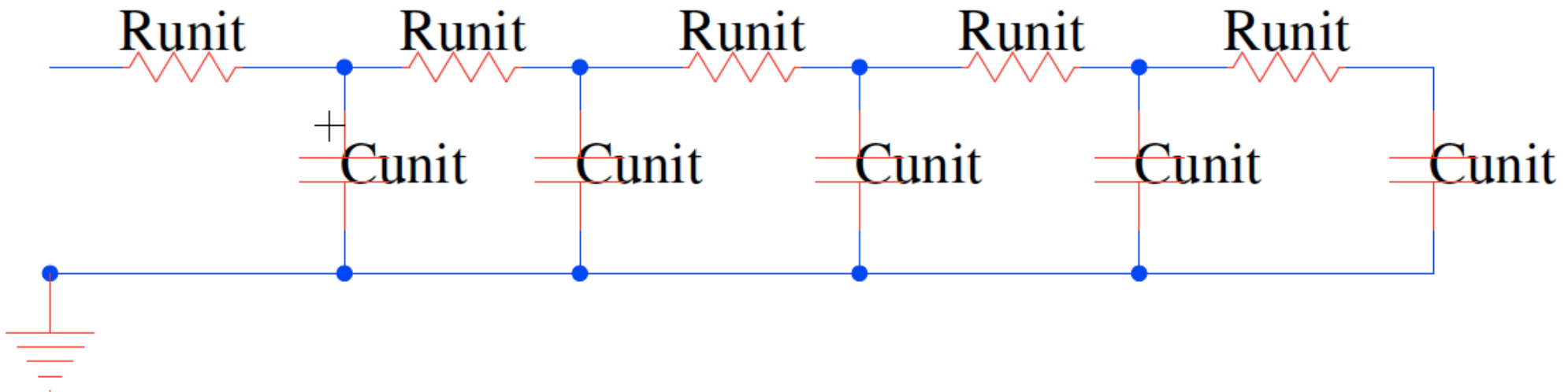
# Wire as Distributed RC Ladder

- Measure wire length in units
  - Say  $\lambda$
  - Each  $\lambda$  unit has  $C_{\text{unit}}$ ,  $R_{\text{unit}}$ 
    - Unit capacitance and resistance of wire of length  $\lambda$








# Wire Delay

- Delay of Wire  $N$  units long:

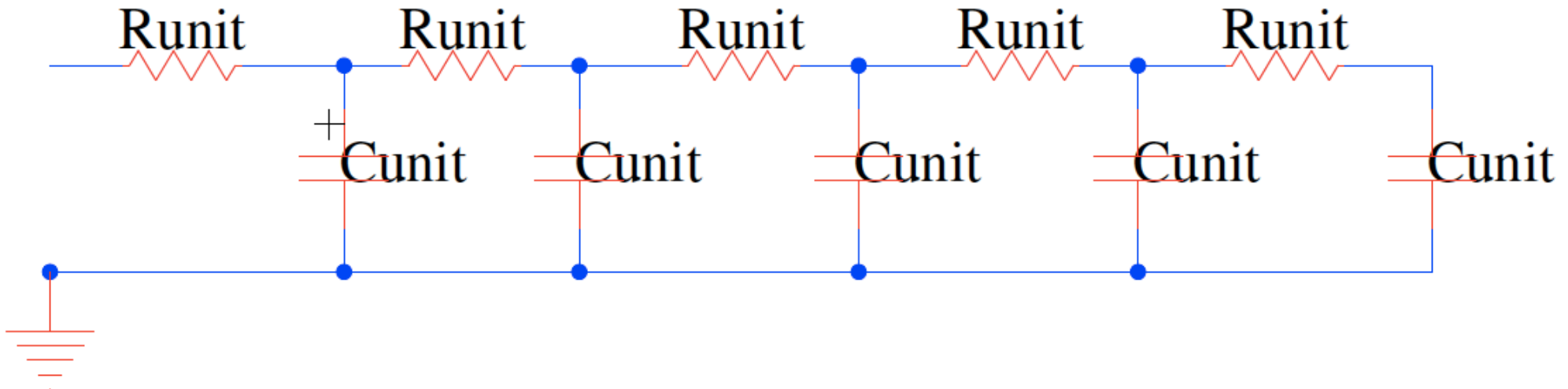




# Wire Delay

□ Delay of Wire N units long:


$$R_{\text{unit}}C_{\text{unit}}$$

 
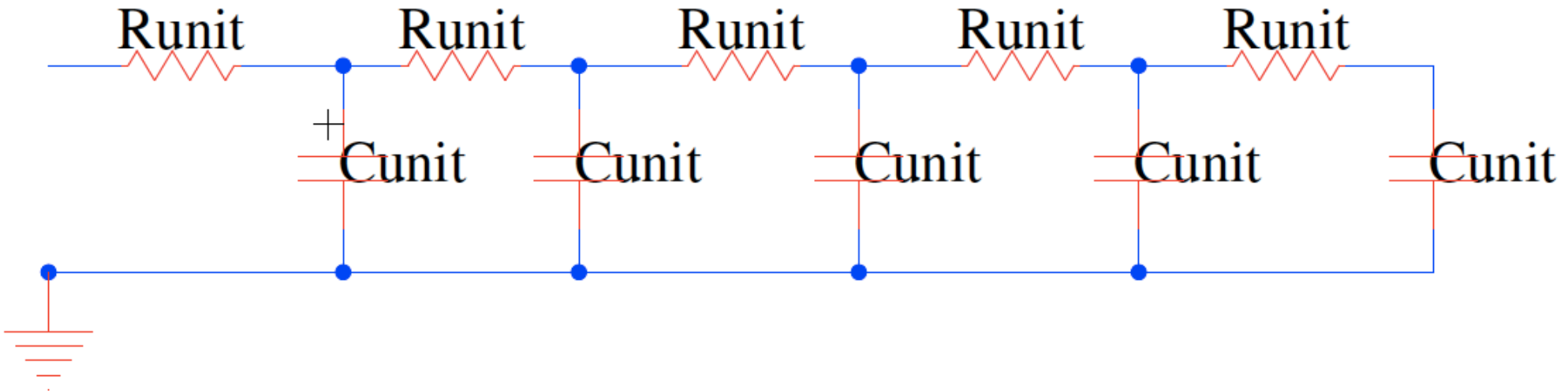
# Wire Delay

□ Delay of Wire N units long:


$$R_{\text{unit}}C_{\text{unit}} + 2R_{\text{unit}}C_{\text{unit}}$$


 
# Wire Delay

□ Delay of Wire N units long:

$$\begin{aligned} & R_{\text{unit}}C_{\text{unit}} \\ & + 2R_{\text{unit}}C_{\text{unit}} \\ & + 3R_{\text{unit}}*C_{\text{unit}} + \dots + NR_{\text{unit}}*C_{\text{unit}} \\ & = (R_{\text{unit}}*C_{\text{unit}})*(N+(N-1)+(N-2)+\dots+1) \end{aligned}$$






# Sum of integers (preclass 2)

---

- What's the sum of the integer 1 to N?

$$\sum_{k=0}^N k =$$



# Sum of integers

---


- What's the sum of the integer 1 to N?

$$\sum_{k=0}^N k = \frac{N(N+1)}{2} \approx \frac{N^2}{2}$$
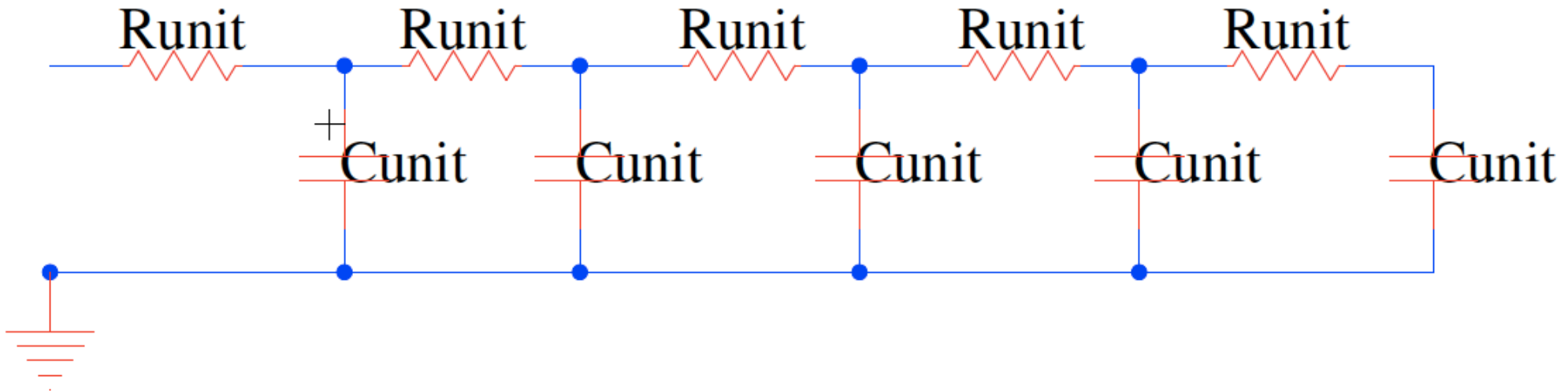
# Wire Delay (preclass 3)

□ Delay of Wire N units long:

$$\begin{aligned} & R_{\text{unit}} * (N * C_{\text{unit}}) \\ & + R_{\text{unit}} * ((N-1) * C_{\text{unit}}) \\ & + R_{\text{unit}} * (N-2) * C_{\text{unit}} + \dots + R_{\text{unit}} * C_{\text{unit}} \\ & = (R_{\text{unit}} * C_{\text{unit}}) * (N + N-1 + N-2 + \dots + 1) \\ & \sim R_{\text{unit}} C_{\text{unit}} * N^2 / 2 \end{aligned}$$




# Lumped RC Wire? (preclass 4)

- What would the delay be if we treated the wire as lumped R and C?

$$R_{\text{wire}} = N \times R_{\text{unit}}$$
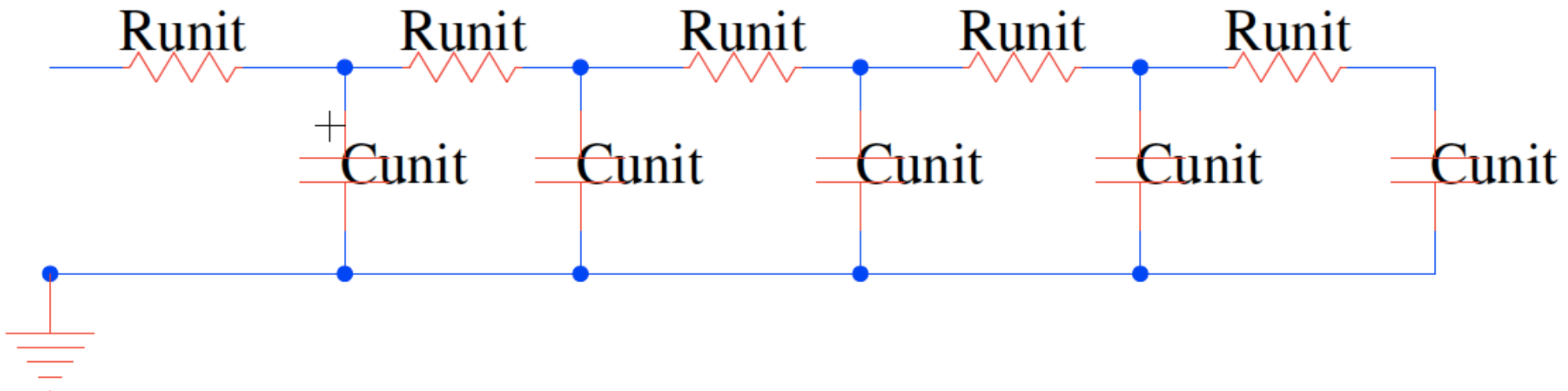
$$C_{\text{wire}} = N \times C_{\text{unit}}$$







# Wire Delay

---

- ❑  $R_{\text{wire}} = N * R_{\text{unit}}$
- ❑  $C_{\text{wire}} = N * C_{\text{unit}}$
- ❑ Lumped RC wire delay =  $R_{\text{unit}} * C_{\text{unit}} * N^2$
- ❑ Distributed RC Wire delay =  $R_{\text{unit}} * C_{\text{unit}} * N^2 / 2$
  
- ❑ Distributed has half the delay of lumped RC product
- ❑ Delay is quadratic in length of wire in both cases

# Apply to Gates



---

Pass Transistor and CMOS




# Pass Transistor XOR

□ Delay when  $A=B=1$ ?

 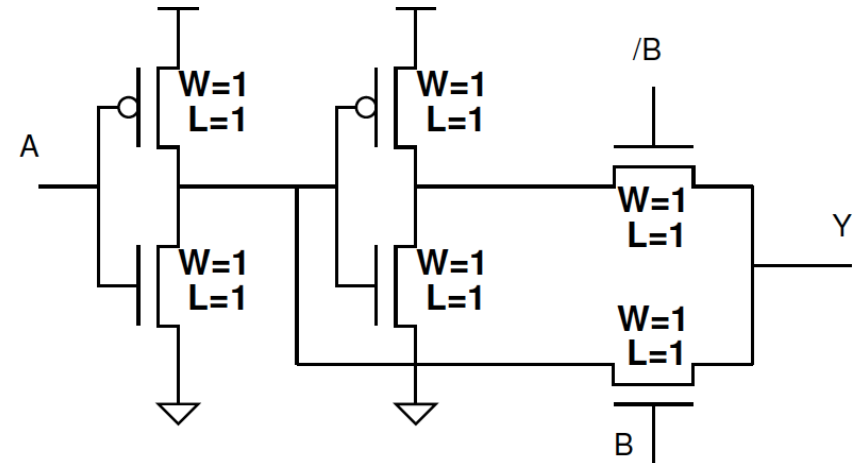
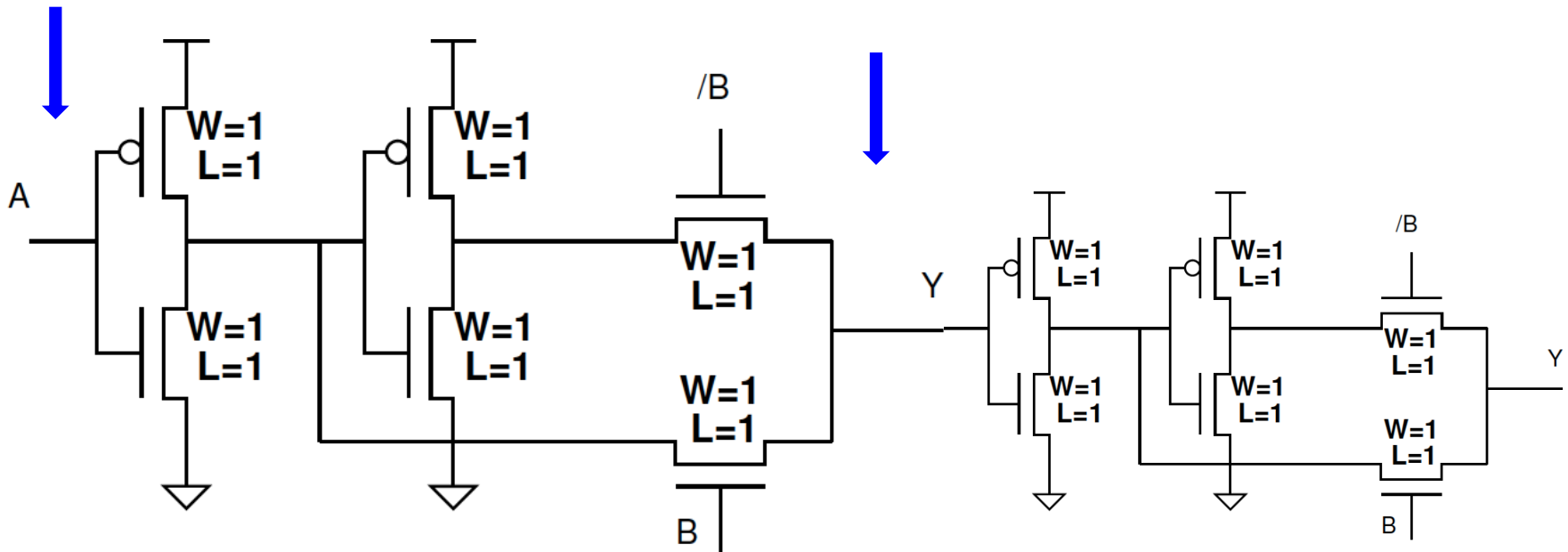
# Pass Transistor XOR (preclass 5)


- Delay when  $A=1, B=0$ ?
  - Start with equivalent RC circuit



# Unbuffered (preclass 6)

□ Circuit → Delay?


■ 2 stages

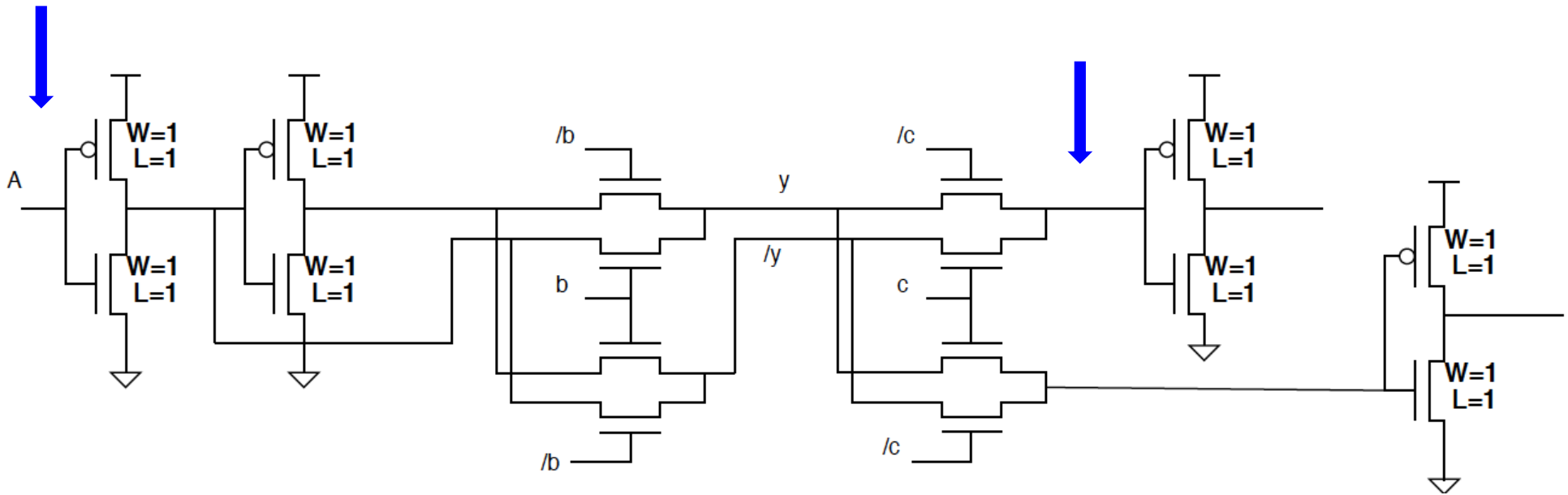

# Unbuffered (preclass 7)


□ Circuit → Delay?

■ 3 stages

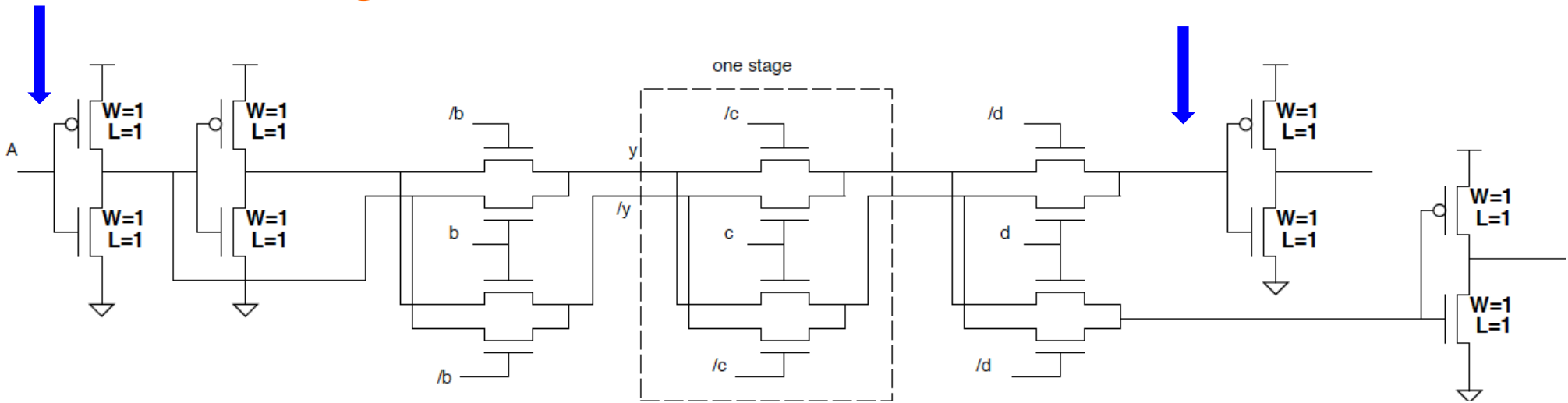

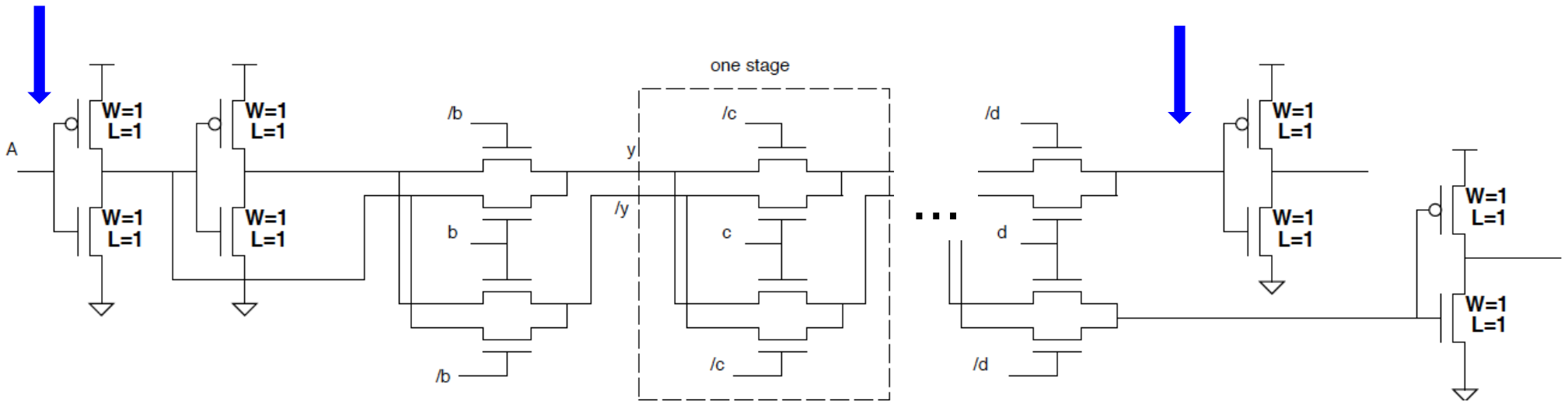
# Unbuffered (preclass 8)

□ Delay as a function of number of stages,  $k$ ?





# CMOS XOR (preclass 9)

- Delay with  $C_{diff} > 0$ ?

 





# Review: Two-Input NOR Gate (NOR2)

 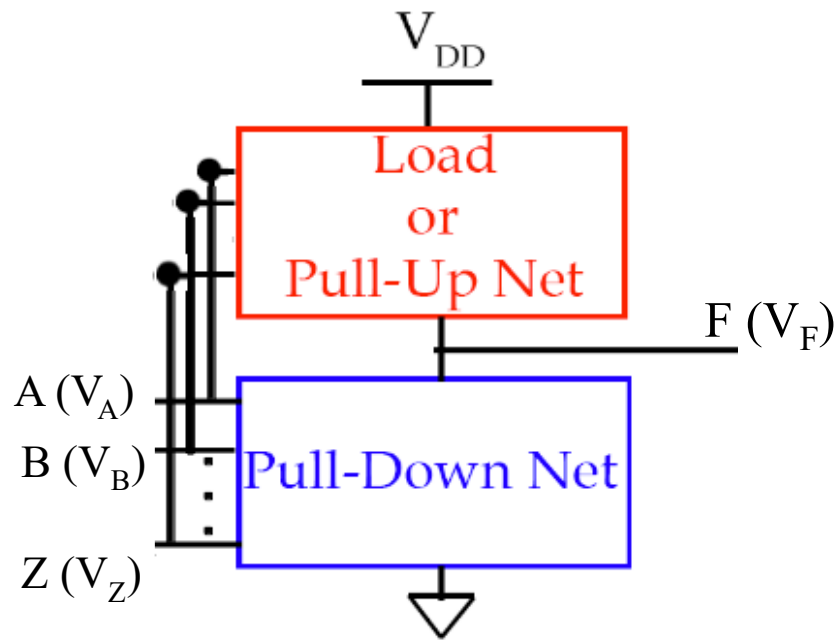

- ❑ Worst case delay of NOR2?
  - Minimum size, Loaded with itself

# NOR2 Transfer Curve

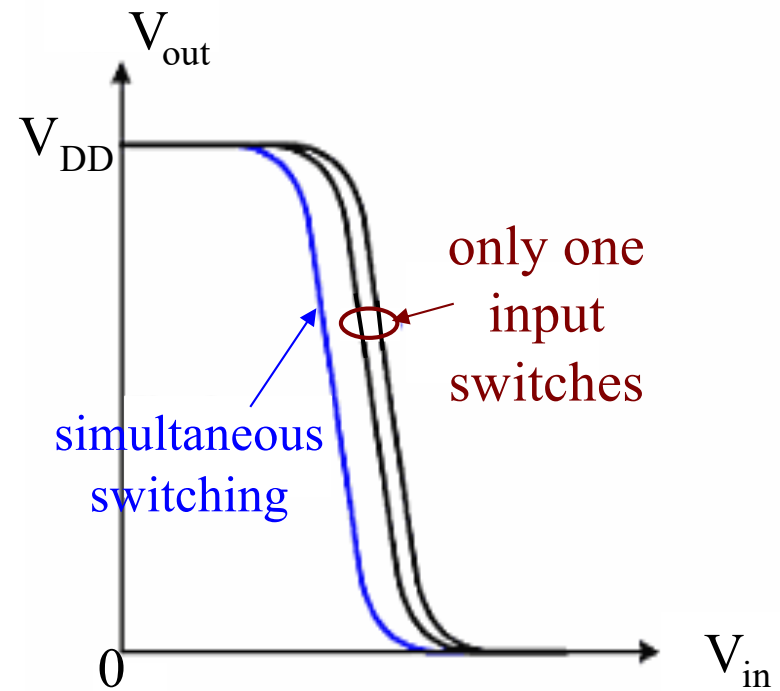 

## 3 VTC Cases

$$V_1 = 0 \text{ V}; V_2 = 0 \rightarrow V_{DD}$$

$$V_1 = 0 \rightarrow V_{DD}; V_2 = 0$$


$$V_1 \text{ and } V_2 = 0 \rightarrow V_{DD} \text{ simultaneously}$$

Switching Threshold Voltage:

$$V_1 = V_2 = V_{out} = V_t$$


# NOR2 Delay (preclass 10)

- Worst case delay for Pull-up?

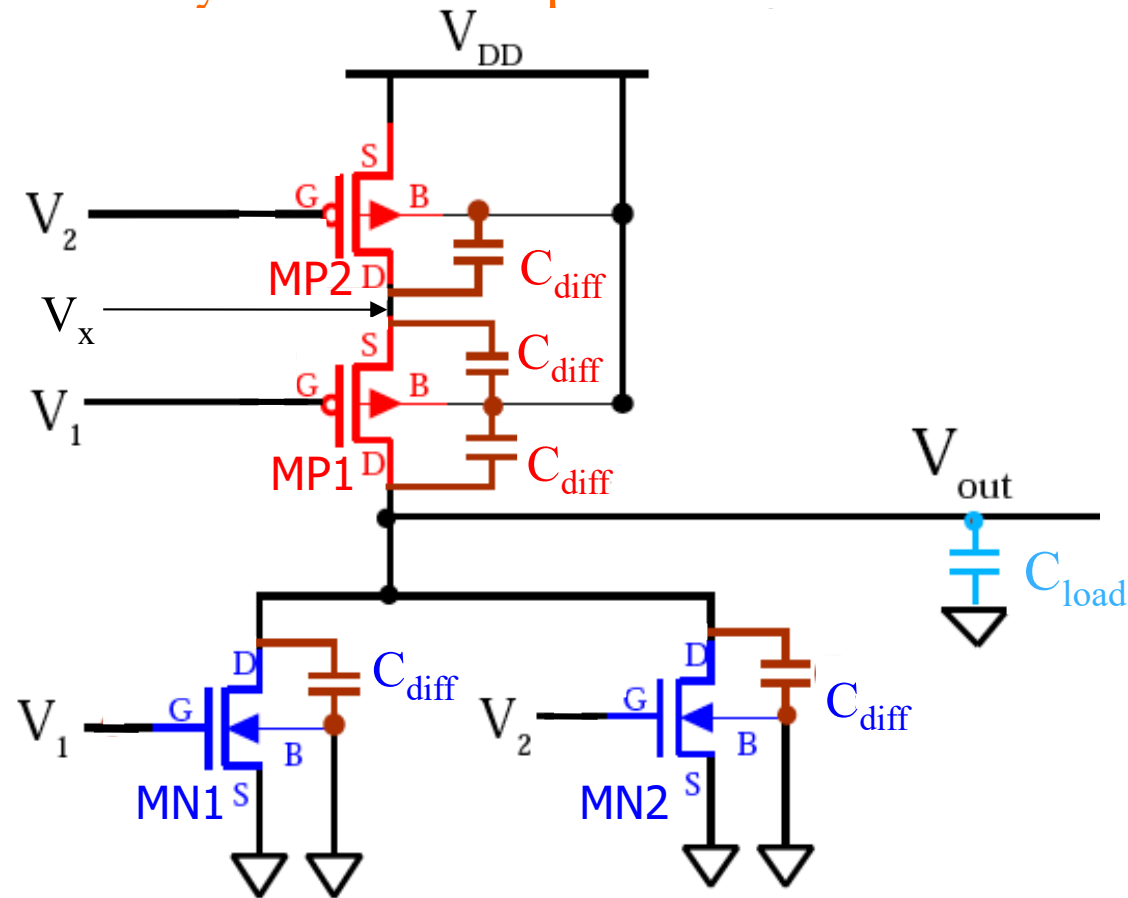

# NOR2 Delay

- Worst case delay for Pull-up?

 

Worst Case for Pull-up  $\rightarrow V_1 = 0, V_2 = V_{DD} \rightarrow 0$  @ $t=0$  &  $V_x \approx V_{out} = 0 \rightarrow V_{DD}$


# NOR2 Delay

□ Worst case delay for Pull-up?

$$C_{\text{load-NR2}} \approx 2C_{\text{diff}} + 3C_{\text{diff}} + C_{\text{load}}$$

$$R_{\text{EQV}} = R_{p2} + R_{p1}$$


Lumped Model

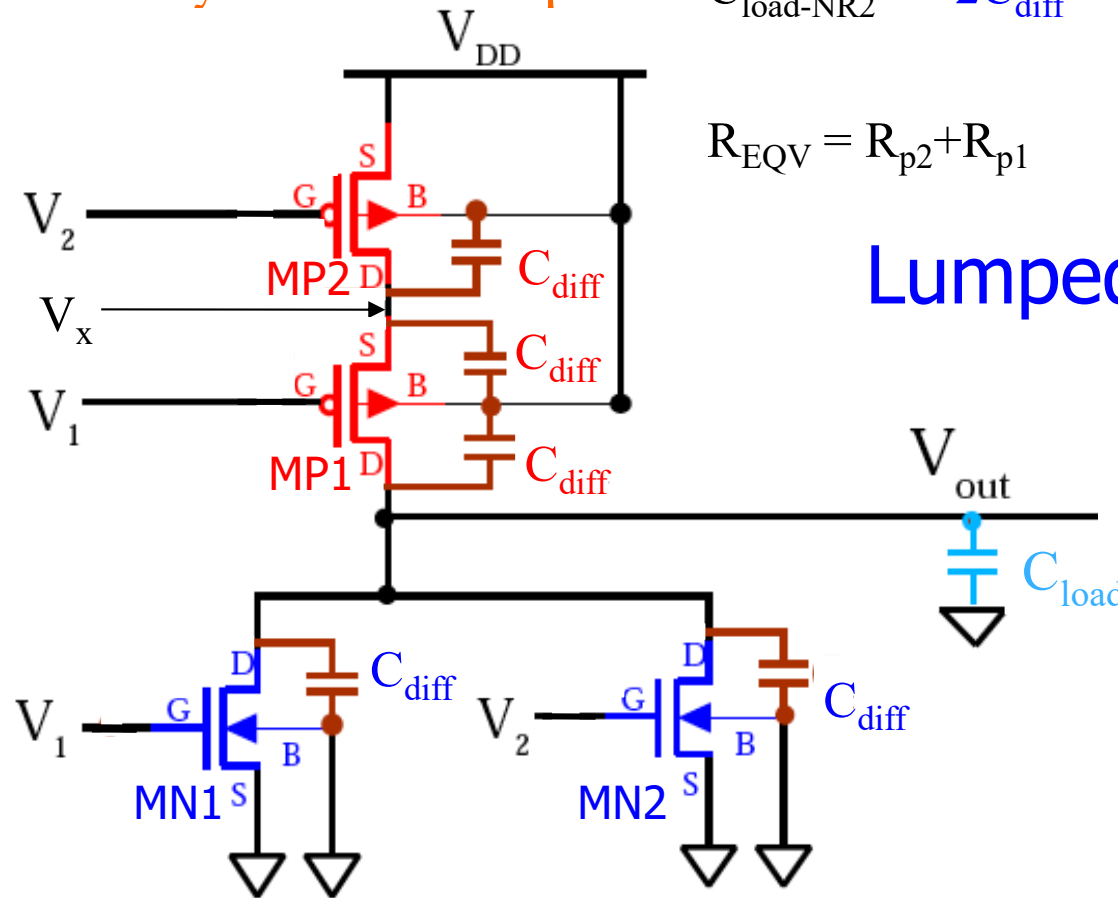

Worst Case for Pull-up  $\rightarrow V_1 = 0, V_2 = V_{DD} \rightarrow 0$  @ $t=0$  &  $V_x \approx V_{out} = 0 \rightarrow V_{DD}$

# NOR2 Delay

□ Worst case delay for Pull-up?

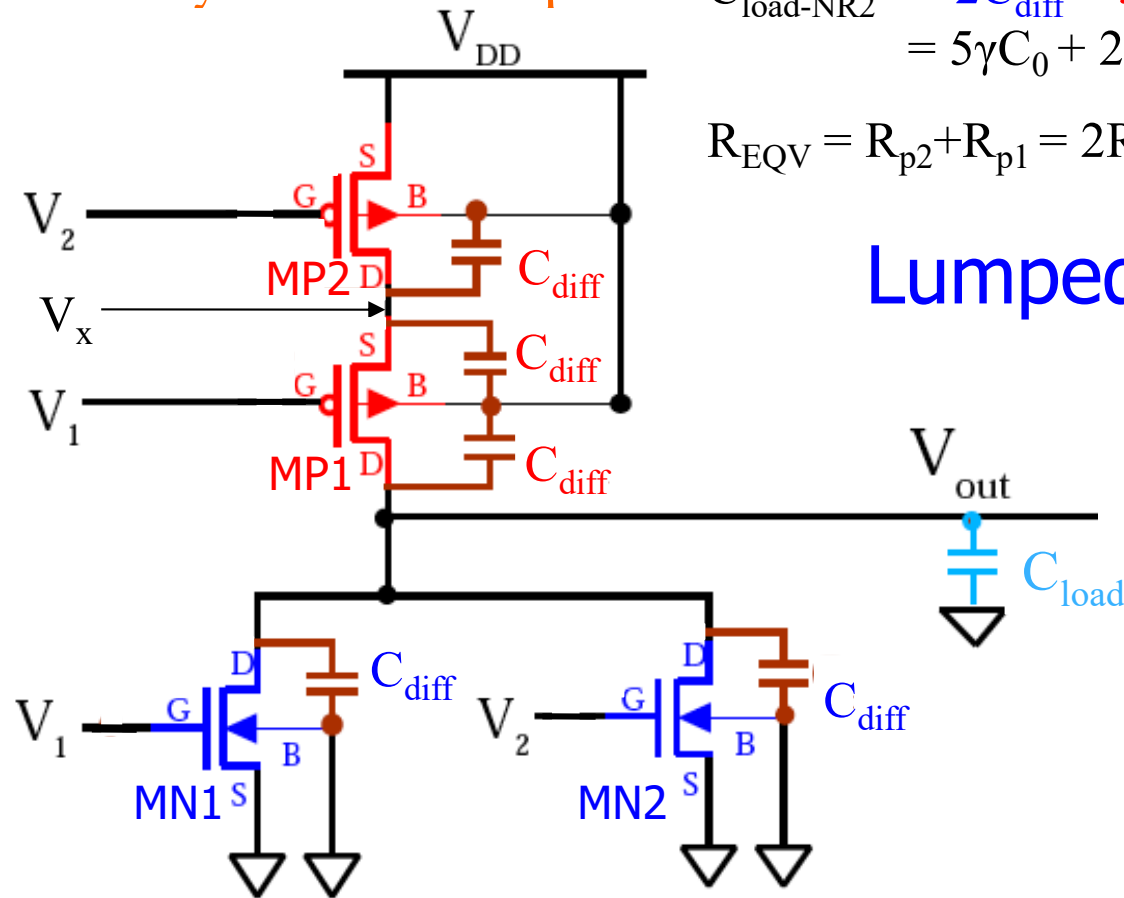

$$C_{\text{load-NR2}} \approx 2C_{\text{diff}} + 3C_{\text{diff}} + C_{\text{load}} = 5\gamma C_0 + 2C_0$$

$$R_{\text{EQV}} = R_{p2} + R_{p1} = 2R_0$$


Lumped Model

Worst Case for Pull-up  $\rightarrow V_1 = 0, V_2 = V_{DD} \rightarrow 0$  @  $t=0$  &  $V_x \approx V_{\text{out}} = 0 \rightarrow V_{DD}$

$$\text{delay} = (5\gamma C_0 + 2C_0)(2R_0) = (10\gamma + 4)\tau$$

# NOR2 Delay

□ Worst case delay?

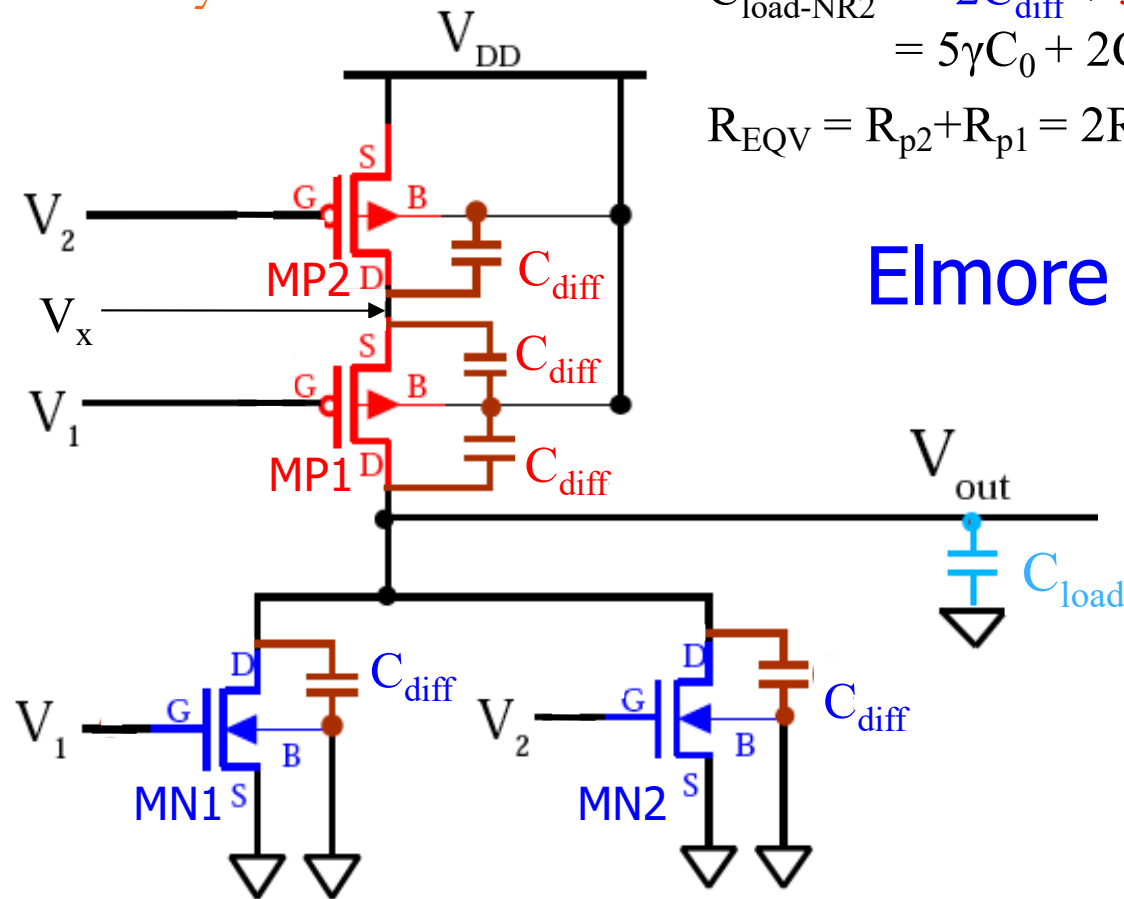

$$C_{\text{load-NR2}} \approx 2C_{\text{diff}} + 3C_{\text{diff}} + C_{\text{load}} \\ = 5\gamma C_0 + 2C_0$$


$$R_{\text{EQV}} = R_{\text{p2}} + R_{\text{p1}} = 2R_0$$

Elmore Model?

Worst Case for Pull-up  $\rightarrow V_1 = 0, V_2 = V_{\text{DD}} \rightarrow 0$  @ $t=0$  &  $V_x \approx V_{\text{out}} = 0 \rightarrow V_{\text{DD}}$

# NOR2 Delay

Worst case delay?

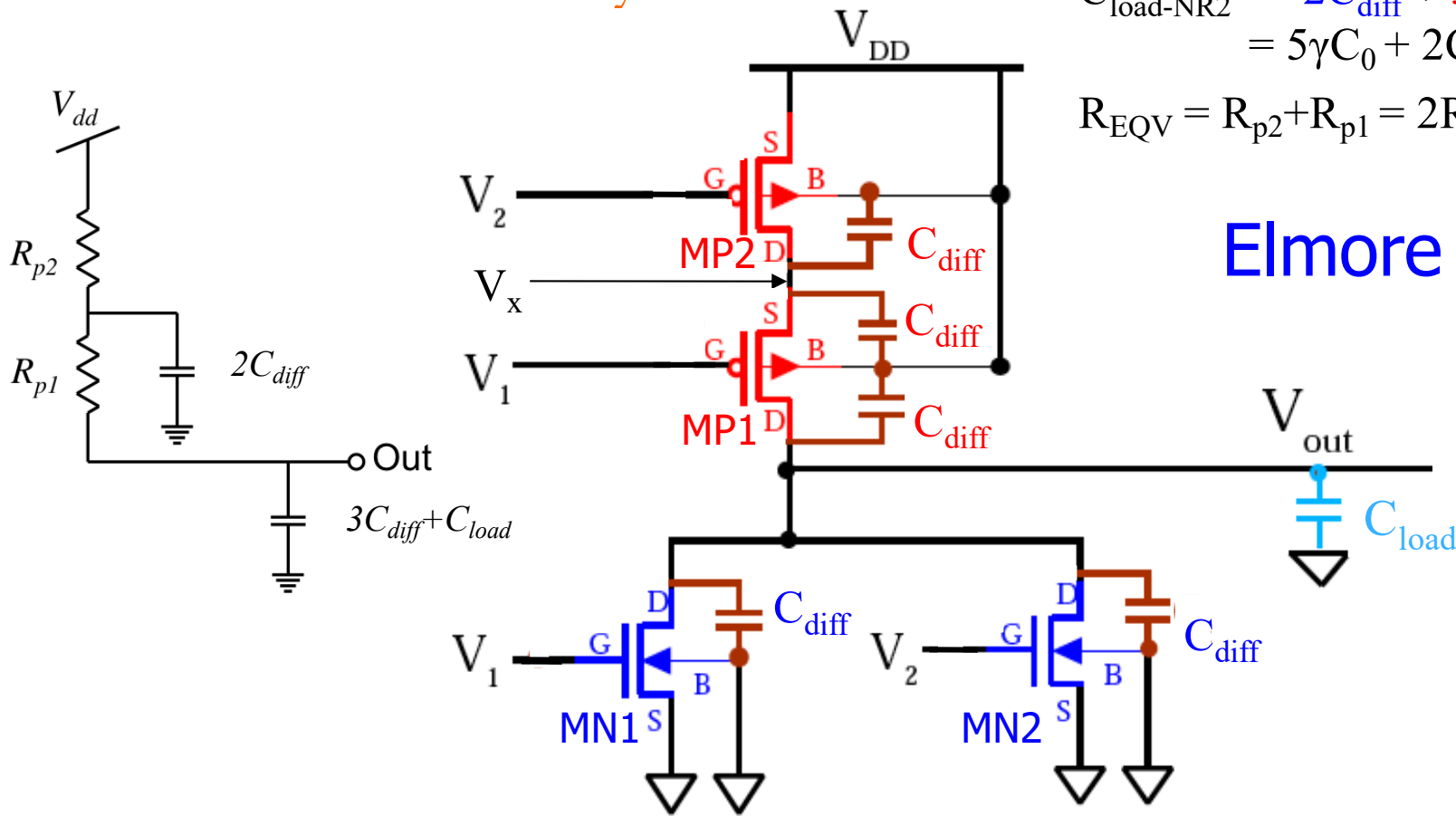

$$C_{load-NR2} \approx 2C_{diff} + 3C_{diff} + C_{load} = 5\gamma C_0 + 2C_0$$

$$R_{EQV} = R_{p2} + R_{p1} = 2R_0$$


Elmore Model?

Worst Case for Pull-up  $\rightarrow V_1 = 0, V_2 = V_{DD} \rightarrow 0$  @  $t=0$  &  $V_x \approx V_{out} = 0 \rightarrow V_{DD}$



# NOR2 Delay

Worst case delay?

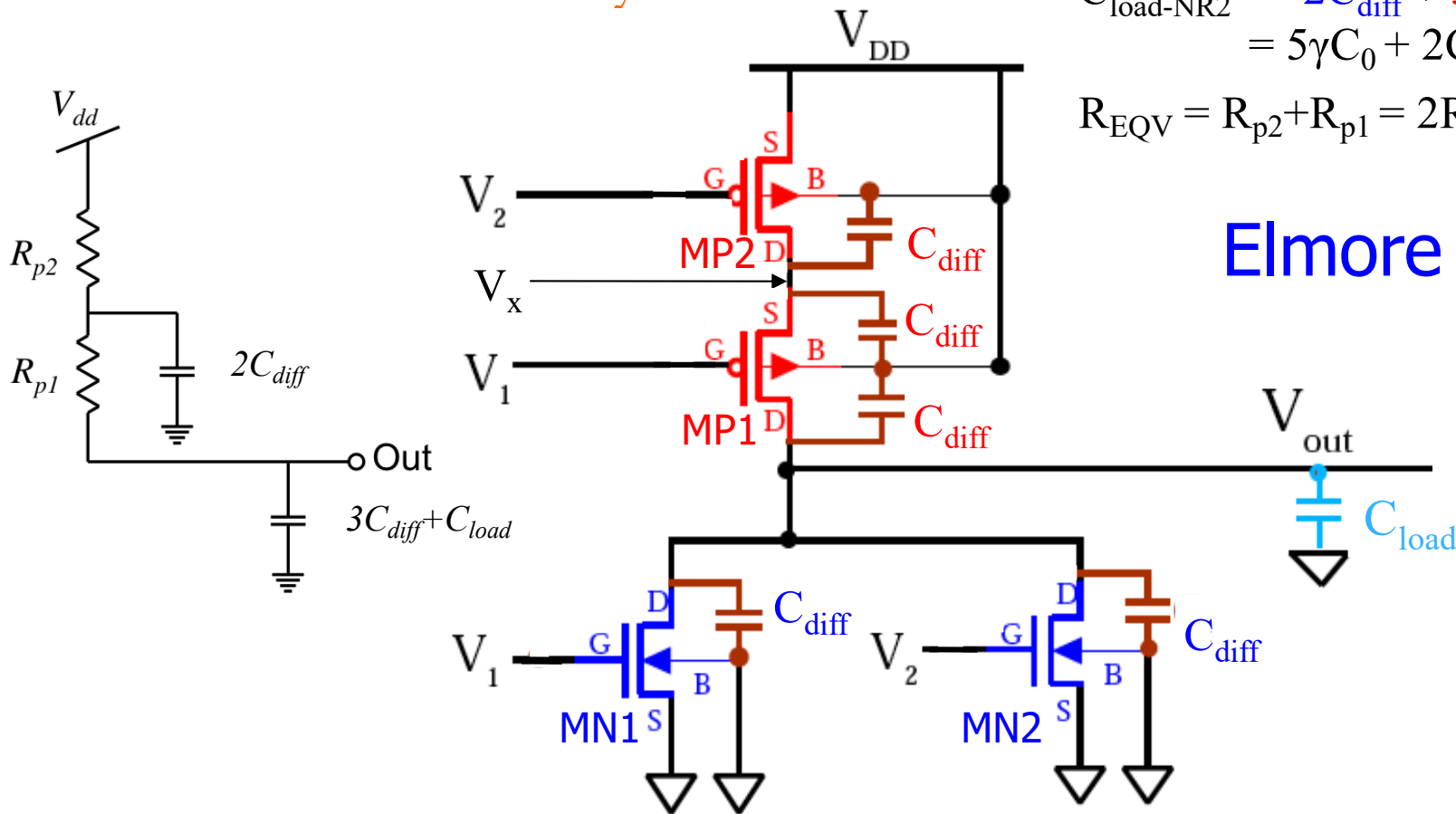

$$C_{\text{load-NR2}} \approx 2C_{\text{diff}} + 3C_{\text{diff}} + C_{\text{load}} = 5\gamma C_0 + 2C_0$$

$$R_{\text{EQV}} = R_{p2} + R_{p1} = 2R_0$$


Elmore Model?

Worst Case for Pull-up  $\rightarrow V_1 = 0, V_2 = V_{DD} \rightarrow 0 @t=0$  &  $V_x \approx V_{\text{out}} = 0 \rightarrow V_{DD}$

$$\text{delay} = (2C_{\text{diff}})(R_{p2}) + (3C_{\text{diff}} + C_{\text{load}})(R_{p1} + R_{p2}) = (8\gamma + 4)\tau$$


# NOR2 Delay

□ Worst case delay Pull-down?

 

# NOR2 Delay


□ Worst case delay Pull-down?

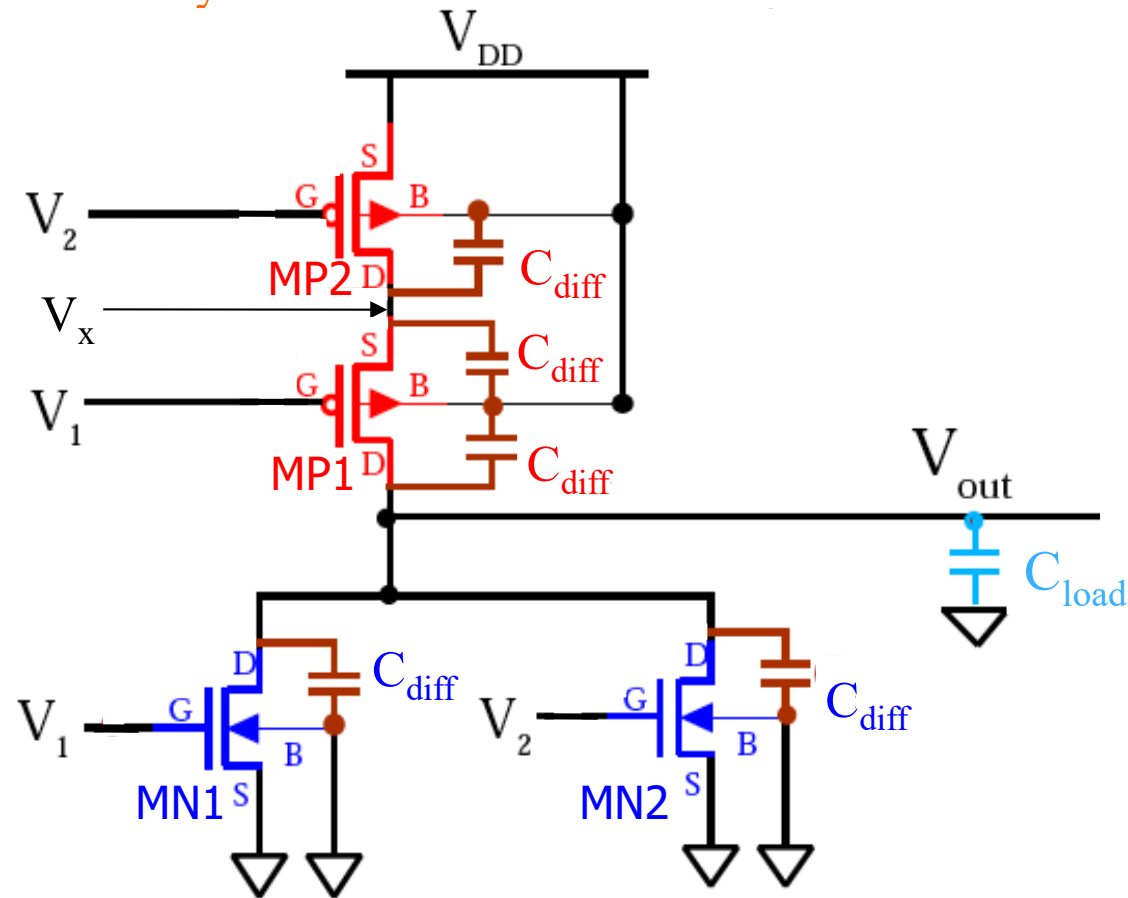

Worst case for Pull-down  $\rightarrow V_1 = 0, V_2 = 0 \rightarrow V_{DD} @ t=0$  &  $V_x \approx V_{out} = V_{DD} \rightarrow 0$

# NOR2 Delay


- Worst case delay Pull-down?

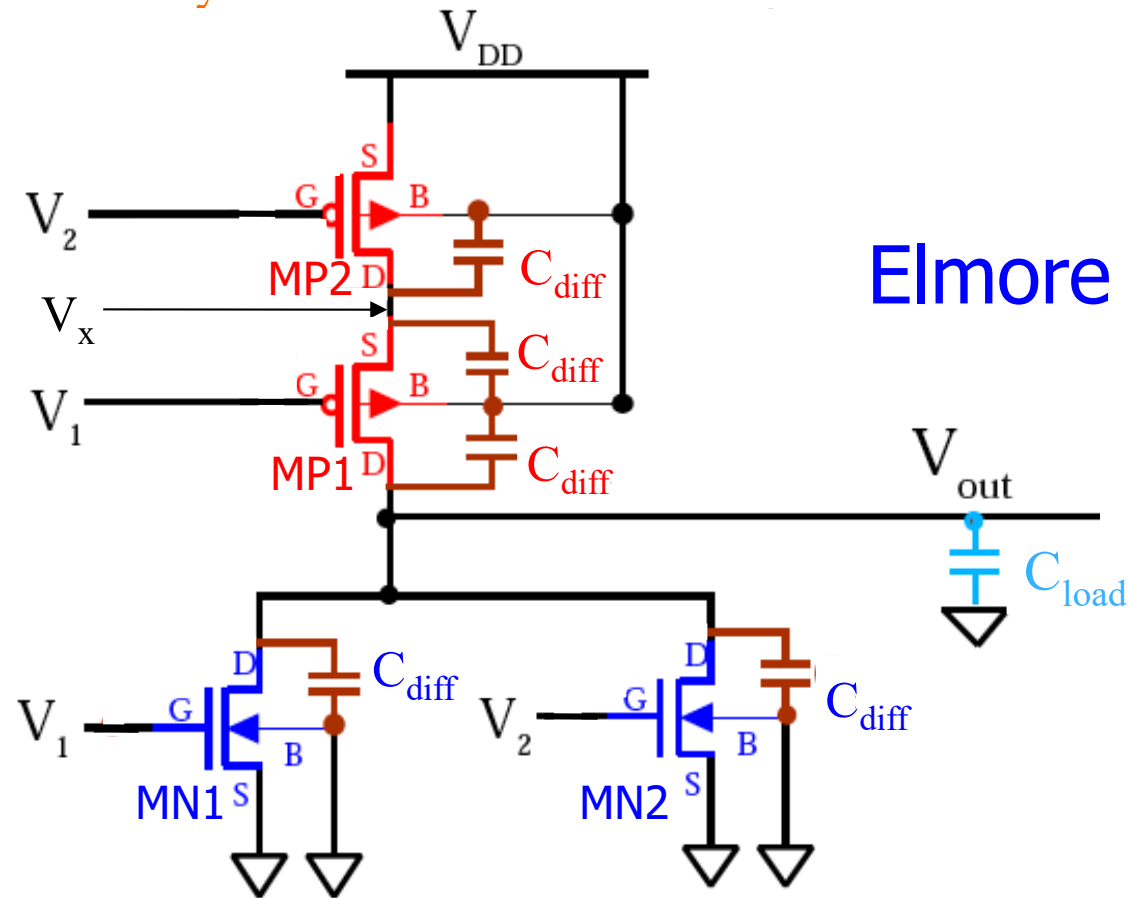

Worst case for Pull-down  $\rightarrow V_1 = 0, V_2 = 0 \rightarrow V_{DD} @ t=0$  &  $V_x \approx V_{out} = V_{DD} \rightarrow 0$

# NOR2 Delay

Worst case delay Pull-down?

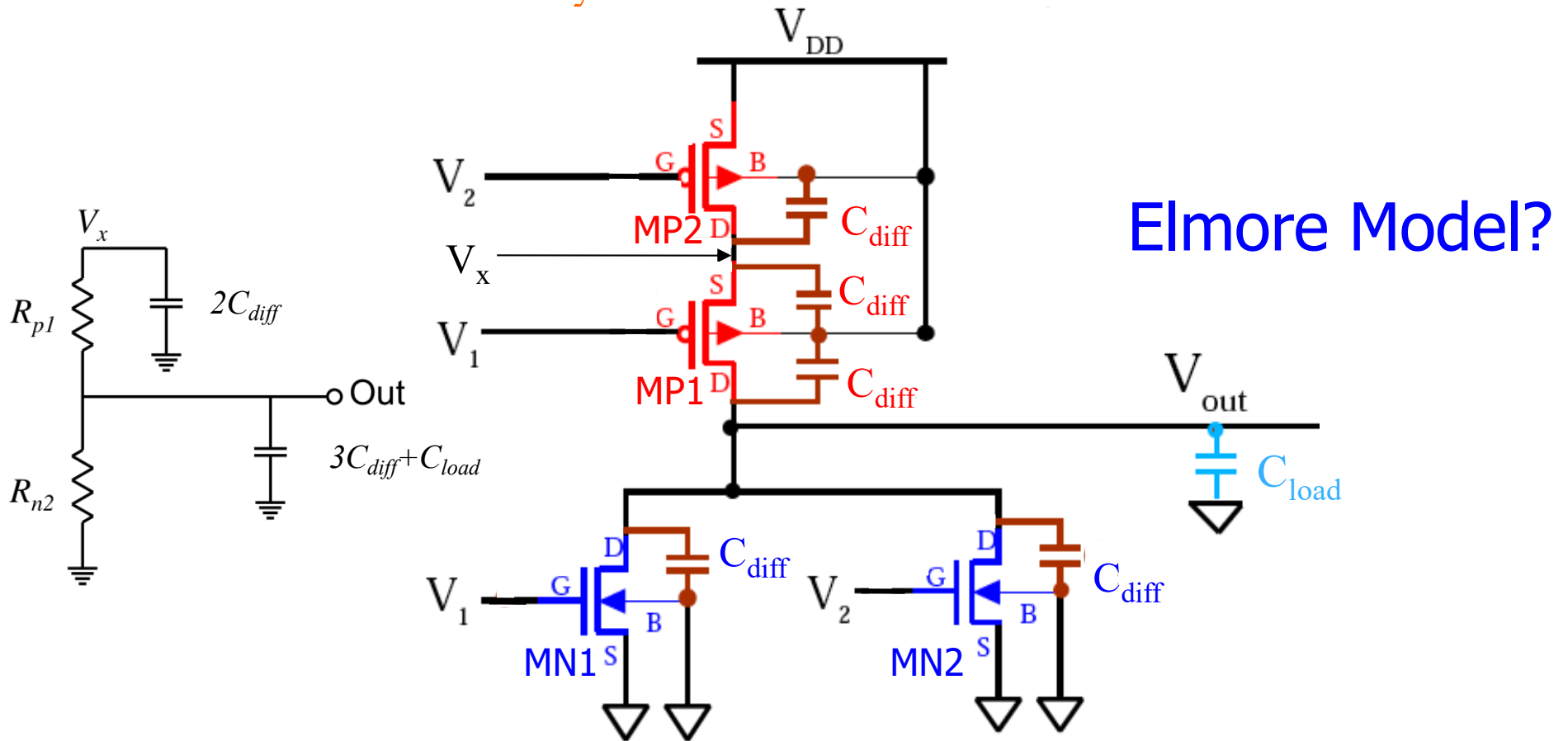


Worst case for Pull-down  $\rightarrow V_1 = 0, V_2 = 0 \rightarrow V_{DD} @ t=0$  &  $V_x \approx V_{out} = V_{DD} \rightarrow 0$


$$\text{delay} = (2C_{diff})(R_{p1} + R_{n2}) + (3C_{diff} + C_{load})(R_{n2}) = (7\gamma + 2)\tau$$




# NAND2 Delay (preclass 11)

 

# Parasitic Caps for NAND2 (worst case)

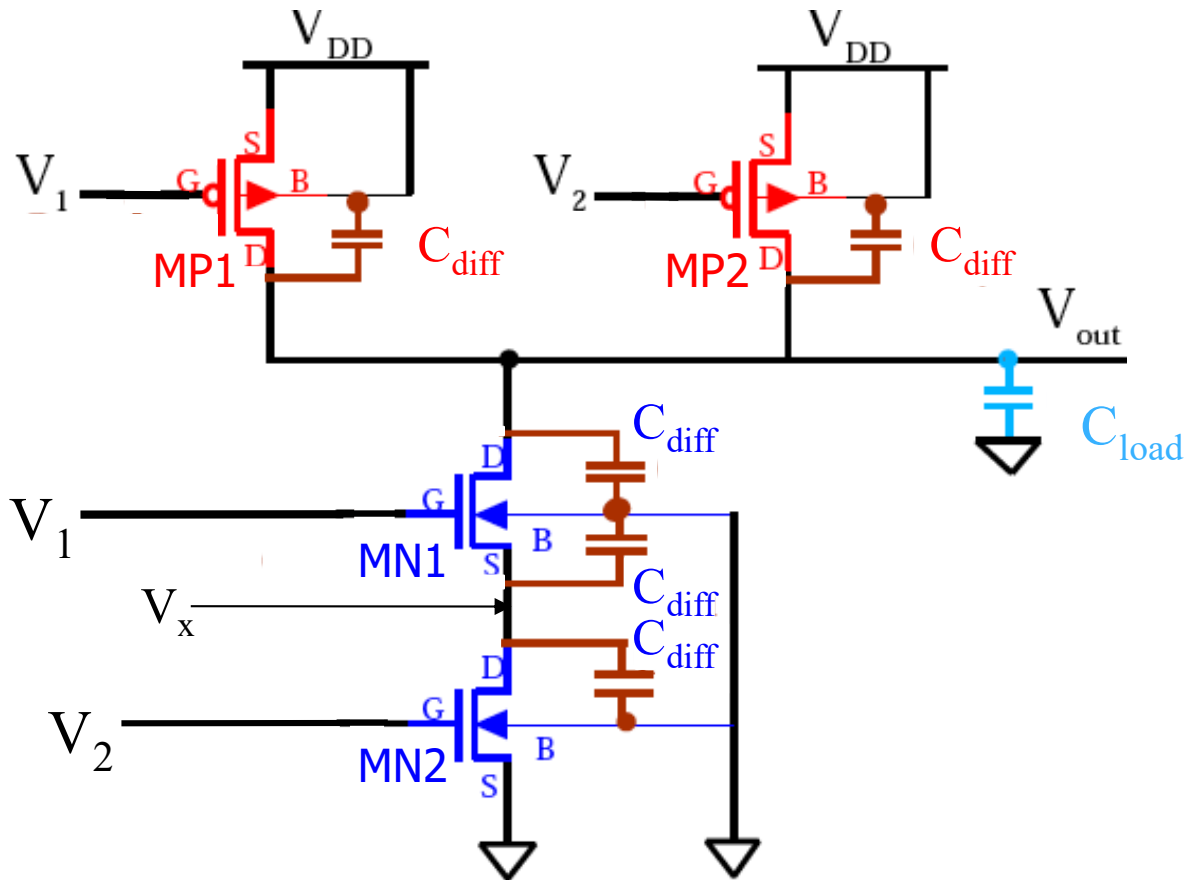


# Parasitic Caps for NAND2 (worst case)

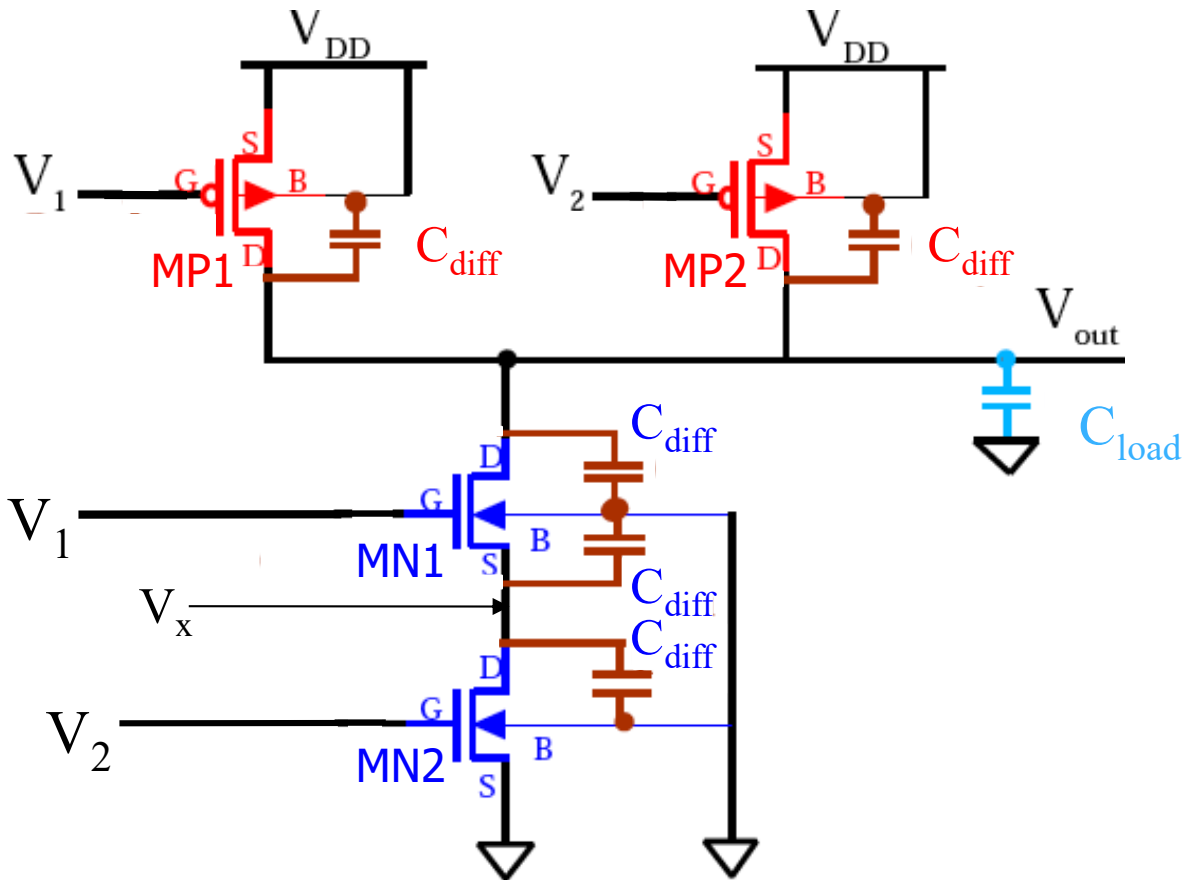

Worst case for Pull-up →




# Parasitic Caps for NAND2 (worst case)

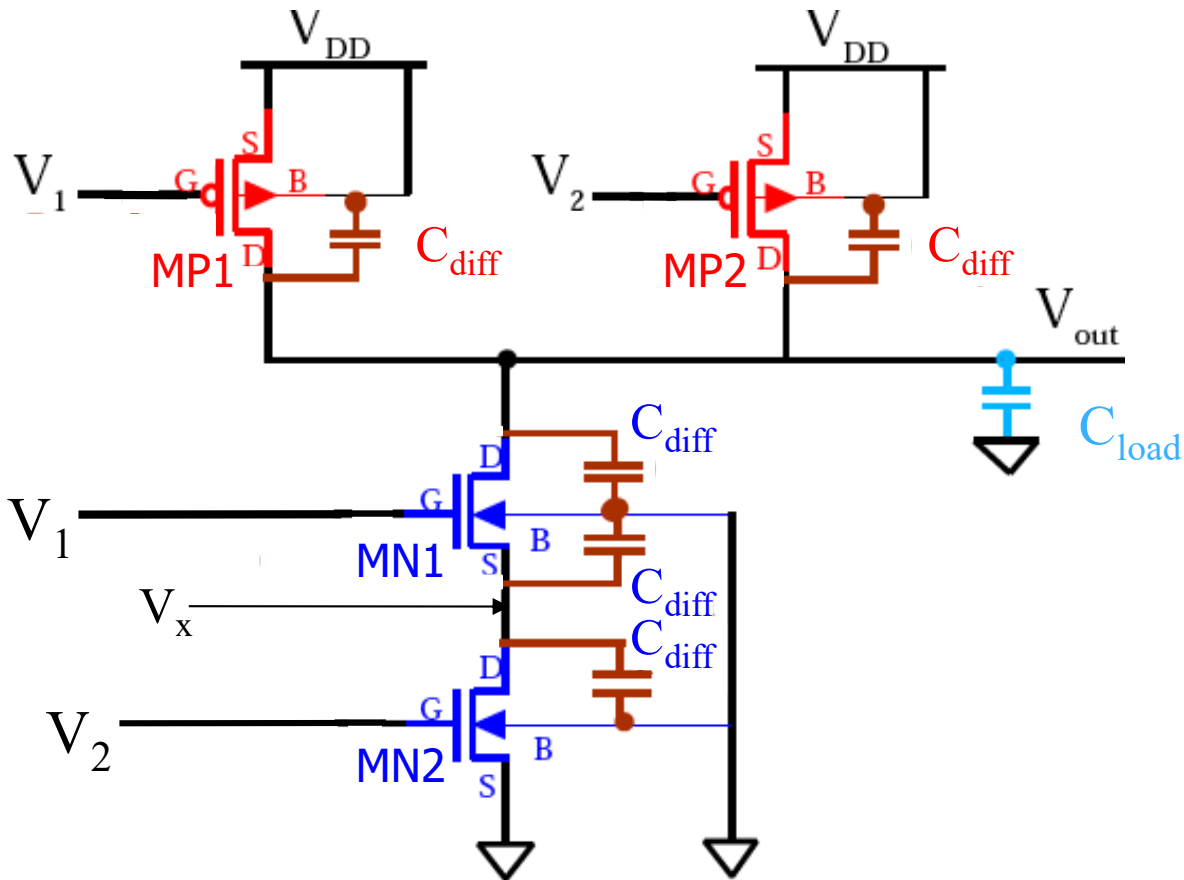


Worst case for Pull-up  $\rightarrow V_1 = V_{DD}, V_2 = V_{DD} \rightarrow 0 @t=0$  &  $V_x \approx V_{out} = 0 \rightarrow V_{DD}$

# Parasitic Caps for NAND2 (worst case)

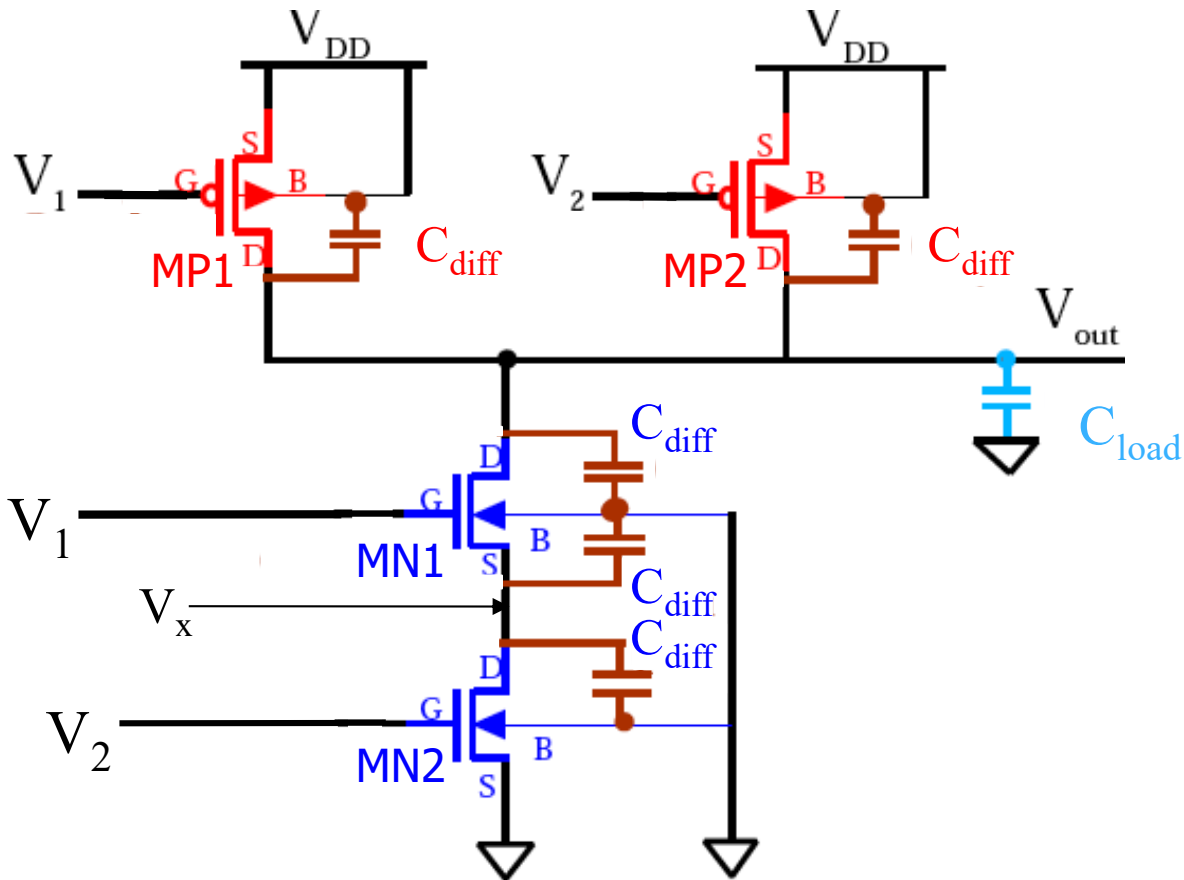

Worst case for pull down →

# Parasitic Caps for NAND2 (worst case)

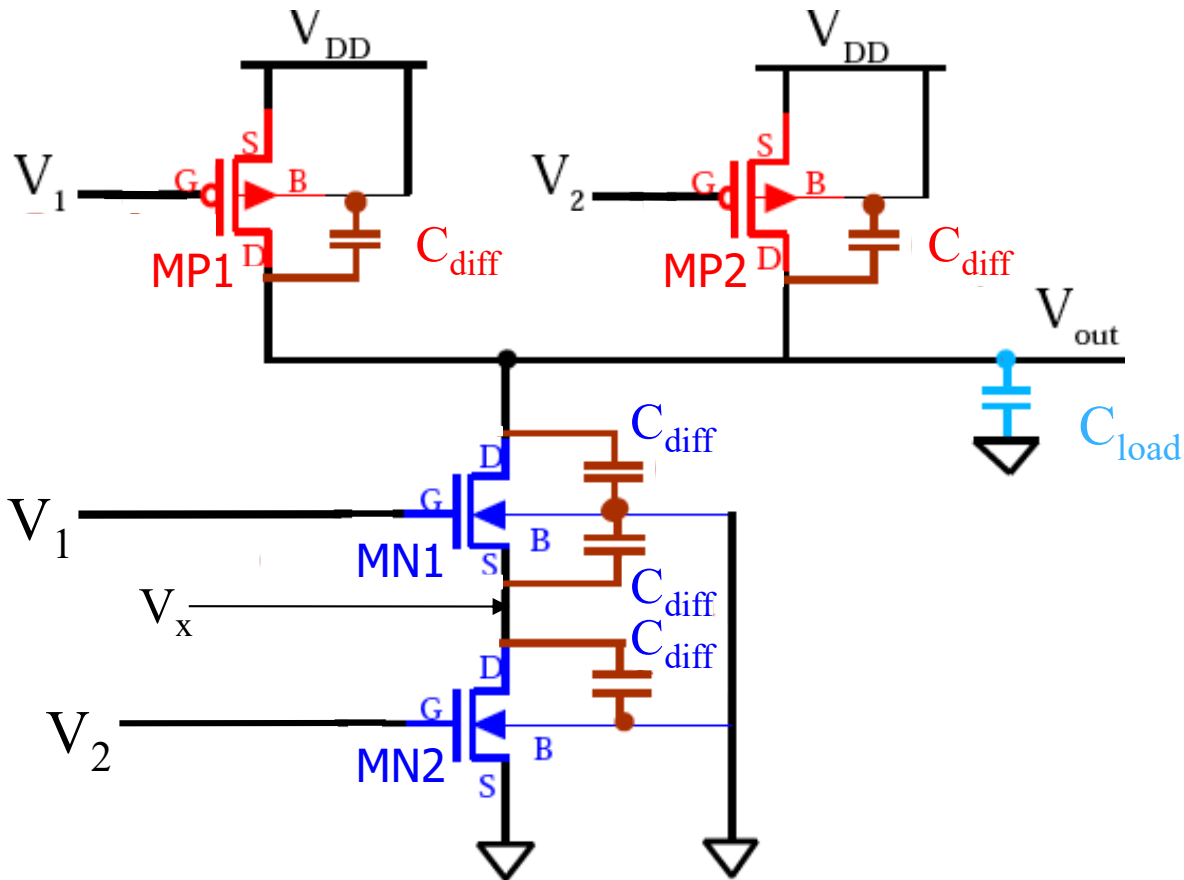

Worst case for pull down  $\rightarrow V_1 = V_{DD}, V_2 = 0 \rightarrow V_{DD} @ t=0$  &  $V_x \approx V_{out} = V_{DD} \rightarrow 0$



# Logic Types

---

- ❑ CMOS Gates
  - Dual pull-down and pull-up networks, only one enabled at a time
  - Performance of gate is strong function of the fanin of gate
    - Techniques to improve performance include sizing, input reordering, and buffering (staging)
- ❑ Ratioed Gates
  - Have active pull-down (-up) network connected to load device
  - Reduced gate complexity at expense of static power asymmetric transfer function
    - Techniques to improve performance include sizing to improve noise margins and reduce static power
- ❑ Pass Gates
  - Implement logic gate as switch network for area and often delay win
  - Long cascades of switches result in quadratic increase in delay
  - Also suffer from reduced noise margins ( $V_T$  drop)
    - Use level-restoring buffers to improve noise margins
- ❑ Dynamic logic ... next time



# Idea

---

- ❑ Elmore delay calculation allows us to estimate delay for distributed RC network
  - Necessary for pass transistors
- ❑ Wires are distributed RC
  - Half delay lumped calculation
  - Still quadratic in length



# Admin

---

- Project 1 out now
  - Design 8-bit ripple-carry adder
    - You already know how to do this
    - Refresh yourself on binary addition of 2 bits
  - Work **individually**
  - Full Report due F 3/28
  - **Can't pass the class if you don't turn in projects**
    - Can't do project last minute



# Acknowledgement

---

- ❑ Prof. André DeHon (University of Pennsylvania)
- ❑ Prof. Tania Khanna (University of Pennsylvania)