 


Today's Question: How do we drive a large load
 (e.g. $C_{load} = 4 \times 10^4 C_0$) with minimum delay?
 Detail buffer count and sizing.

Assume:

- velocity saturated sizing for gate drive; inverter sizing is: $W_n=2$, $W_p=2$
- Start with $C_{diff} = 0$ case (for simplicity)

1. If we had one inverter stage to size, how should it be sized?




(a) Write delay equation from $R_0/2$ drive through driving C_{load} .

(b) Symbolic expression for delay-minimizing W_N .

(c) Concrete size, W_N , for $C_{load} = 4 \times 10^4 C_0$.

 2. If we had k inverter stages to size, how should the each be sized?



(a) Write delay equation.

(b) Symbolic expression for delay-minimizing W_{Ni} .

(c) Symbolic expression for total delay using solution above.

3. What number of stages, N , minimizes total delay?

(a) Expression to minimize total delay.


(b) Solve for k .

(c) What is the stage size relation at the optimal k ?

(d) What is the stage count for $C_{load} = 4 \times 10^4 C_0$?

(e) What is the minimum delay for $C_{load} = 4 \times 10^4 C_0$?

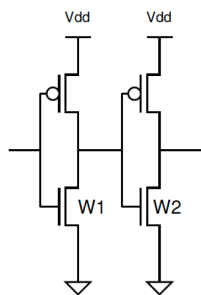4. If $C_{diff} = \gamma C_{gate}$, what is the stage delay for a $W1$ inverter driving a $W2$ inverter?



5. How does optimal stages and buffering change if we include $C_{diff} = \gamma C_{gate}$?

(a) Write delay equation.

(b) Symbolic expression for delay-minimizing W_{Ni} .

(c) Compare with $C_{diff} = 0$ ($\gamma = 0$) case above.

(d) Symbolic expression for total delay.

(e) What is the optimal stage size relation when $\gamma \geq 0$?

(f) For what γ are the following the optimal ρ ?

(**Hint:** solve for γ in terms of ρ)

ρ	γ
3	
4	