

# ESE3700: Circuit-Level Modeling, Design, and Optimization for Digital Systems

---

Lec 16: April 2, 2025  
Dynamic Logic





# Today

---


- Dynamic (Clocked) Logic
  - Strategy
  - Form
  - Compare CMOS

# Clocking

---




# Latch Timing Issues

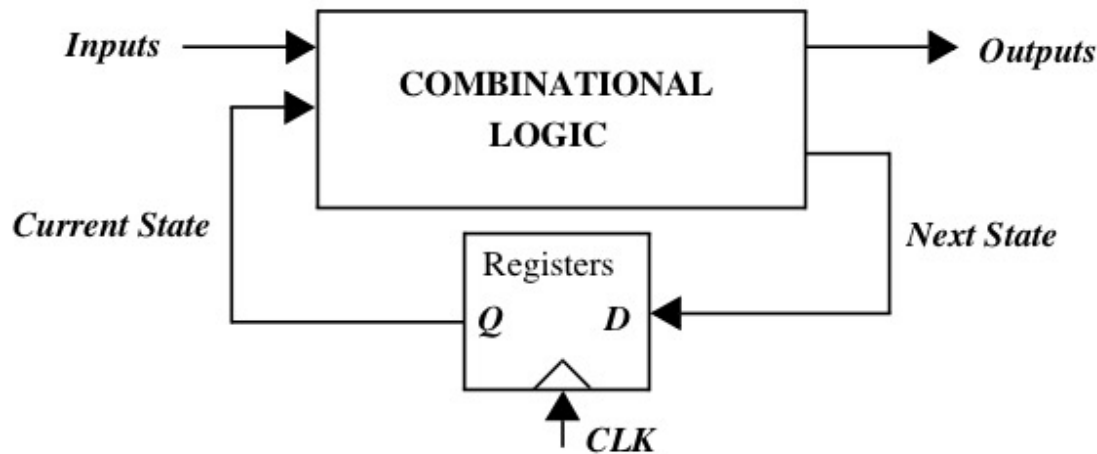

$$T \geq t_{c-q} + t_{plogic} + t_{su}$$
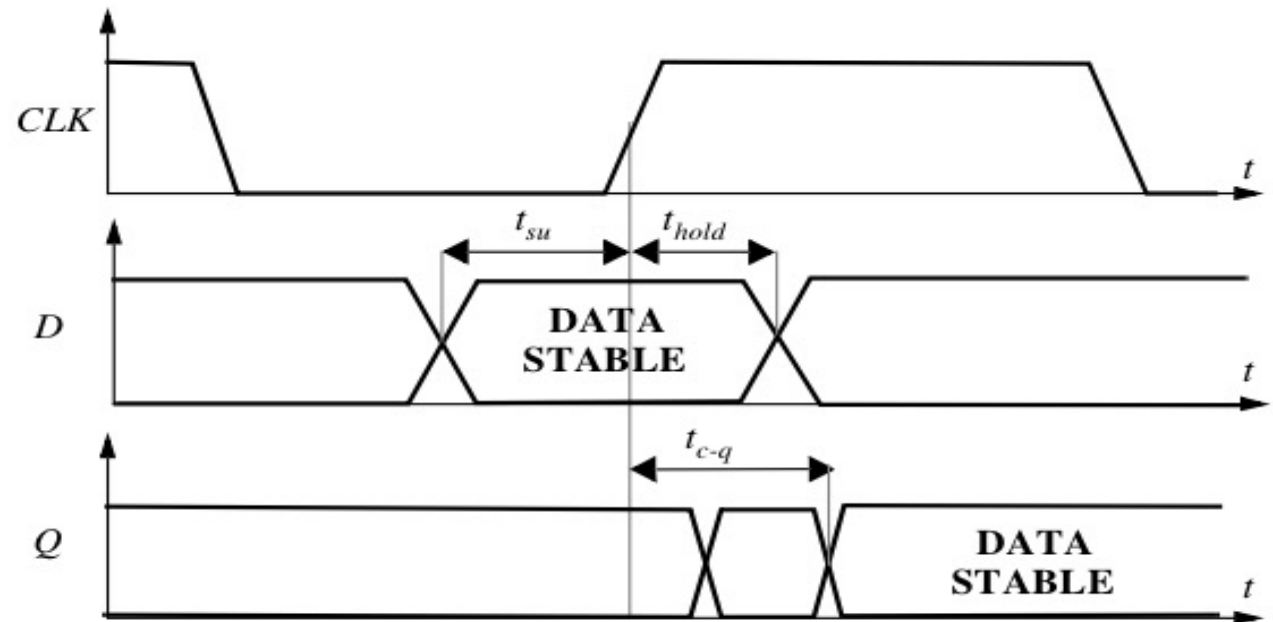
$$t_{cdregister} + t_{cdlogic} \geq t_{hold}$$





# Clocking Highlights

---

- ❑ Breaking logic up with registers allows circuit to run at high frequency
  - Inputs decoupled from outputs
- ❑ Clock discipline simplifies logic composition
  - Abstracts many internal timing details
  - Just concerned with making clock period long enough
- ❑ Design Discipline – keeping data stable around clock edge
  - Setup, hold time – determined by latch circuit
  - Worst case and minimum  $\text{Clk} \rightarrow \text{Q}$  delay for latch



# Clocking

---

- ❑ Circuits typically operate in a clocked environment
  - Synchronous circuits
- ❑ Gives some additional structure we can exploit →  
dynamic logic


# Dynamic Logic

---


 
# Motivation


- We would like to avoid driving both pullup/pulldown networks
  - reduce capacitive load
    - Power, delay






 
# Motivation

- ❑ We would like to avoid driving both pullup/pulldown networks
  - reduce capacitive load
    - Power, delay
- ❑ Ratioed Logic



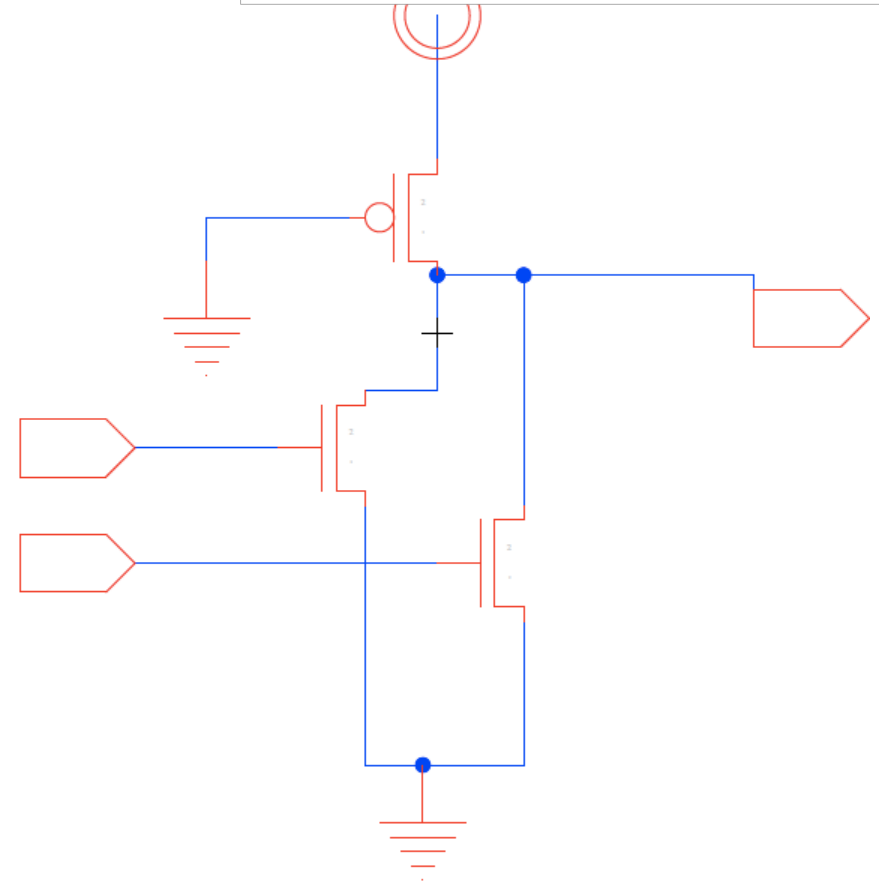
 
# Motivation

- We would like to avoid driving both pullup/pulldown networks
  - reduce capacitive load
    - Power, delay
- Ratioed Logic cons:
  - Large devices for ratioing
    - Meeting noise margins
  - Slow pullup
  - Static power



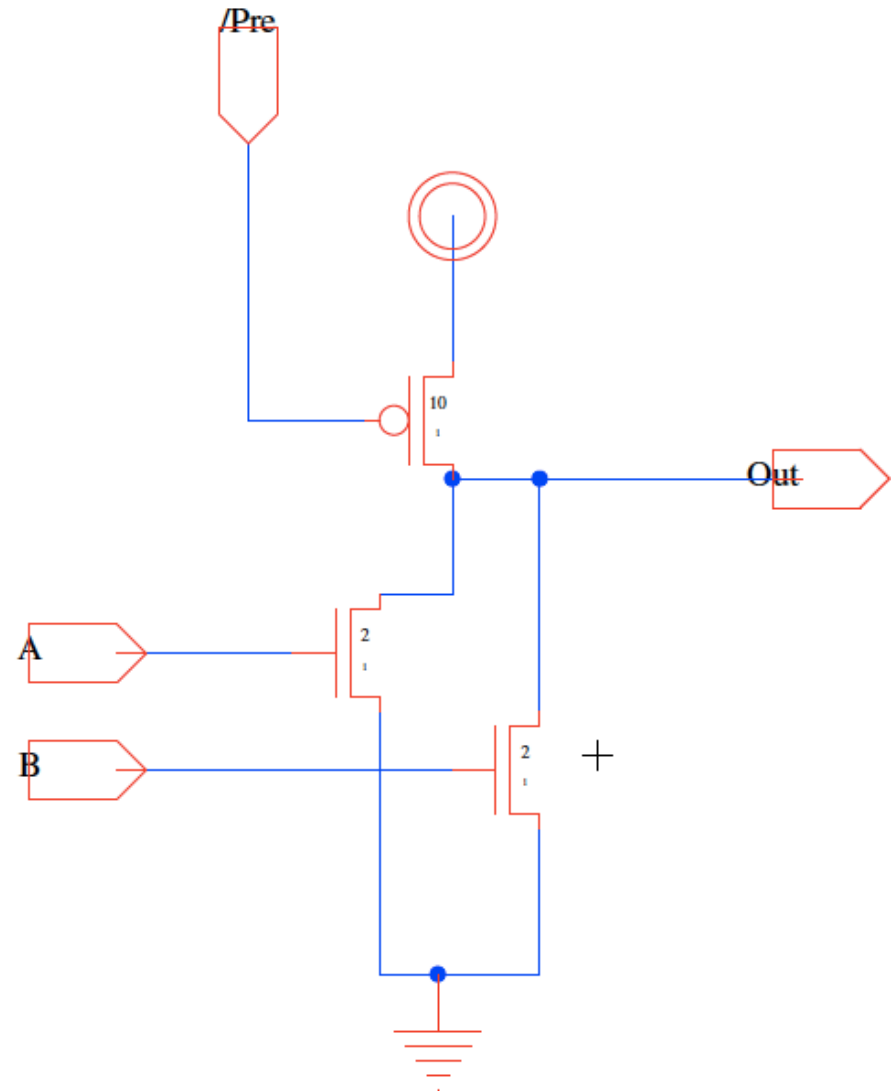 
# Idea

- Use clock to disable pullup network during logic evaluation



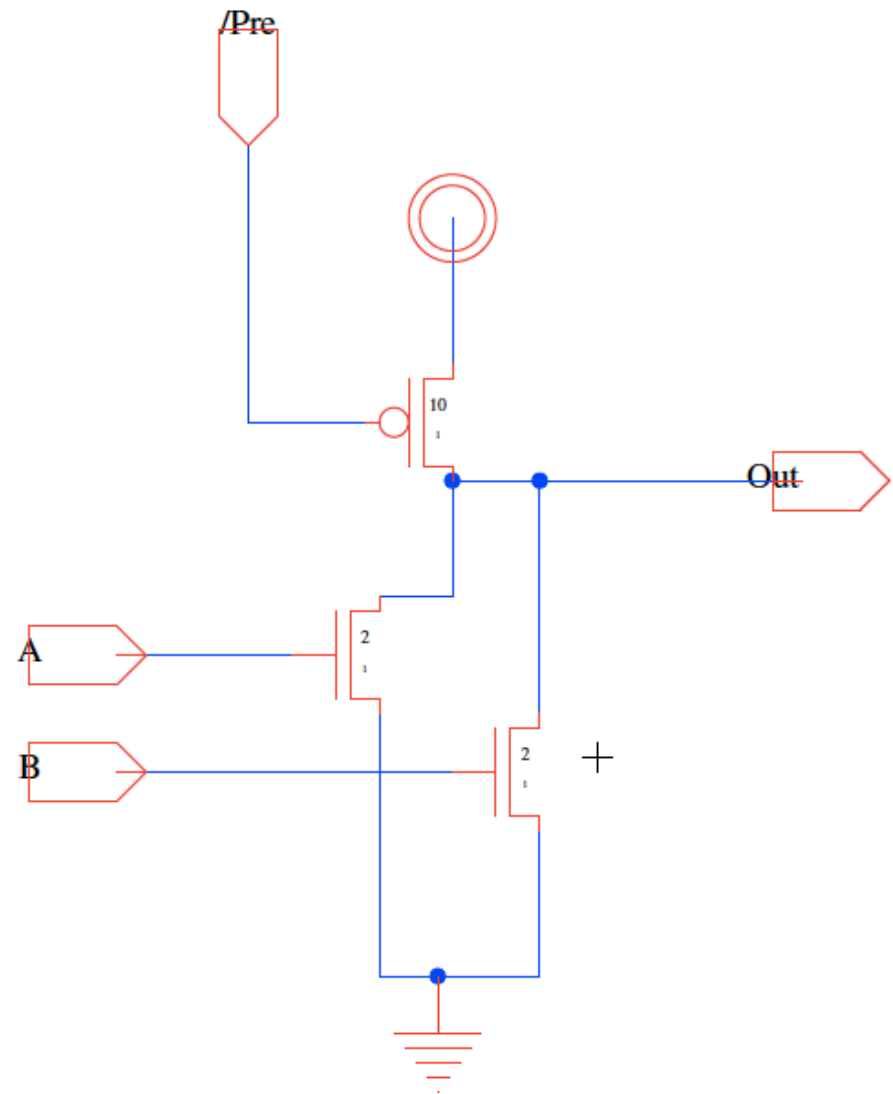
# Idea

- ❑ Use clock to disable pullup network during logic evaluation
- ❑ Define two phases
  - Pre-charge
    - Output pre-charged
  - Evaluation
    - Pulldown network evaluates gate logic



 
# Discuss (Preclass 1)

- ❑ Use CLK to disable pullup during evaluation
- ❑ What is  $V_{out}$  when:
  - $\text{/Pre}=0, A=B=0$ ?
  - $\text{/Pre}=0 \rightarrow 1, A=B=0$ ?
  - $\text{/Pre}=1, A=0, B=0 \rightarrow 1$ ?



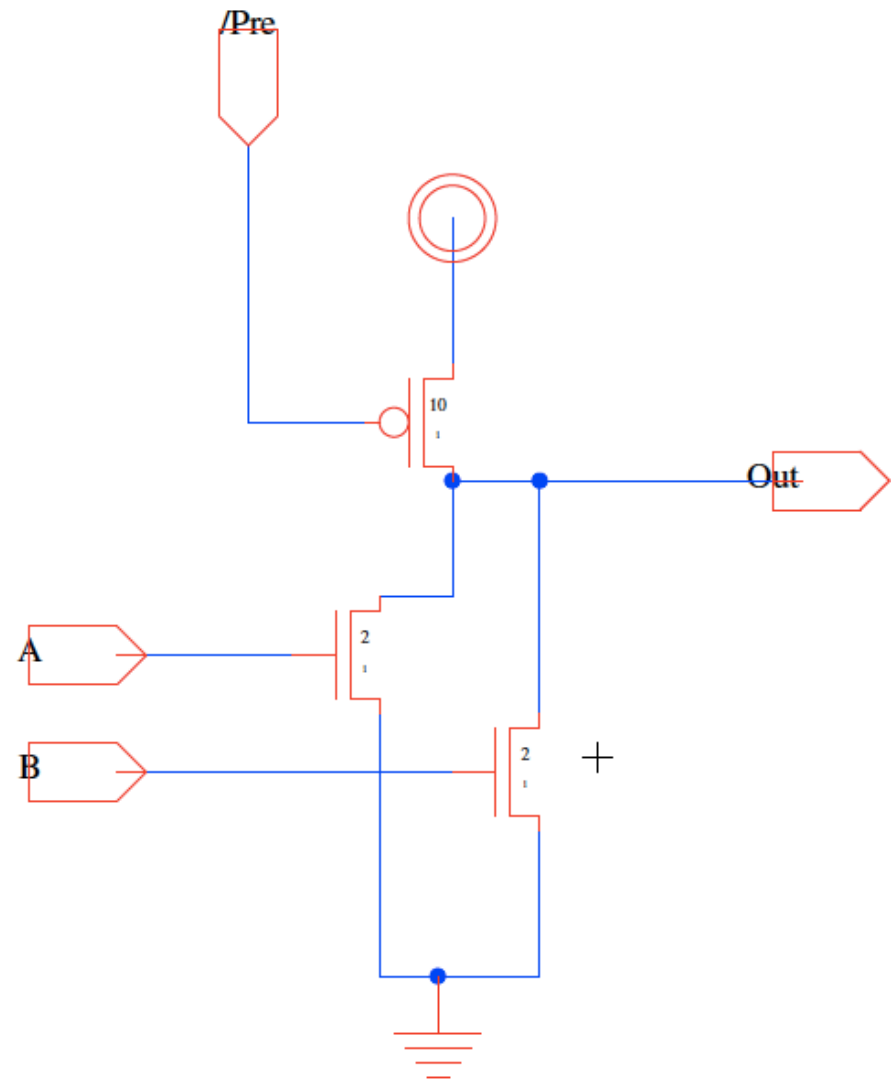
# Discuss (Preclass 1)

- ❑ Use CLK to disable pullup during evaluation
- ❑ What is  $V_{out}$  when:
  - $/Pre=0, A=B=0$ ?
  - $/Pre=0 \rightarrow 1, A=B=0$ ?
  - $/Pre=1, A=0, B=0 \rightarrow 1$ ?
- ❑ Sizing implication?
- ❑ Concerns?
- ❑ Requirements?



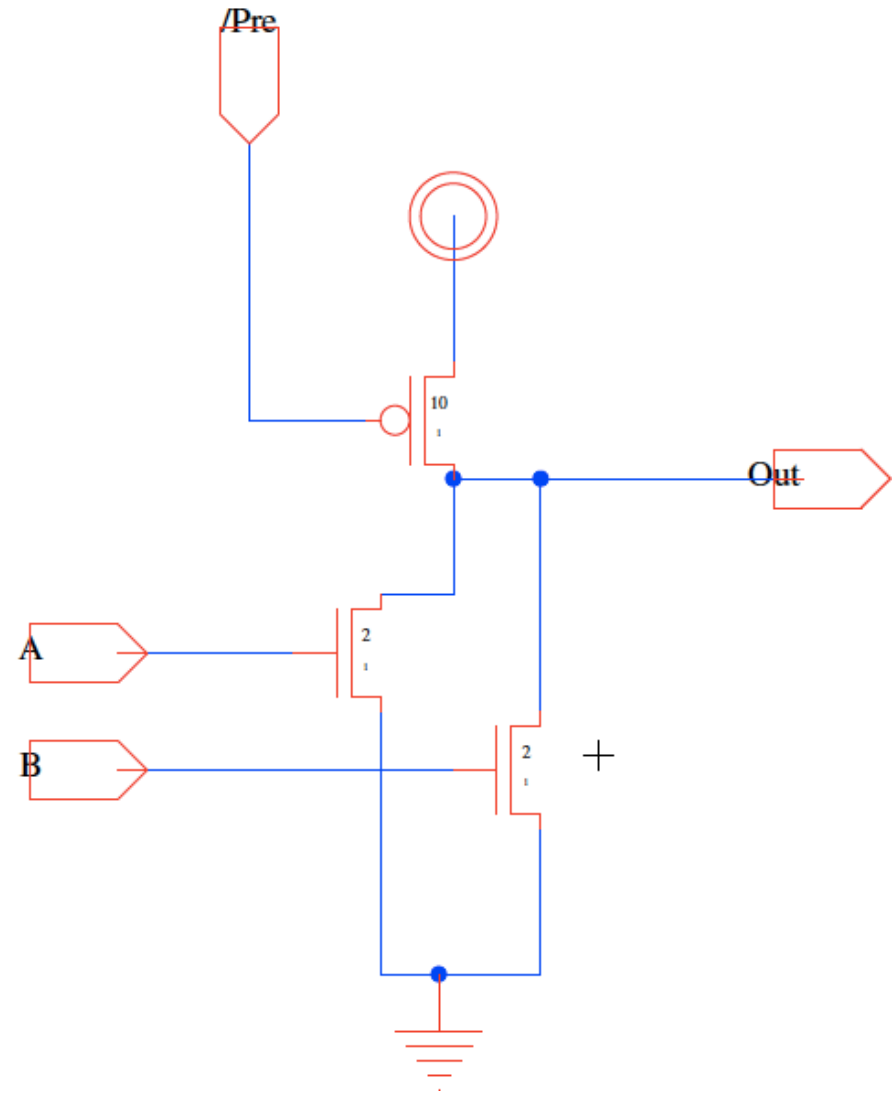
# Advantages

- ❑ Large load device
  - Driven by CLK—not data
  - Can pullup quickly without putting load on logic
- ❑ Single pulldown network
  - Don't have to size for ratio with pullup
  - Swings rail-to-rail





# Cascaded Dynamic Logic


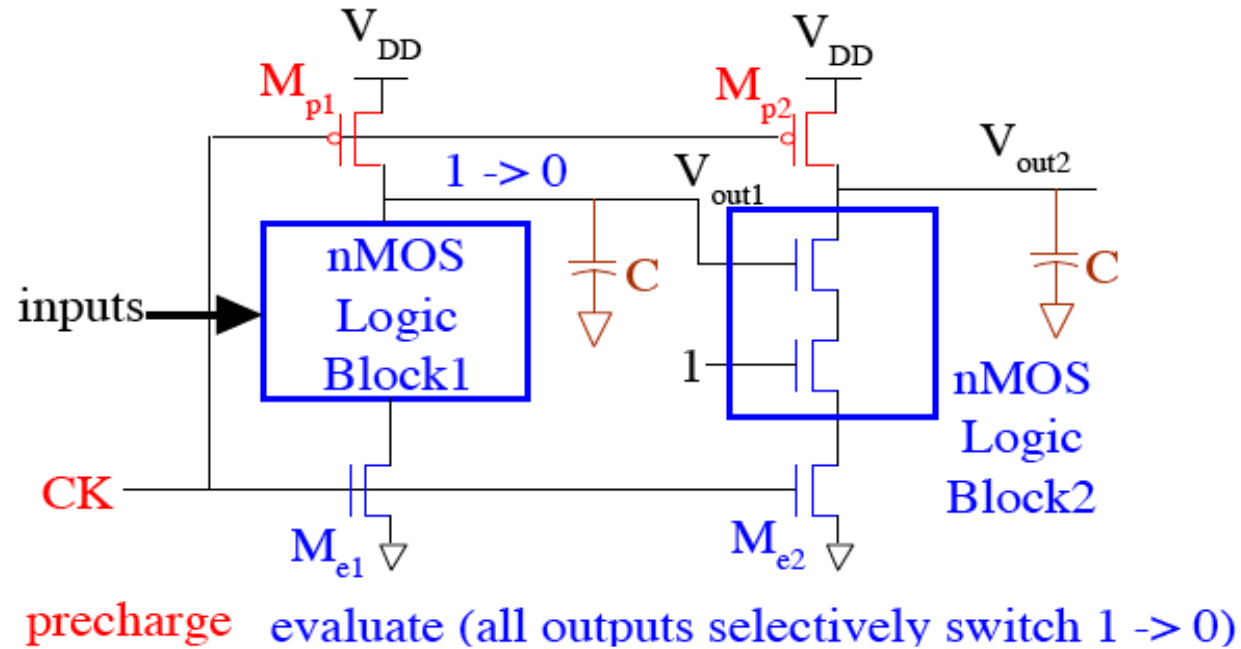





# Cascaded Dynamic Logic

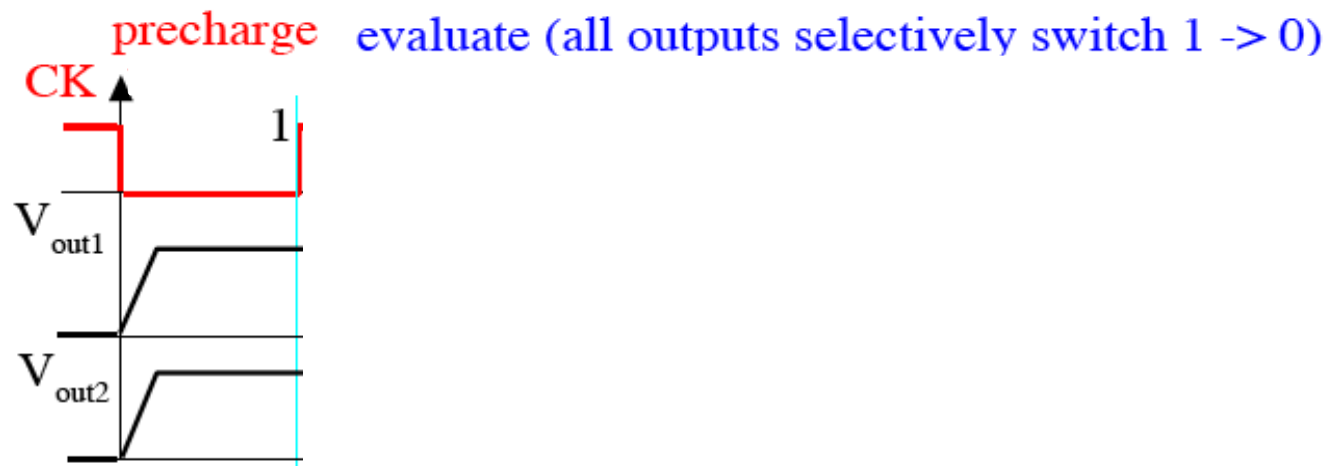 


# Cascaded Dynamic Logic

  



# Cascaded Dynamic Logic

 

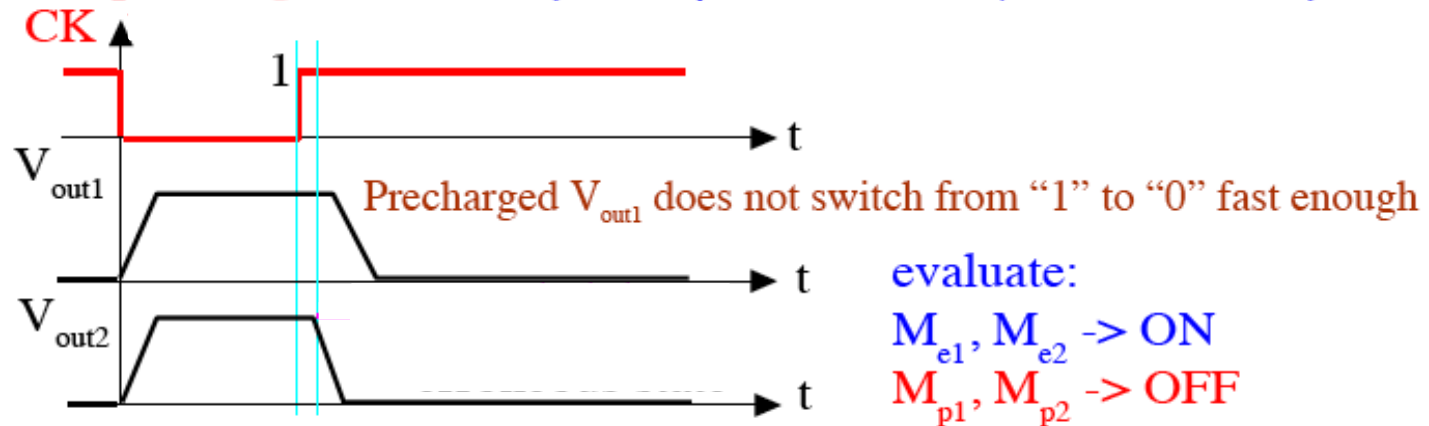precharge evaluate (all outputs selectively switch 1 -> 0)



# Cascaded Dynamic Logic

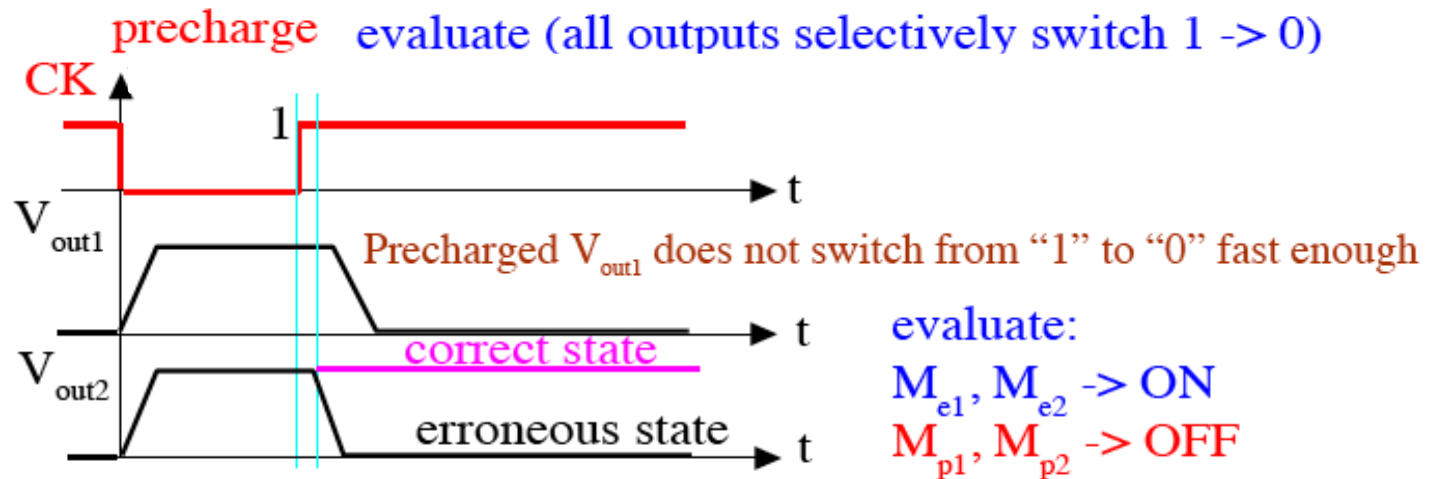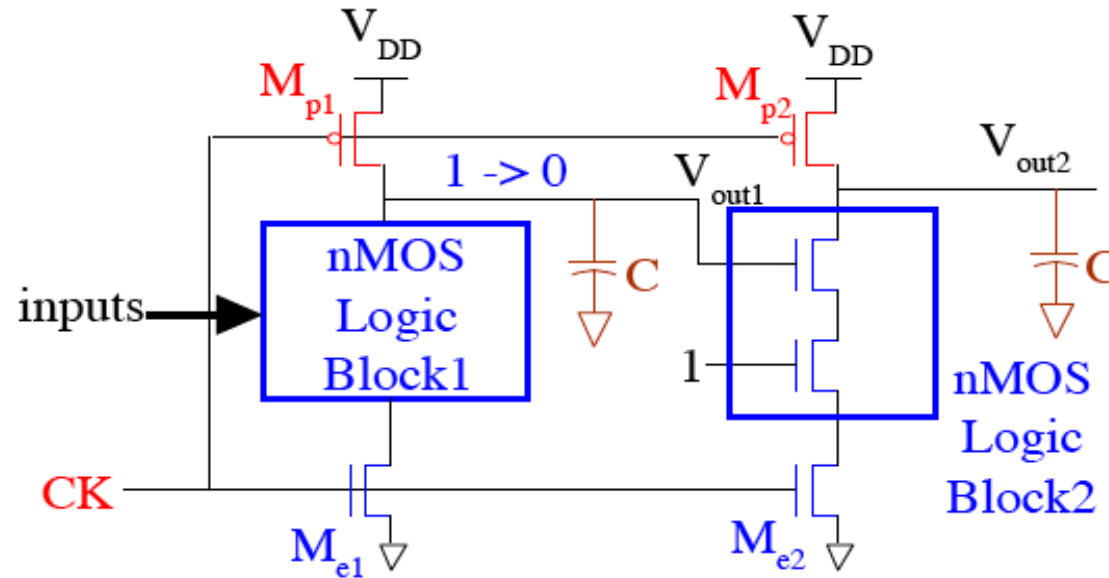


**PROBLEM: ALL STAGES MUST EVALUATE SIMULTANEOUSLY  
 SINGLE CLOCK DOES NOT PERMIT PIPELINING OF STAGES**




# Domino Logic

---

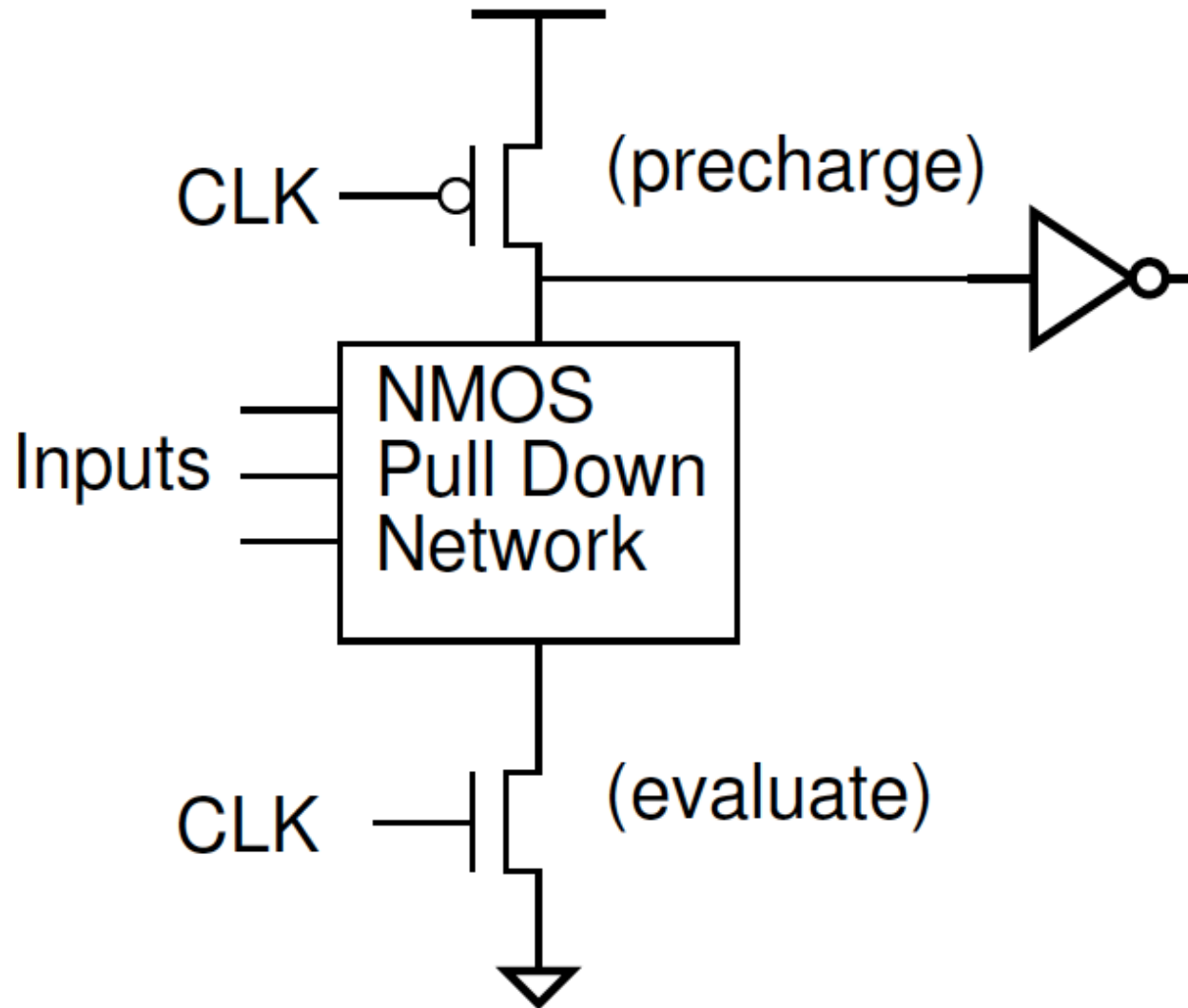

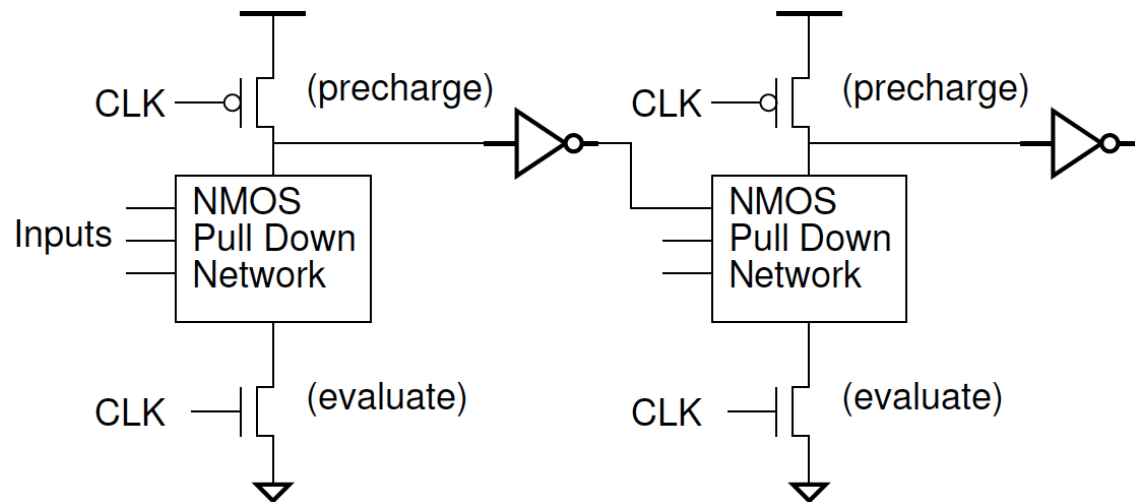
# Requirements


- ❑ Single transition
  - Once transitioned, it is done → like domino falling
- ❑ All inputs at 0 during precharge
  - “Outputs” pre-charged to 1 then inverted to 0
- ❑ Non-inverting gates fundamental gate



# Cascaded Domino CMOS Logic Gates


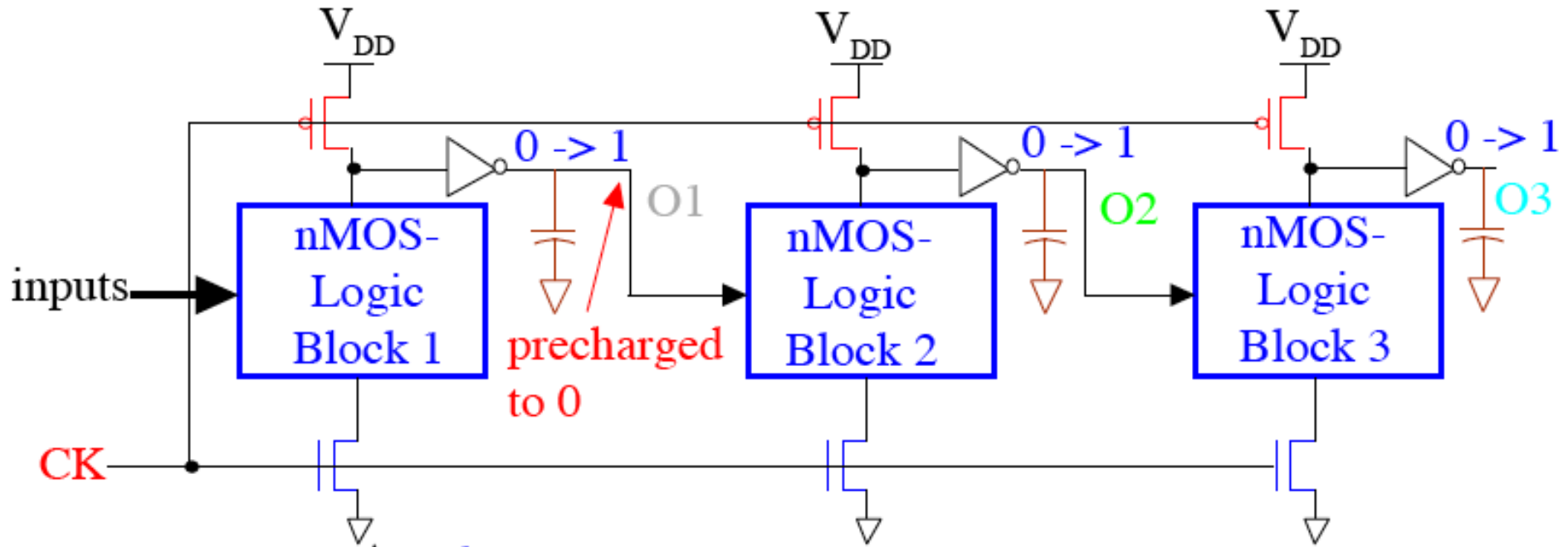


# Cascaded Domino CMOS Logic Gates

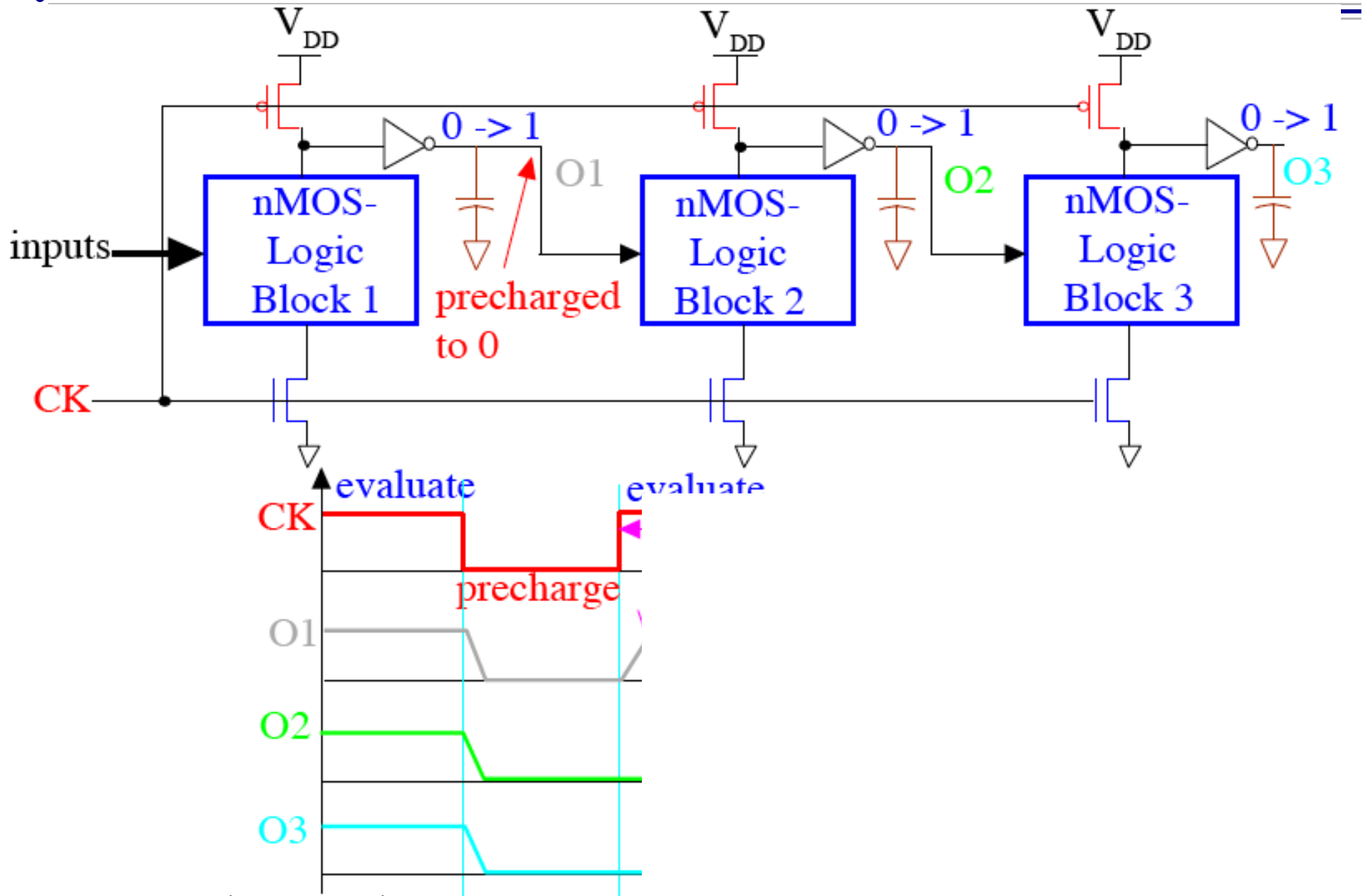




# Cascaded Domino CMOS Logic Gates

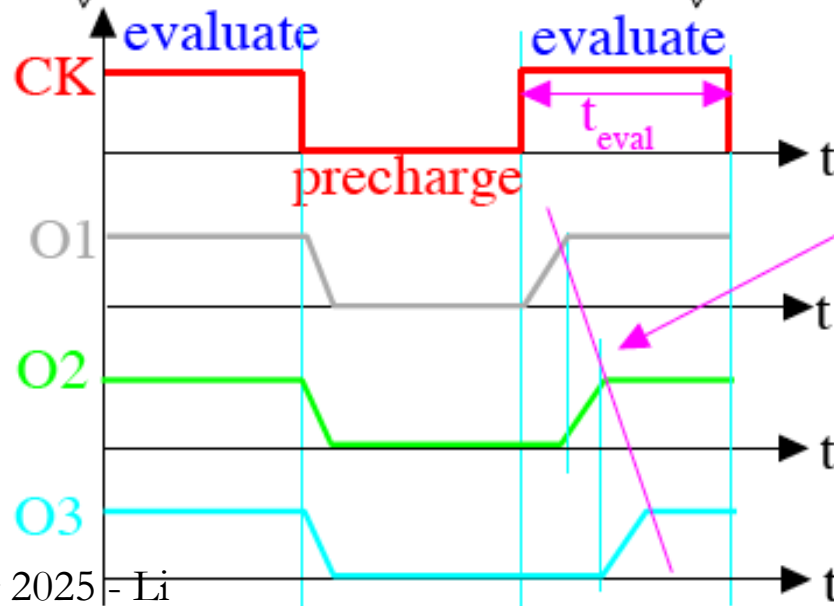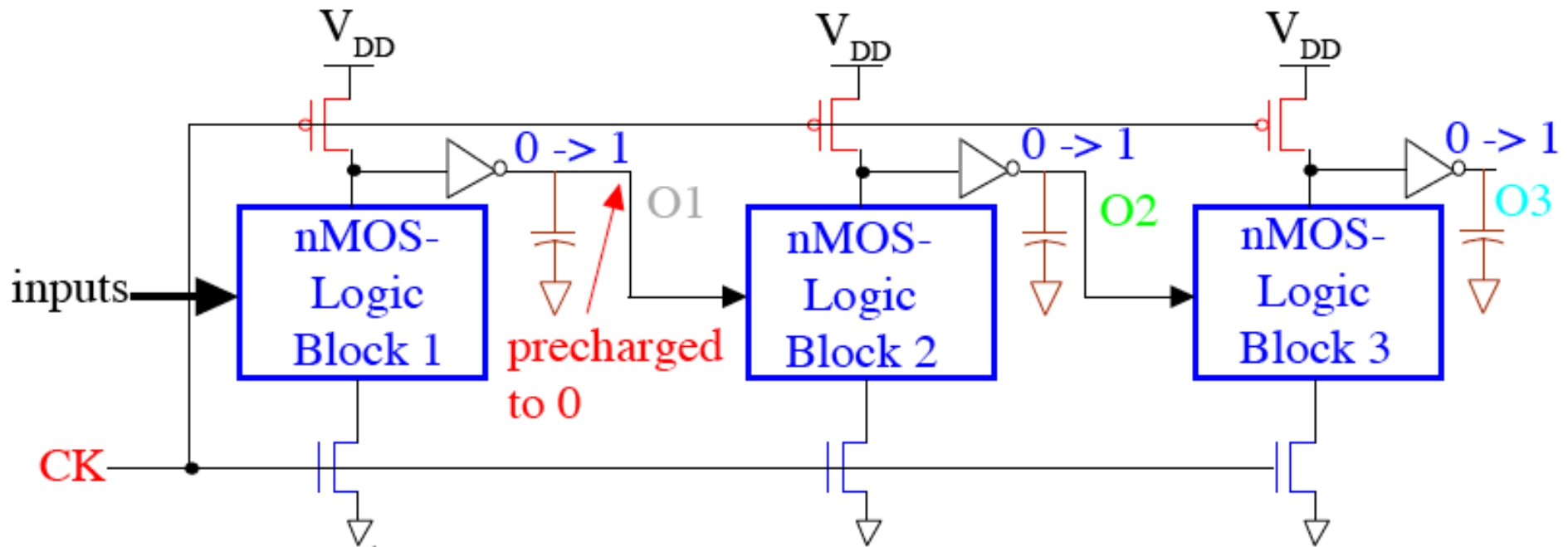

propagating gate decisions

Max # stages limited:  
total prop delay  $< t_{eval}$ .

# Domino or4 (Preclass 2)

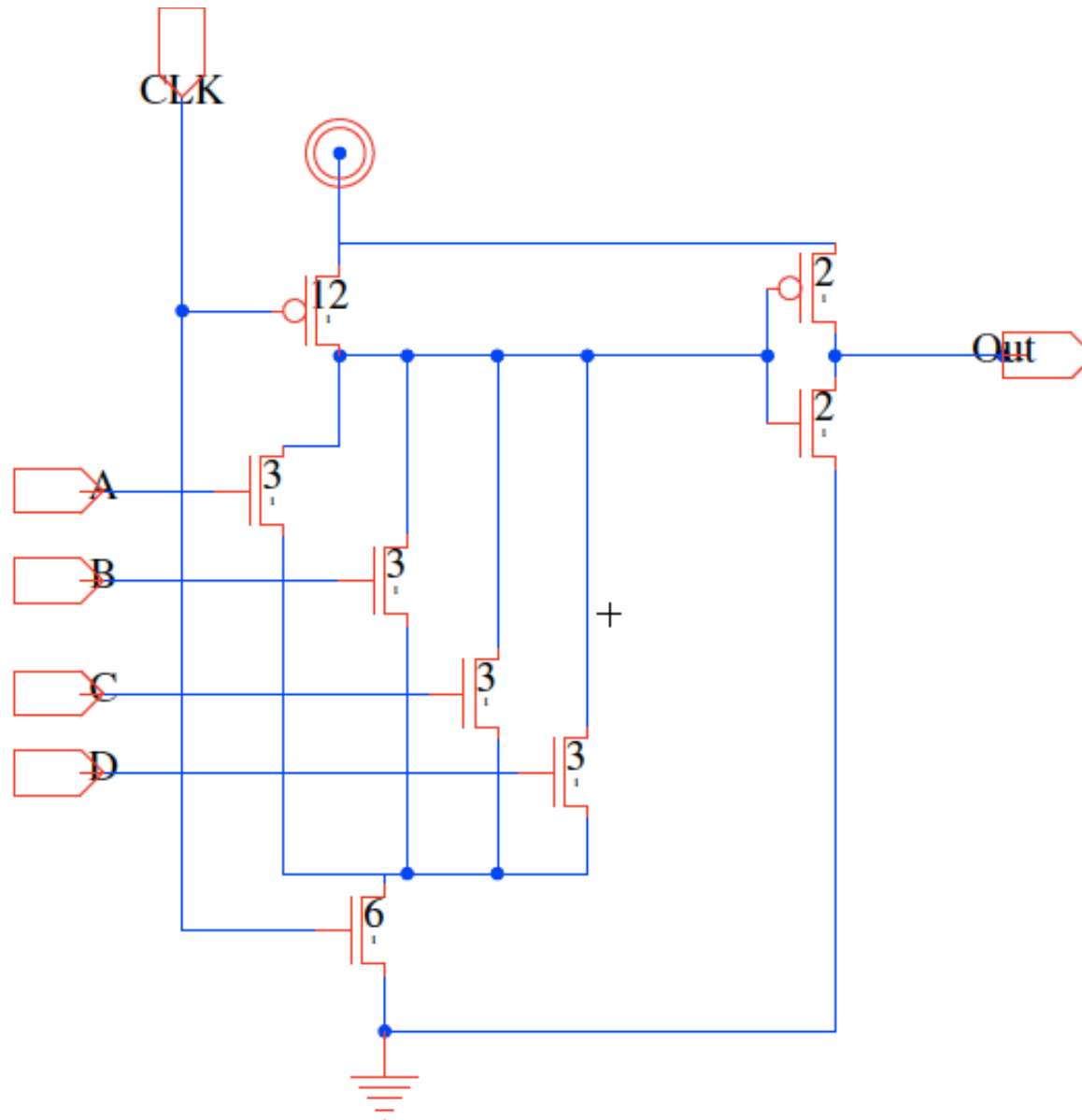


# Domino Logic (Preclass 2)

## □ Performance

- $R_0/2$  input


## □ Compare to CMOS cases?

- nor4
- or4
- nand4

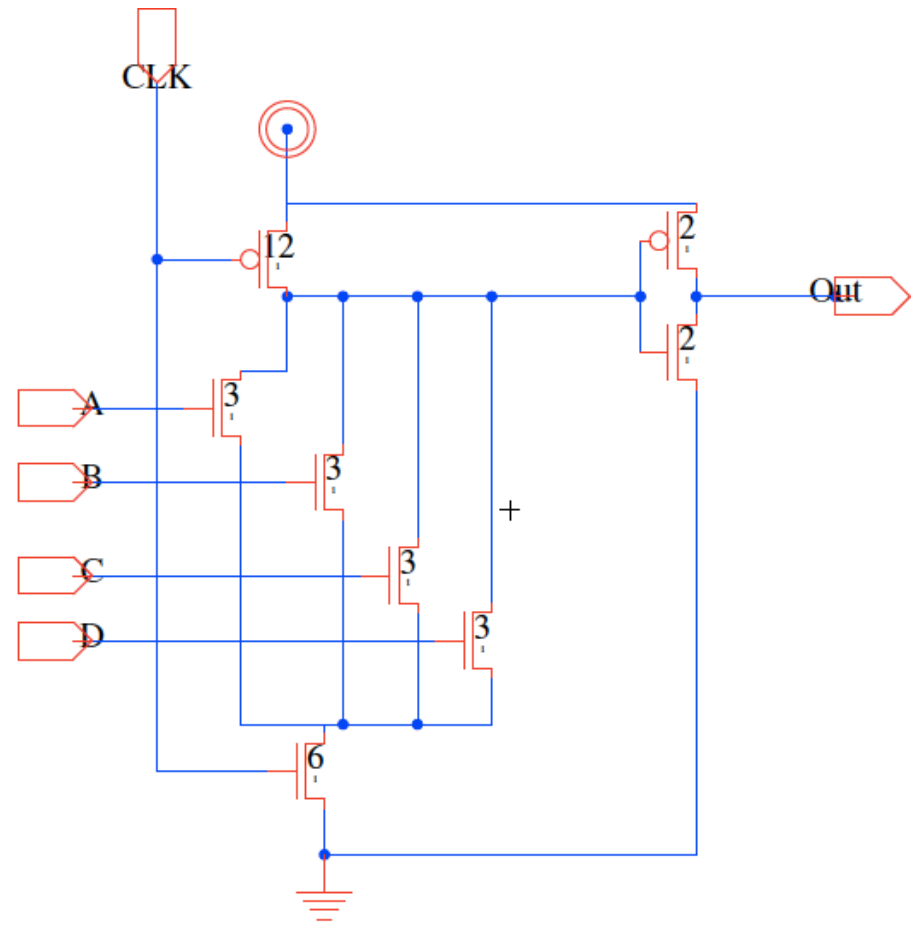

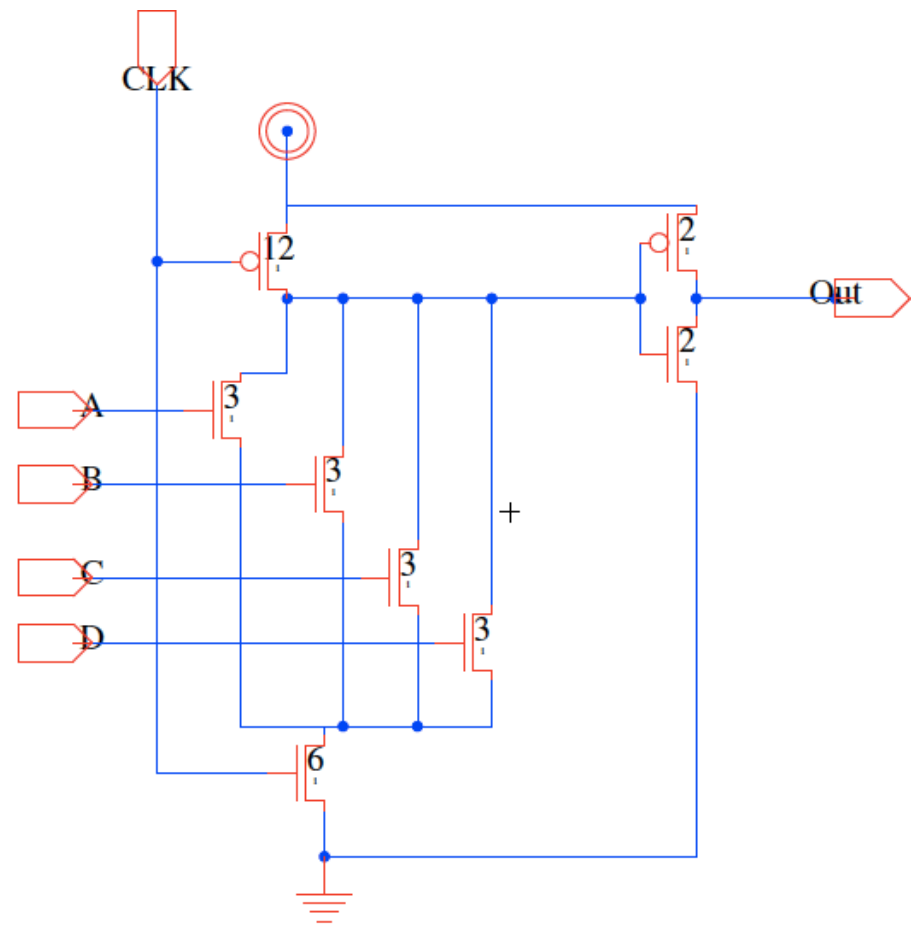
# Dynamic OR4 (Preclass 2)

- ❑ Precharge time?
- ❑ Driving input
  - With  $R_0/2$  inverter
- ❑ Driving inverter?
- ❑ Self output Delay?



 
# CMOS NOR4 (Preclass 2)

- Driving input
  - With  $R_0/2$  inverter
- Self output Delay?


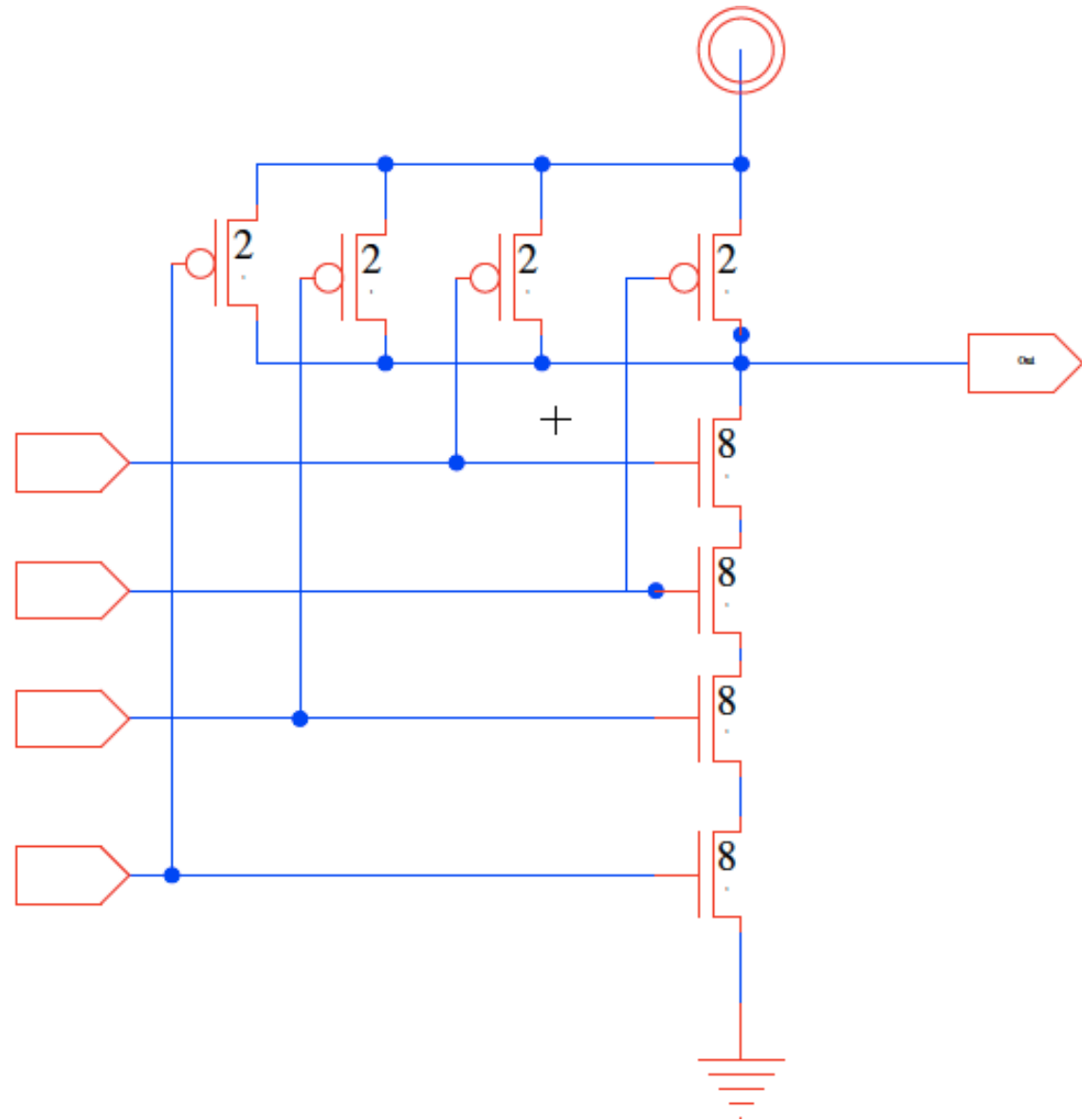
# CMOS NAND4 (Preclass 2)

- Driving input
  - With  $R_0/2$
- Driving self cap?





# Dynamic Logic Issues

---

- ❑ Noise sensitive
  - During evaluation phase, when output is high it's floating and therefore more susceptible to noise
- ❑ Power
  - Eliminates static current
  - Higher activity factor—always a  $0 \rightarrow 1$  transition, large pre-charge device dissipates extra switching power



# Observe

---

- ❑ Better (lower) ratio of input capacitance to drive strength
- ❑ Particularly good for
  - Driving large loads
  - Large fanin gates
- ❑ Harder to design with
  - Timing and polarity restrictions
  - Avoiding noise
    - Especially with today's high variation tech
- ❑ Can consume more energy





# Idea

---

- ❑ Clock discipline simplifies logic composition
  - Breaking logic up with registers allows circuit to run at high frequency
  - Abstracts many internal timing details
    - Setup/Hold time,  $\text{clk} \rightarrow \text{q}$  delay
  - Just concerned with making clock period long enough
- ❑ Dynamic/clocked logic
  - Only build/drive one pulldown network
    - Domino Logic
  - Fast transition propagation
  - Spend delay (capacitance) on pullup of critical path of logic
  - More complicated design, power dissipation
    - Reserve for when most needed



# Admin

---

- ❑ Homework 6
  - Due **Friday 4/11**
- ❑ Wednesday 4/16 Midterm 2
  - 1:45pm-3:45pm **in class**
  - **Midterm 2 Review session (4/16) - in class**
  - Lectures 11-18
  - Closed note, calculator allowed
  - All old exams online
    - 2015-2024
  - **Do review your preclass!!**



# Acknowledgement

---

- ❑ Prof. André DeHon (University of Pennsylvania)
- ❑ Prof. Tania Khanna (University of Pennsylvania)