

ESE 568: Mixed Signal Design and Modeling

Lec 5: September 17th, 2018
Basic 2-stage Opamp Design



Penn ESE 568 Fall 2018 - Khanna


Opamp



Penn ESE 568 Fall 2018 - Khanna

Ideal Opamp

- The ideal opamp characterized by seven properties
 - Knowledge of these properties is sufficient to design and analyze a large number of useful circuits
- Basic opamp properties
 - Infinite open-loop voltage gain
 - Infinite input impedance
 - Zero output impedance
 - Zero noise contribution
 - Zero DC output offset
 - Infinite bandwidth
 - Differential inputs that stick together
 - Zero input differential voltage


 


Penn ESE 568 Fall 2018 - Khanna


3

Opamp Practical Circuits

- Voltage comparator

  

- Voltage follower

 


Penn ESE 568 Fall 2018 - Khanna


4

Opamp Practical Circuits

- Integrating amplifier

 

- Differentiating amplifier

 


Penn ESE 568 Fall 2018 - Khanna

5

Opamp Design



Ideal Opamp

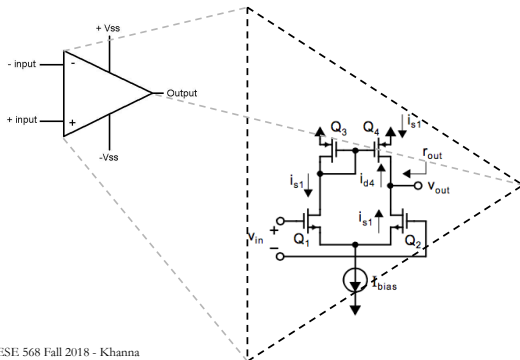

Penn ESE 568 Fall 2018 - Khanna

7

Steps in Designing a CMOS Opamp

- 1) Choosing or creating the basic structure of the opamp
 - This step results in a schematic showing the transistors and their interconnections
 - This diagram does not change throughout the remainder of the design unless the specifications cannot be met, then a new or modified structure must be developed
- 2) Selection of the dc currents and transistor sizes
 - a.k.a Biasing and sizing
 - Most of the effort of design is in this category
 - Simulators are used to aid the designer in this phase

Penn ESE 568 Fall 2018 - Khanna

8

Steps in Designing a CMOS Opamp

- 3) Physical implementation of the design
 - Layout of the transistors
 - Floorplanning the connections, pin-outs, power supply buses and grounds
 - Extraction of the physical parasitics and re-simulation
 - Verification that the layout is a physical representation of the circuit
- 4) Fabrication
- 5) Measurement
 - Verification of the specifications
 - Modification of the design as necessary
 - Make sure it's not necessary!

Penn ESE 568 Fall 2018 - Khanna

9

Design Variables

- Boundary conditions (constraints):
 - 1. Process specification (V_T , μ , C_{ox} , etc.)
 - 2. Supply voltage and range
 - 3. Supply current and range
 - 4. Operating temperature and range

Penn ESE 568 Fall 2018 - Khanna

10

Design Variables

- Specifications:
 - 1. Open-loop Gain
 - 2. Gain bandwidth
 - 3. Settling time
 - 4. Slew rate
 - 5. Input common-mode range, ICMR
 - 6. Common-mode rejection ratio, CMRR
 - 7. Power-supply rejection ratio, PSRR
 - 8. Output-voltage swing
 - 9. Output resistance
 - 10. Offset
 - 11. Noise
 - 12. Layout area

Penn ESE 568 Fall 2018 - Khanna

11

Specifications

- 1. Open-loop Gain
 - Typically an op-amp may have a maximal open-loop gain of around 10^5

$$A_{OL} = \frac{V_{out}}{V_{in}^+ - V_{in}^-}$$

Penn ESE 568 Fall 2018 - Khanna


12

Specifications

- 1. Open-loop Gain
 - Typically an op-amp may have a maximal open-loop gain of around 10^5

$$A_{OL} = \frac{V_{out}}{V_{in}^+ - V_{in}^-}$$


- 2. Gain bandwidth

 

Specifications


- 3. Settling time
- 4. Slew rate

$$SR = \max \left(\left| \frac{dy_{out}(t)}{dt} \right| \right)$$

 

Specifications

 - 5. Input common-mode range, ICMR
 - The input common-mode range is the range of common-mode voltages over which the differential amplifier continues to sense and amplify the difference signal with the same gain.
 - Typically, the ICMR is defined by the common-mode voltage range over which all MOSFETs remain in the saturation region.



Specifications

- 6. Common-mode rejection ratio, CMRR
 - CMRR is a measure of how well the differential amplifier rejects the common-mode input voltage in favor of the differential-input voltage.

$$CMRR = \frac{a_{vd}}{a_{vc}}$$

- 7. Power-supply rejection ratio, PSRR

$$PSRR_+ = \frac{a_{vd}}{a_+}$$

$$PSRR_- = \frac{a_{vd}}{a_-}$$

Specifications

- 8. Output-voltage swing
 - Expected output swing
- 9. Output resistance
 - Resistance seen into the output
- 10. Offset
 - Output offset voltage ($V_{OS(out)}$)
 - The output offset voltage is the voltage which appears at the output of the differential amplifier when the input terminals are connected together.


Specifications

- 8. Output-voltage swing
 - Expected output swing
- 9. Output resistance
 - Resistance seen into the output
- 10. Offset
 - Output offset voltage ($V_{OS(out)}$)
 - The output offset voltage is the voltage which appears at the output of the differential amplifier when the input terminals are connected together.
 - Input referred offset voltage ($V_{OS(in)} = V_{OS}$)
 - The input referred offset voltage is equal to the output offset voltage divided by the differential voltage gain.
 - $V_{OS} = V_{OS(out)}/A_{VD}$

Opamp Design Output

- 1) The topology
- 2) The dc currents
- 3) The W and L values of transistors
- 4) The values of components

- I.e Schematic and biasing

 

Penn ESE 568 Fall 2018 - Khanna

19

Opamp Design Practical Advice

- 1) Decide upon a suitable topology
 - The topology should be the one capable of meeting most of the specifications
 - Try to avoid "inventing" a new topology but start with an existing topology
- 2) Determine the type of compensation needed to meet the specifications
 - Consider the load and stability requirements
 - Use some form of Miller compensation or a self-compensated approach
- 3) Design dc currents and device sizes for proper dc, ac, and transient performance
 - This begins with hand calculations based upon approximate design equations.
 - Compensation components are also sized in this step of the procedure.
 - After each device is sized by hand, a circuit simulator is used to fine tune the design

Penn ESE 568 Fall 2018 - Khanna

20

Opamp Design Practical Advice

- Two basic steps of design:
 - 1) "First-cut" - this step is to use hand calculations to propose a design that has potential of satisfying the specifications. Design robustness is developed in this step.
 - 2) Optimization - this step uses the computer to refine and optimize the design.


Penn ESE 568 Fall 2018 - Khanna

21

Basic 2-stage Opamp




2-Stage Opamp

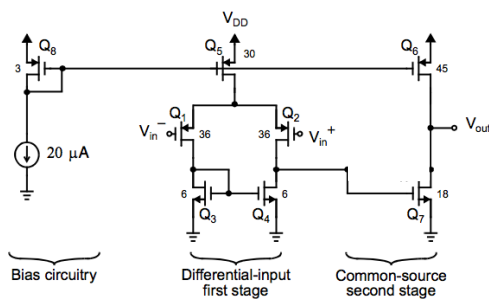

Penn ESE 568 Fall 2018 - Khanna

23

2-Stage Opamp

 

Penn ESE 568 Fall 2018 - Khanna

24


Design Variables

- Specifications:
 - 1. Open-loop Gain
 - 2. Gain bandwidth
 - 3. Settling time
 - 4. Slew rate
 - 5. Input common-mode range, ICMR
 - 6. Common-mode rejection ratio, CMRR
 - 7. Power-supply rejection ratio, PSRR
 - 8. Output-voltage swing
 - 9. Output resistance
 - 10. Offset
 - 11. Noise
 - 12. Layout area


Basic 2-stage Opamp



2-Stage Opamp

 


Differential DC Gain

 

- Inputs are equal in magnitude but opposite in sign to each other
- By linearity and symmetry, i_{s1} must equal $-i_{s2}$
 - This implies i_R is zero, so that voltage drop across r_{o4} is zero
 - The sources of M_1 and M_2 are therefore at incremental ground and decoupled from each other!

2-Stage Opamp

- 1. Open-loop Gain

 


$$A_{v1} = -g_{m1}(r_{ds2} \parallel r_{ds4})$$

$$A_{v2} = -g_{m7}(r_{ds6} \parallel r_{ds7})$$


2-Stage Opamp

- 2. Frequency Response

 

2-Stage Opamp

 - 2a. Frequency Response – no compensation $C_C=0$




- Two poles:

$$p_1 = -\frac{1}{R_{o1}C_1} \quad p_2 = -\frac{1}{R_{o2}C_2}$$

2-Stage Opamp

 
- 2a. Frequency Response – no compensation $C_C=0$




$$p_1 = -\frac{1}{R_{o1}C_1} \quad p_2 = -\frac{1}{R_{o2}C_2}$$

$$A(s) = \frac{A_0}{\left(1 - \frac{s}{p_1}\right)\left(1 - \frac{s}{p_2}\right)}$$

2-Stage Opamp Transfer Functions

 


2-Stage Opamp Transfer Functions

 

Phase Margin

 - Find phase at unity-gain frequency (ω_0)
- Add 180° for phase margin
- Red
 - Phase at $\omega_0 = -81.3^\circ$
 - PM = 98.7°
- Blue
 - Phase at $\omega_0 = -231^\circ$
 - PM = -50°



Stability


 


Fig. 6.11(a) Typical transient responses of systems

Stability vs. Phase Margin



2nd Order Transient Curves

 


From Dorf, Richard C. Modern Control Systems, Addison-Wesley Publishing Company, Reading, Massachusetts, Third Edition, 1981. TEXAS INSTRUMENTS

Phase Margin

  - Find phase at unity-gain frequency (ω_0)
- Add 180° for phase margin
- Want phase margin $>45^\circ$ ($\sim 60^\circ$)
 - Problem: Hard to do with 2-stage opamp with high gain
 - Solution: Split the poles



 
Impact of Pole Splitting with Compensation Cap



- Pole splitting allows the dominant pole frequency to be dramatically decreased and the main parasitic pole to be dramatically increased
 - We can achieve higher unity gain frequency with improved phase margin

2-Stage Opamp

 - 2b. Frequency Response – with compensation $C_C > 0$




- Two poles:

$$p_1 \approx -\frac{1}{R_{o1}(g_{m1}R_{o2}C_C)}$$

$$p_2 \approx -\frac{g_{m2}C_C}{C_1C_2 + C_1C_C + C_C C_2} \approx -\frac{g_{m2}}{C_2}$$


2-Stage Opamp

 - 2b. Frequency Response – with compensation $C_C > 0$




Nulling Resistor

 - $$z_1 = \frac{1}{C_C \left(\frac{1}{G_{m2}} - R_Z \right)}$$
 - If $R_Z = \frac{1}{G_{m2}}$, zero cancelled
 - If $R_Z > \frac{1}{G_{m2}}$, zero moves to left half-plane \Rightarrow improving phase margin



Transistor for R_Z

 


Penn ESE 568 Fall 2018 - Khanna

43

2-Stage Opamp – Unity Gain Freq

- Equivalent capacitance at node v_1

 


Penn ESE 568 Fall 2018 - Khanna

44

2-Stage Opamp – Unity Gain Freq

 - Equivalent capacitance at node v_1 : $C_{eq} = C_C(1 + A_{v2}) \approx C_C A_{v2}$




Penn ESE 568 Fall 2018 - Khanna

45

2-Stage Opamp – Unity Gain Freq

 - Equivalent capacitance at node v_1 : $C_{eq} = C_C(1 + A_{v2}) \approx C_C A_{v2}$




$$|A_v(j\omega_0)| = 1 \text{ for } \omega_0 = \frac{g_{m1}}{C_C}$$

Penn ESE 568 Fall 2018 - Khanna

46

2-Stage Opamp


- 3/4. Settling Time/Slew Rate

 

Penn ESE 568 Fall 2018 - Khanna

47

2-Stage Opamp – Slew Rate

 


Penn ESE 568 Fall 2018 - Khanna

48

2-Stage Opamp

- 3/4. Settling Time/Slew Rate

 


Penn ESE 568 Fall 2018 - Khanna

49

2-Stage Opamp

- 3/4. Settling Time/Slew Rate

 


$$SR = \left. \frac{dv_{out}}{dt} \right|_{max} = \frac{I_{C1} |_{max}}{C_C} = \frac{I_{D5}}{C_C}$$

Penn ESE 568 Fall 2018 - Khanna

50


Finite Slew Rate Effect

- Ex. Unity-gain Follower

 

$$v_i = A \sin(\omega t)$$

$$\left. \frac{dv_o}{dt} \right|_{MAX} = A\omega$$

 


If slew rate < ωA : large signal distortion results

Penn ESE 568 Fall 2018 - Khanna

51

2-Stage Opamp

- 3/4. Settling Time/Slew Rate

 

$$SR = \left. \frac{dv_{out}}{dt} \right|_{max} = \frac{I_{C1} |_{max}}{C_C} = \frac{I_{D5}}{C_C}$$

$$\omega_0 = \frac{g_{m1}}{C_C}$$

Penn ESE 568 Fall 2018 - Khanna

52

Unity Gain Freq and Slew Rate

- Relationship between unity gain frequency and slew rate:

$$\omega_0 = \frac{g_{m1}}{C_C} \quad SR = \frac{I_{D5}}{C_C} \quad \rightarrow \quad SR = \frac{I_{D5}}{g_{m1}} \omega_0$$

- For 45° phase margin: $\omega_0 = |p_2|$

$$SR = \frac{I_{D5}}{g_{m1}} |p_2|$$

Penn ESE 568 Fall 2018 - Khanna

53

Unity Gain Freq and Slew Rate

- Relationship between unity gain frequency and slew rate:

$$\omega_0 = \frac{g_{m1}}{C_C} \quad SR = \frac{I_{D5}}{C_C} \quad \rightarrow \quad SR = \frac{I_{D5}}{g_{m1}} \omega_0$$

- For 45° phase margin: $\omega_0 = |p_2|$

$$SR = \frac{I_{D5}}{g_{m1}} |p_2|$$

$$p_2 = -\frac{g_{m7} C_C}{C_1 C_2 + C_1 C_C + C_2 C_C} = -\frac{g_{m7}}{C_2}$$

Penn ESE 568 Fall 2018 - Khanna

54

Design Variables

- Specifications:
 - 1. Open-loop Gain
 - 2. Gain bandwidth
 - 3. Settling time
 - 4. Slew rate
 - 5. Input common-mode range, ICMR
 - 6. Common-mode rejection ratio, CMRR
 - 7. Power-supply rejection ratio, PSRR
 - 8. Output-voltage swing
 - 9. Output resistance
 - 10. Offset
 - 11. Noise
 - 12. Layout area

Admin

- HW 2 and 3 due Su
 - Want to make sure every has Cadence set up and running