

ESE 570: Digital Integrated Circuits and VLSI Fundamentals


Lec 10: February 14, 2017
MOS Inverter: Dynamic Characteristics




Lecture Outline

- Review: Symmetric CMOS Inverter Design
- Inverter Power
- Dynamic Characteristics
 - Delay

Review: CMOS Inverter: Visual VTC

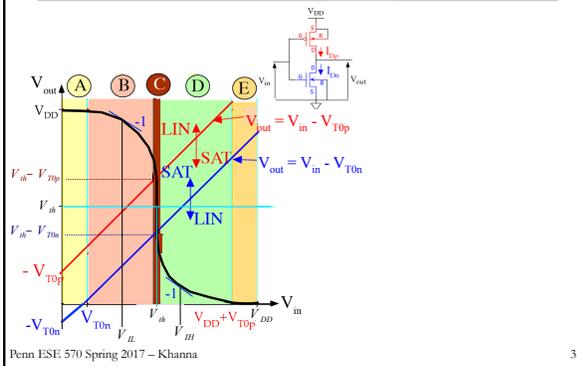

Review: CMOS Inverter: Visual VTC

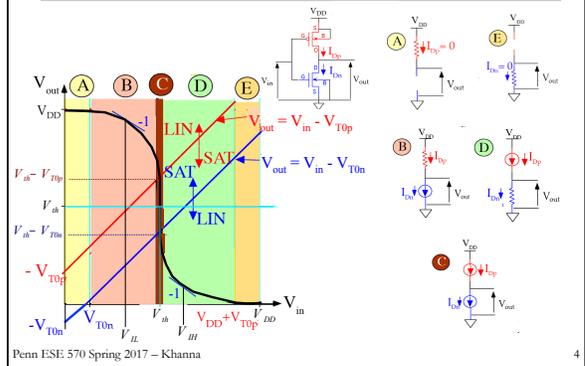

Review: CMOS Inverter: Design/Sizing

$$V_{th} = \frac{V_{T0n} + \sqrt{\frac{1}{k_R} (V_{DD} + V_{T0p})}}{1 + \sqrt{\frac{1}{k_R}}} \rightarrow k_R = \left(\frac{V_{DD} + V_{T0p} - V_{th}}{V_{th} - V_{T0n}} \right)^2$$

Important design Eq. for CMOS inverter VTC.

If \$V_{th}\$ is set to ideal case: \$V_{th} = \frac{1}{2} V_{DD}\$

$$k_R = \left(\frac{V_{DD} + V_{T0p} - 1/2 V_{DD}}{1/2 V_{DD} - V_{T0n}} \right)^2 = \left(\frac{1/2 V_{DD} + V_{T0p}}{1/2 V_{DD} - V_{T0n}} \right)^2$$

If \$V_{T0n} = -V_{T0p} = -V_{T0}\$ (symmetric CMOS)

$$k_R = \left(\frac{V_{DD} + V_{T0p} - 1/2 V_{DD}}{1/2 V_{DD} - V_{T0n}} \right)^2 = \left(\frac{1/2 V_{DD} + V_{T0}}{1/2 V_{DD} + V_{T0}} \right)^2 = 1 \rightarrow 1 = \frac{\mu_n W_n}{\mu_p W_p} \rightarrow \frac{W_p}{W_n} = \frac{\mu_n}{\mu_p}$$

Review: Noise Margin Example

Compute the noise margins for a symmetric CMOS inverter has been designed to achieve \$V_{th} = V_{DD}/2\$, where \$V_{DD} = 5\$ V and \$V_{T0n} = -V_{T0p} = 1\$ V.

$$NM_H = V_{OH} - V_{IH} \quad V_{IL} = \frac{1}{8} (3 V_{DD} + 2 V_{T0})$$

$$NM_L = V_{IL} - V_{OL} \quad V_{IH} = \frac{1}{8} (5 V_{DD} - 2 V_{T0})$$

$$NM_H = NM_L = 2.125$$

RECALL (with \$V_{DD} = 5\$ V)

1. Preferred Design => \$NM_H, NM_L > V_{DD}/4 = 1.25\$ V
2. Ideal NM => \$NM_H = NM_L = 2.5\$ V > \$V_{DD}/2\$

Inverter Power




Power

□ $P = I \times V$


□ Tricky part:

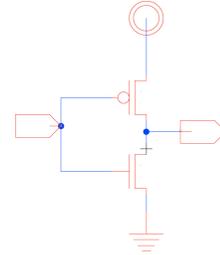- Understanding I
- (pairing with correct V)




Static Current

□ $P = I_{static} \times V_{DD}$

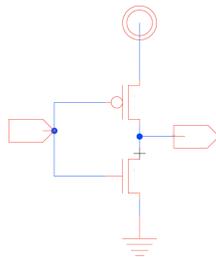

Switching Currents

□ Dynamic current flow:

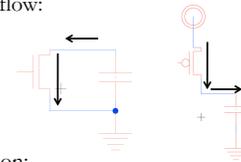


□ If both transistor on:

- Current path from V_{dd} to Gnd
- Short circuit current




Currents Summary

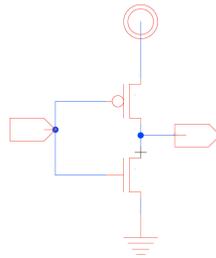- I changes over time
- At least two components
 - I_{static} – no switching
 - I_{switch} – when switching
 - I_{dyn} and I_{sc}



Currents Summary

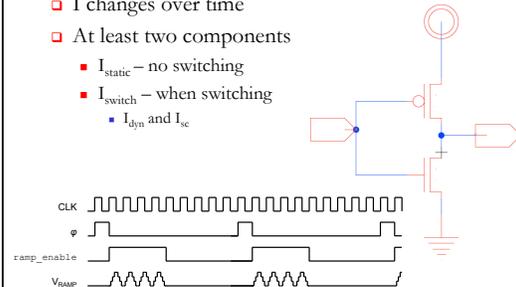- I changes over time
- At least two components
 - I_{static} – no switching
 - I_{switch} – when switching
 - I_{dyn} and I_{sc}



Switching


Dynamic Power



Switching Currents

$$\square I_{total}(t) = I_{static}(t) + I_{switch}(t)$$
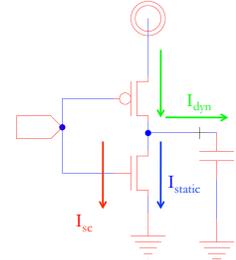
$$\square I_{switch}(t) = I_{sc}(t) + I_{dyn}(t)$$




Charging

$\square I_{dyn}(t)$ – why is it changing?


- $\square I_{ds} = f(V_{ds}, V_{gs})$
- \square and V_{gs} , V_{ds} changing

$$I_{DS} \approx v_{sat} C_{OX} W \left(V_{GS} - V_T - \frac{V_{DSAT}}{2} \right)$$
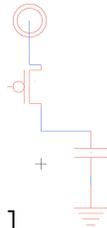
$$I_{DS} = \mu_n C_{OX} \left(\frac{W}{L} \right) \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$



Switching Energy – focus on $I_{dyn}(t)$

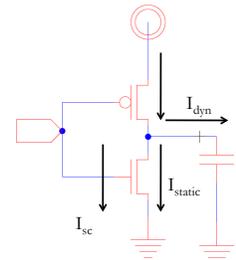


Switching Energy – focus on $I_{dyn}(t)$

$$E = \int P(t) dt$$

$$= \int I(t) V_{dd} dt$$

$$= V_{dd} \int I(t) dt$$

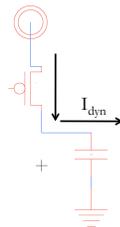

Switching Energy


\square Do we know what this is?

$$\int I_{dyn}(t) dt$$

$$E = \int P(t) dt$$

$$= \int I(t) V_{dd} dt$$

$$= V_{dd} \int I(t) dt$$

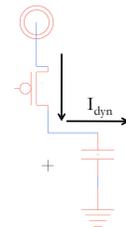


Switching Energy

- Do we know what this is?

$$Q = \int I_{dyn}(t) dt$$

$$E = \int P(t) dt$$

$$= \int I(t) V_{dd} dt$$
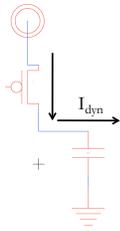
$$= V_{dd} \int I(t) dt$$


Penn ESE 570 Spring 2017 - Khanna 19


Switching Energy

- Do we know what this is?
- What is Q?

$$Q = \int I_{dyn}(t) dt$$

$$E = \int P(t) dt$$

$$= \int I(t) V_{dd} dt$$
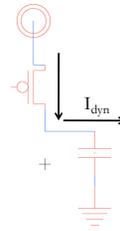
$$= V_{dd} \int I(t) dt$$


Penn ESE 570 Spring 2017 - Khanna 20

Switching Energy


- Do we know what this is?
- What is Q?

$$Q = \int I_{dyn}(t) dt$$

$$E = \int P(t) dt$$

$$= \int I(t) V_{dd} dt$$

$$= V_{dd} \int I(t) dt$$
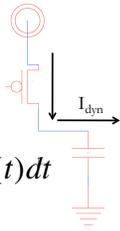
$$Q = CV = \int I(t) dt$$


Penn ESE 570 Spring 2017 - Khanna 21

Switching Energy

- Do we know what this is?
- What is Q?

$$Q = \int I_{dyn}(t) dt$$

$$E = \int P(t) dt$$


$$= \int I(t) V_{dd} dt$$

$$= V_{dd} \int I(t) dt$$

$$Q = CV = \int I(t) dt$$

$$E = CV^2_{dd}$$

Capacitor charging energy

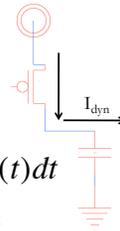

Penn ESE 570 Spring 2017 - Khanna 22

Switching Power

- Every time output switches 0→1 pay:
 - E = CV²
- P_{dyn} = (# 0→1 trans) × CV² / time
- # 0→1 trans = 1/2 # of transitions
- P_{dyn} = (# trans) × 1/2 CV² / time

Penn ESE 570 Spring 2017 - Khanna 23

Switching


Short Circuit Power



Penn ESE 570 Spring 2017 - Khanna 24

Short Circuit Power

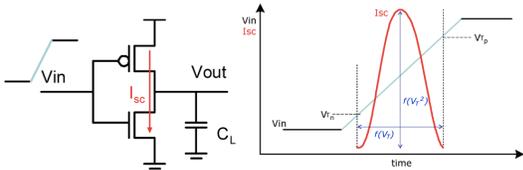- Between V_{TN} and $V_{dd} - V_{TP}$
 - Both N and P devices conducting




Penn ESE 570 Spring 2017 - Khanna

25

Short Circuit Power

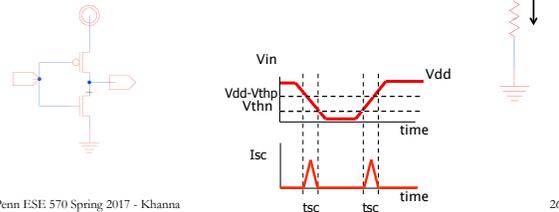- Between V_{TN} and $V_{dd} - V_{TP}$
 - Both N and P devices conducting
- Roughly:





Penn ESE 570 Spring 2017 - Khanna

26

Peak Current

- I_{peak} around $V_{dd}/2$
 - If $|V_{TN}| = |V_{TP}|$ and sized equal rise/Spring
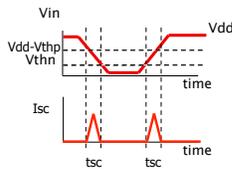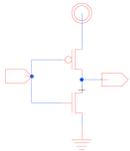
$$I_{DS} \approx v_{sat} C_{OX} W \left(V_{GS} - V_T - \frac{V_{DSAT}}{2} \right)$$



Penn ESE 570 Spring 2017 - Khanna



27

Peak Current

- I_{peak} around $V_{dd}/2$
 - If $|V_{TN}| = |V_{TP}|$ and sized equal rise/Spring

$$I_{DS} \approx v_{sat} C_{OX} W \left(V_{GS} - V_T - \frac{V_{DSAT}}{2} \right)$$
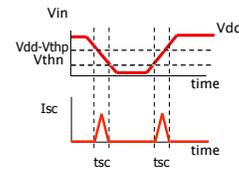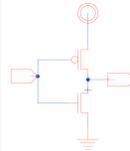
$$\int I(t) dt \approx I_{peak} \times t_{sc} \times \left(\frac{1}{2} \right)$$



Penn ESE 570 Spring 2017 - Khanna

28



Peak Current

- I_{peak} around $V_{dd}/2$
 - If $|V_{TN}| = |V_{TP}|$ and sized equal rise/Spring

$$I_{DS} \approx v_{sat} C_{OX} W \left(V_{GS} - V_T - \frac{V_{DSAT}}{2} \right)$$

$$\int I(t) dt \approx I_{peak} \times t_{sc} \times \left(\frac{1}{2} \right)$$
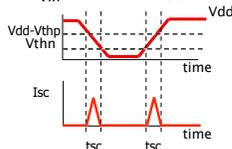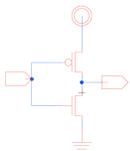
$$E = V_{in} \times I_{peak} \times t_{sc} \times \left(\frac{1}{2} \right)$$



Penn ESE 570 Spring 2017 - Khanna

29

Short Circuit Energy

- Make it look like a capacitance, C_{SC}
 - $Q = I \times t$
 - $Q = CV$

$$E = V_{dd} \times \left(I_{peak} \times t_{sc} \times \left(\frac{1}{2} \right) \right)$$

$$E = V_{dd} \times Q_{SC}$$

$$E = V_{dd} \times (C_{SC} V_{dd}) = C_{SC} V_{dd}^2$$

Penn ESE 570 Spring 2017 - Khanna

30

Short Circuit Energy

- Every time switch ($0 \rightarrow 1$ and $1 \rightarrow 0$)
 - Also dissipate short-circuit energy: $E = CV^2$
 - Different $C = C_{sc}$
 - C_{cs} "fake" capacitance (for accounting)


Dynamic Characteristics




Inverter Delay

- Caused by charging and discharging the capacitive load
 - What is the load?


Inverter Delay

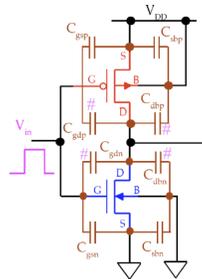

Inverter Delay

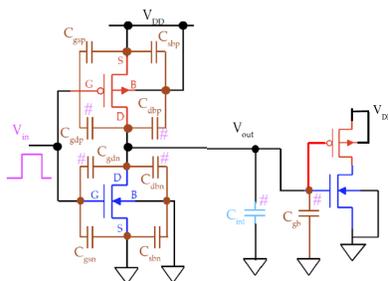

Inverter Delay

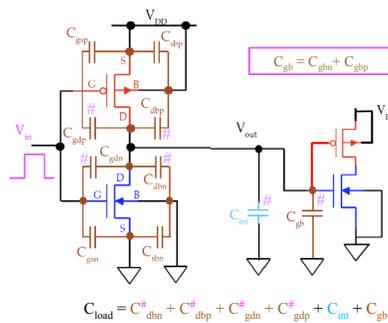

Inverter Delay

Usually
 $C_{db} \gg C_{gd}$
 $C_{sb} \gg C_{gs}$

$$C_{load} \approx C_{dbn} + C_{dbp} + C_{int} + C_{gb}$$





Penn ESE 570 Spring 2017 – Khanna 37

Inverter Delay

$n = \text{fan-out} \geq 1$

$$C_{load} \approx C_{dbn} + C_{dbp} + C_{int} + nC_{gb}$$

Penn ESE 570 Spring 2017 – Khanna 38

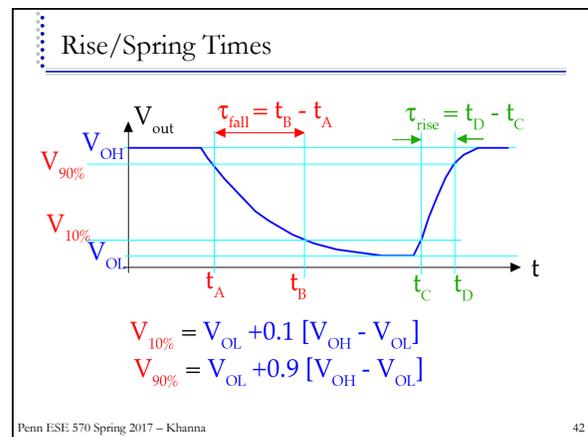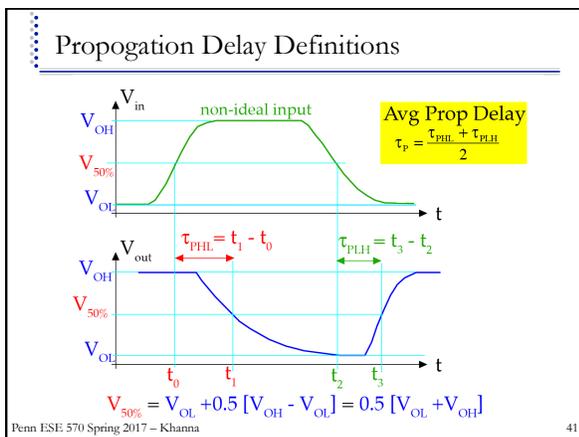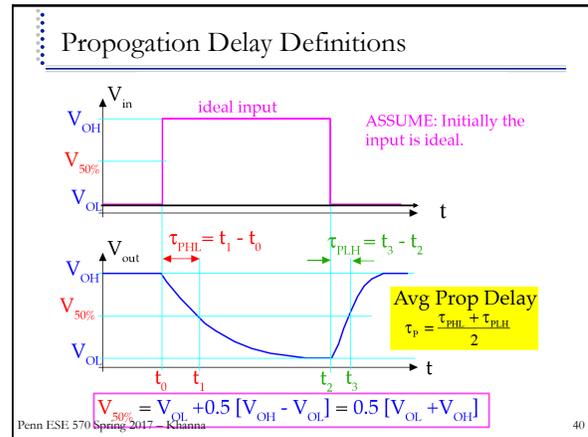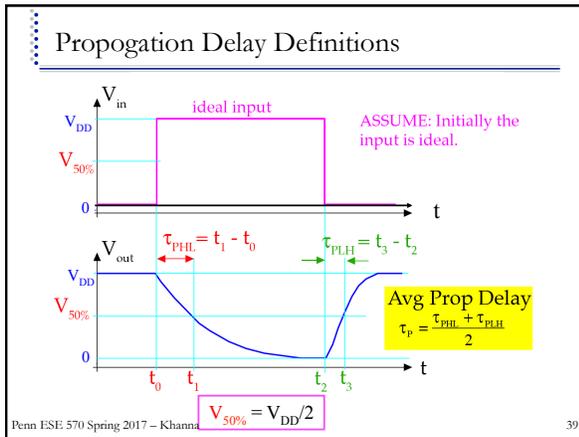

MOS Inverter Dynamic Performance


- ANALYSIS (OR SIMULATION): For a given MOS inverter schematic and C_{load} , estimate (or measure) the propagation delays
- DESIGN: For given specs for the propagation delays and C_{load} , determine the MOS inverter schematic

METHODS:

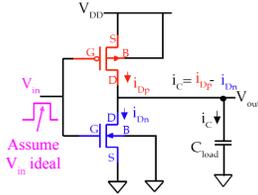1. Average Current Model

$$\tau_{PHL} = C_{load} \frac{\Delta V_{HL}}{I_{avg,HL}} = C_{load} \frac{V_{OH} - V_{50\%}}{I_{avg,HL}}$$

$$\tau_{PLH} = C_{load} \frac{\Delta V_{LH}}{I_{avg,LH}} = C_{load} \frac{V_{50\%} - V_{OL}}{I_{avg,LH}}$$



MOS Inverter Dynamic Performance


- ANALYSIS (OR SIMULATION): For a given MOS inverter schematic and C_{load} , estimate (or measure) the propagation delays
- DESIGN: For given specs for the propagation delays and C_{load} , determine the MOS inverter schematic

METHODS:

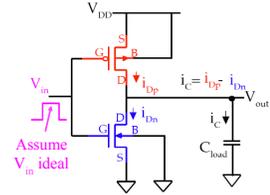2. Differential Equation Model

$$i_C = C_{load} \frac{dV_{out}}{dt} \Rightarrow \int dt = C_{load} \int \frac{dV_{out}}{i_C}$$

$$dt = \tau_{PHL} \text{ or } \tau_{PLH}$$



MOS Inverter Dynamic Performance


- ANALYSIS (OR SIMULATION): For a given MOS inverter schematic and C_{load} , estimate (or measure) the propagation delays
- DESIGN: For given specs for the propagation delays and C_{load} , determine the MOS inverter schematic

METHODS:

3. 1st Order RC delay Model

$$\tau_{PHL} \approx 0.69 \cdot C_{load} \cdot R_n$$

$$\tau_{PLH} \approx 0.69 \cdot C_{load} \cdot R_p$$

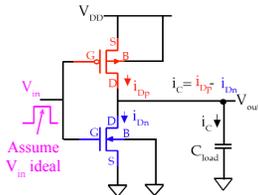

Method 1


Average Current Model



Calculation of Propagation Delays

$$\tau_{PHL} = C_{load} \frac{\Delta V_{HL}}{I_{avg,HL}} = C_{load} \frac{V_{OH} - V_{50\%}}{I_{avg,HL}}$$

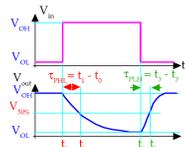
$$\tau_{PLH} = C_{load} \frac{\Delta V_{LH}}{I_{avg,LH}} = C_{load} \frac{V_{50\%} - V_{OL}}{I_{avg,LH}}$$



Calculation of Propagation Delays

$$\tau_{PHL} = C_{load} \frac{\Delta V_{HL}}{I_{avg,HL}} = C_{load} \frac{V_{OH} - V_{50\%}}{I_{avg,HL}}$$
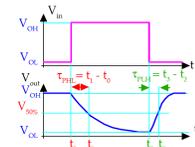
$$\tau_{PLH} = C_{load} \frac{\Delta V_{LH}}{I_{avg,LH}} = C_{load} \frac{V_{50\%} - V_{OL}}{I_{avg,LH}}$$




$I_{avg,HL}$ -> approximate average C_{load} current during high-to-low V_{out} transition

$$I_{avg,HL} = \frac{1}{2} [i_C(V_{in} = V_{OH}, V_{out} = V_{OH}) + i_C(V_{in} = V_{OH}, V_{out} = V_{50\%})]$$

Calculation of Propagation Delays

$$\tau_{PHL} = C_{load} \frac{\Delta V_{out}}{I_{avg,HL}} = C_{load} \frac{V_{OH} - V_{50\%}}{I_{avg,HL}}$$
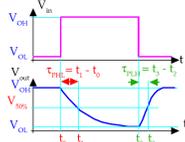
$$\tau_{PLH} = C_{load} \frac{\Delta V_{out}}{I_{avg,LH}} = C_{load} \frac{V_{50\%} - V_{OL}}{I_{avg,LH}}$$



$I_{avg,HL}$ -> approximate average C_{load} current during high-to-low V_{out} transition

$$I_{avg,HL} = \frac{1}{2} [i_C(V_{in} = V_{OH}, V_{out} = V_{OH}) + i_C(V_{in} = V_{OH}, V_{out} = V_{50\%})]$$


$I_{avg,LH}$ -> approximate average C_{load} current during low-to-high V_{out} transition

$$I_{avg,LH} = \frac{1}{2} [i_C(V_{in} = V_{OL}, V_{out} = V_{OL}) + i_C(V_{in} = V_{OL}, V_{out} = V_{50\%})]$$

Calculation of Rise/Spring Times

$$\tau_{fall} = C_{load} \frac{\Delta V_{out}}{I_{avg,90\%-10\%}} = C_{load} \frac{V_{90\%} - V_{10\%}}{I_{avg,90\%-10\%}}$$

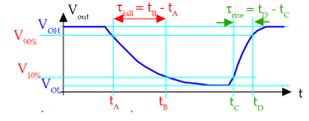
$$\tau_{rise} = C_{load} \frac{\Delta V_{out}}{I_{avg,10\%-90\%}} = C_{load} \frac{V_{90\%} - V_{10\%}}{I_{avg,10\%-90\%}}$$



Calculation of Rise/Spring Times

$$\tau_{fall} = C_{load} \frac{\Delta V_{out}}{I_{avg,90\%-10\%}} = C_{load} \frac{V_{90\%} - V_{10\%}}{I_{avg,90\%-10\%}}$$
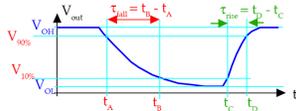
$$\tau_{rise} = C_{load} \frac{\Delta V_{out}}{I_{avg,10\%-90\%}} = C_{load} \frac{V_{90\%} - V_{10\%}}{I_{avg,10\%-90\%}}$$




$I_{avg,90\%-10\%}$ -> approximate average C_{load} current during 90%-to-10% V_{out} transition

$$I_{avg,90\%-10\%} = \frac{1}{2} [i_C(V_{in} = V_{OH}, V_{out} = V_{90\%}) + i_C(V_{in} = V_{OH}, V_{out} = V_{10\%})]$$

Calculation of Rise/Spring Times

$$\tau_{fall} = C_{load} \frac{\Delta V_{out}}{I_{avg,90\%-10\%}} = C_{load} \frac{V_{90\%} - V_{10\%}}{I_{avg,90\%-10\%}}$$
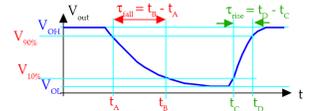
$$\tau_{rise} = C_{load} \frac{\Delta V_{out}}{I_{avg,10\%-90\%}} = C_{load} \frac{V_{90\%} - V_{10\%}}{I_{avg,10\%-90\%}}$$



$I_{avg,90\%-10\%}$ -> approximate average C_{load} current during 90%-to-10% V_{out} transition

$$I_{avg,90\%-10\%} = \frac{1}{2} [i_C(V_{in} = V_{OH}, V_{out} = V_{90\%}) + i_C(V_{in} = V_{OH}, V_{out} = V_{10\%})]$$

$I_{avg,10\%-90\%}$ -> approximate average C_{load} current during 10%-to-90% V_{out} transition

$$I_{avg,10\%-90\%} = \frac{1}{2} [i_C(V_{in} = V_{OL}, V_{out} = V_{10\%}) + i_C(V_{in} = V_{OL}, V_{out} = V_{90\%})]$$


Method 2

Differential Equation Model



Calculating Propagation Delays

Assume V_{in} is an ideal step-input

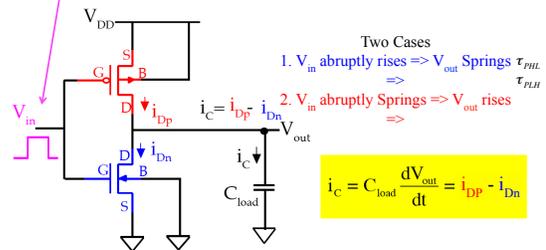

Case 1: V_{in} Abruptly Rises - τ_{PHL}


Penn ESE 570 Spring 2017 - Khanna

55

Case 1: V_{in} Abruptly Rises - τ_{PHL}

Penn ESE 570 Spring 2017 - Khanna


56

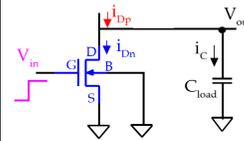

Case 1: V_{in} Abruptly Rises - τ_{PHL}

IC: $V_{out} = V_{DD}, V_{in} = 0 \rightarrow V_{DD}$

nMOS - ON
p-MOS OFF

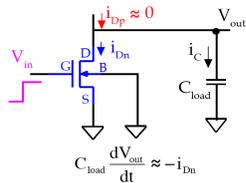


Penn ESE 570 Spring 2017 - Khanna

57

Case 1: V_{in} Abruptly Rises - τ_{PHL}

IC: $V_{out} = V_{DD}, V_{in} = 0 \rightarrow V_{DD}$

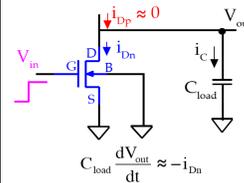nMOS - ON SAT $V_{out} \geq V_{DD} - V_{T0n}$
p-MOS OFF LIN $0 \leq V_{out} < V_{DD} - V_{T0n}$





Penn ESE 570 Spring 2017 - Khanna

58

Case 1: V_{in} Abruptly Rises - τ_{PHL}

IC: $V_{out} = V_{DD}, V_{in} = 0 \rightarrow V_{DD}$

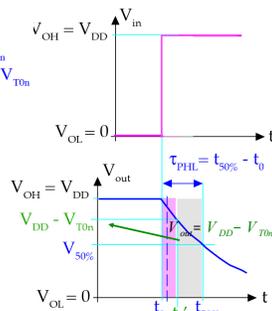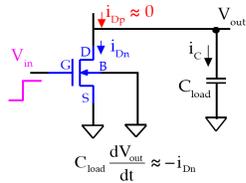
nMOS - ON SAT $V_{out} \geq V_{DD} - V_{T0n}$
p-MOS OFF LIN $0 \leq V_{out} < V_{DD} - V_{T0n}$



Penn ESE 570 Spring 2017 - Khanna

59

Recall: CMOS Inverter: Visual VTC

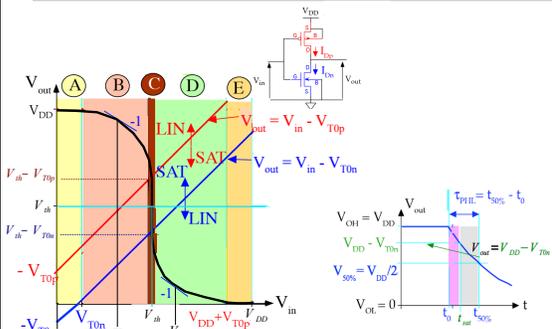

Penn ESE 570 Spring 2017 - Khanna

60

Case 1: V_{in} Abruptly Rises - τ_{PHL}

$C_{load} \frac{dV_{out}}{dt} = -i_{Dn}$
 $dt = C_{load} \frac{-dV_{out}}{i_{Dn}}$
 $\tau_{PHL} = \int_{t_0}^{t_1} dt = C_{load} \int_{V_{out}=0}^{V_{out}=V_{DD}/2} \left(\frac{-1}{i_{Dn}} \right) dV_{out}$
 $\tau_{PHL} = C_{load} \int_{V_{out}=0}^{V_{out}=V_{DD}/2} \left(\frac{-1}{i_{Dn}} \right) dV_{out} + C_{load} \int_{V_{out}=V_{DD}/2}^{V_{out}=V_{DD}} \left(\frac{-1}{i_{Dn}} \right) dV_{out}$

$t_0 \rightarrow t_1$
 $t_1 \rightarrow t_{50\%}$

Penn ESE 570 Spring 2017 – Khanna 61

Case 1: V_{in} Abruptly Rises - τ_{PHL}

saturation $t_0 \rightarrow t_1$
linear $t_1 \rightarrow t_{50\%}$

$\tau_{PHL} = C_{load} \int_{V_{out}=0}^{V_{out}=V_{DD}/2} \left(\frac{-1}{i_{Dn}} \right) dV_{out} + C_{load} \int_{V_{out}=V_{DD}/2}^{V_{out}=V_{DD}} \left(\frac{-1}{i_{Dn}} \right) dV_{out}$

saturation: $i_{Dn} = \frac{k_n}{2} (V_{in} - V_{T0n})^2$
 $\tau_{PHL, sat} = C_{load} \int_{V_{out}=0}^{V_{out}=V_{DD}/2} \left(\frac{-1}{\frac{k_n}{2} (V_{DD} - V_{T0n})^2} \right) dV_{out}$
 $\tau_{PHL, sat} = \frac{-C_{load}}{\frac{k_n}{2} (V_{DD} - V_{T0n})^2} \int_{V_{out}=0}^{V_{out}=V_{DD}/2} dV_{out}$
 $\tau_{PHL, sat} = \frac{2C_{load}V_{DD}}{k_n(V_{DD} - V_{T0n})^2}$

$V_{OH} = V_{DD}$
 $V_{OL} = 0$
 $V_{DD} - V_{T0n}$
 $V_{out} = V_{DD} - V_{T0n}$
 $V_{50\%}$
 $\tau_{PHL} = t_{50\%} - t_0$
 t_0 t_1 $t_{50\%}$

Penn ESE 570 Spring 2017 – Khanna 62

Case 1: V_{in} Abruptly Rises - τ_{PHL}

saturation $t_0 \rightarrow t_1$
linear $t_1 \rightarrow t_{50\%}$

$\tau_{PHL} = C_{load} \int_{V_{out}=0}^{V_{out}=V_{DD}/2} \left(\frac{-1}{i_{Dn}} \right) dV_{out} + C_{load} \int_{V_{out}=V_{DD}/2}^{V_{out}=V_{DD}} \left(\frac{-1}{i_{Dn}} \right) dV_{out}$

linear: $i_{Dn} = \frac{k_n}{2} (V_{in} - V_{T0n})(V_{out} - V_{out}^2)$
 $\tau_{PHL, lin} = C_{load} \int_{V_{out}=V_{DD}/2}^{V_{out}=V_{DD}} \left(\frac{-1}{\frac{k_n}{2} (2(V_{DD} - V_{T0n})V_{out} - V_{out}^2)} \right) dV_{out}$
 $\tau_{PHL, lin} = \frac{2C_{load}}{k_n} \int_{V_{out}=V_{DD}/2}^{V_{out}=V_{DD}} \left(\frac{-1}{(2(V_{DD} - V_{T0n})V_{out} - V_{out}^2)} \right) dV_{out}$
 $\tau_{PHL, lin} = \frac{2C_{load}}{k_n} \cdot \frac{-1}{2(V_{DD} - V_{T0n})} \ln \left(\frac{V_{out}}{2(V_{DD} - V_{T0n}) - V_{out}} \right) \Bigg|_{V_{out}=V_{DD}/2}^{V_{out}=V_{DD}}$

$V_{OH} = V_{DD}$
 $V_{OL} = 0$
 $V_{DD} - V_{T0n}$
 $V_{out} = V_{DD} - V_{T0n}$
 $V_{50\%}$
 $\tau_{PHL} = t_{50\%} - t_0$
 t_0 t_1 $t_{50\%}$

Penn ESE 570 Spring 2017 – Khanna 63

Case 1: V_{in} Abruptly Rises - τ_{PHL}

$\tau_{PHL, lin} = \frac{2C_{load}}{k_n} \cdot \frac{-1}{2(V_{DD} - V_{T0n})} \ln \left(\frac{V_{out}}{2(V_{DD} - V_{T0n}) - V_{out}} \right) \Bigg|_{V_{out}=V_{DD}/2}^{V_{out}=V_{DD}}$
 $\tau_{PHL, lin} = \frac{C_{load}}{k_n(V_{DD} - V_{T0n})} \ln \left(\frac{2(V_{DD} - V_{T0n}) - V_{DD}/2}{V_{DD}/2} \right)$

Penn ESE 570 Spring 2017 – Khanna 64

Case 1: V_{in} Abruptly Rises - τ_{PHL}

saturation $t_0 \rightarrow t_1$
linear $t_1 \rightarrow t_{50\%}$

$\tau_{PHL} = C_{load} \int_{V_{out}=0}^{V_{out}=V_{DD}/2} \left(\frac{-1}{i_{Dn}} \right) dV_{out} + C_{load} \int_{V_{out}=V_{DD}/2}^{V_{out}=V_{DD}} \left(\frac{-1}{i_{Dn}} \right) dV_{out}$

$\tau_{PHL, sat} = \frac{2C_{load}V_{DD}}{k_n(V_{DD} - V_{T0n})^2}$ $\tau_{PHL, lin} = \frac{C_{load}}{k_n(V_{DD} - V_{T0n})} \ln \left(\frac{2(V_{DD} - V_{T0n}) - V_{DD}/2}{V_{DD}/2} \right)$
 $\tau_{PHL} = \frac{2C_{load}V_{DD}}{k_n(V_{DD} - V_{T0n})^2} + \frac{C_{load}}{k_n(V_{DD} - V_{T0n})} \ln \left(\frac{2(V_{DD} - V_{T0n}) - V_{DD}/2}{V_{DD}/2} \right)$

$V_{OH} = V_{DD}$
 $V_{OL} = 0$
 $V_{DD} - V_{T0n}$
 $V_{out} = V_{DD} - V_{T0n}$
 $V_{50\%}$
 $\tau_{PHL} = t_{50\%} - t_0$
 t_0 t_1 $t_{50\%}$

Penn ESE 570 Spring 2017 – Khanna 65

Case 1: V_{in} Abruptly Rises - τ_{PHL}

saturation $t_0 \rightarrow t_1$
linear $t_1 \rightarrow t_{50\%}$

$\tau_{PHL} = C_{load} \int_{V_{out}=0}^{V_{out}=V_{DD}/2} \left(\frac{-1}{i_{Dn}} \right) dV_{out} + C_{load} \int_{V_{out}=V_{DD}/2}^{V_{out}=V_{DD}} \left(\frac{-1}{i_{Dn}} \right) dV_{out}$

$\tau_{PHL, sat} = \frac{2C_{load}V_{DD}}{k_n(V_{DD} - V_{T0n})^2}$ $\tau_{PHL, lin} = \frac{C_{load}}{k_n(V_{DD} - V_{T0n})} \ln \left(\frac{2(V_{DD} - V_{T0n}) - V_{DD}/2}{V_{DD}/2} \right)$
 $\tau_{PHL} = \frac{2C_{load}V_{DD}}{k_n(V_{DD} - V_{T0n})^2} + \frac{C_{load}}{k_n(V_{DD} - V_{T0n})} \ln \left(\frac{2(V_{DD} - V_{T0n}) - V_{DD}/2}{V_{DD}/2} \right) \propto R_n$
 $\tau_{PHL} = C_{load} \left(\frac{1}{k_n(V_{DD} - V_{T0n})^2} \left[\frac{2V_{DD}}{V_{DD} - V_{T0n}} + \ln \left(\frac{2(V_{DD} - V_{T0n}) - V_{DD}/2}{V_{DD}/2} \right) \right] \right)$

$V_{OH} = V_{DD}$
 $V_{OL} = 0$
 $V_{DD} - V_{T0n}$
 $V_{out} = V_{DD} - V_{T0n}$
 $V_{50\%}$
 $\tau_{PHL} = t_{50\%} - t_0$
 t_0 t_1 $t_{50\%}$

Penn ESE 570 Spring 2017 – Khanna 66

Case 1: V_{in} Abruptly Rises - τ_{PHL}

$$\tau_{PHL} = C_{load} \left[\frac{1}{k_n(V_{DD} - V_{T0n})} \left[\frac{2V_{T0n}}{(V_{DD} - V_{T0n})} + \ln \left(\frac{2(V_{DD} - V_{T0n})}{V_{DD}/2} - 1 \right) \right] \right]$$

Recall from static CMOS Inverter:

$$V_{th} = \frac{V_{T0n} + \sqrt{\frac{1}{k_R} (V_{DD} + V_{T0p})}}{1 + \sqrt{\frac{1}{k_R}}} \rightarrow k_R = \left(\frac{V_{DD} + V_{T0p} - V_{th}}{V_{th} - V_{T0n}} \right)^2$$

DESIGN: (1) $V_{th} \rightarrow k_R$; (2) $\tau_{PHL} \rightarrow k_n$; (3) k_R & $k_n \rightarrow k_p$

Case 1: V_{in} Abruptly Rises - τ_{PHL}

$$\tau_{PHL} = C_{load} \left[\frac{1}{k_n(V_{DD} - V_{T0n})} \left[\frac{2V_{T0n}}{(V_{DD} - V_{T0n})} + \ln \left(\frac{2(V_{DD} - V_{T0n})}{V_{DD}/2} - 1 \right) \right] \right]$$

Recall from static CMOS Inverter:

$$V_{th} = \frac{V_{T0n} + \sqrt{\frac{1}{k_R} (V_{DD} + V_{T0p})}}{1 + \sqrt{\frac{1}{k_R}}} \rightarrow k_R = \left(\frac{V_{DD} + V_{T0p} - V_{th}}{V_{th} - V_{T0n}} \right)^2$$

DESIGN: (1) $V_{th} \rightarrow k_R$; (2) $\tau_{PHL} \rightarrow k_n$; (3) k_R & $k_n \rightarrow k_p$

(1) $V_{th} \rightarrow k_R$; (2) $\tau_{PLH} \rightarrow k_p$; (3) k_R & $k_p \rightarrow k_n$

Idea

- $P_{tot} = P_{static} + P_{dyn} + P_{sc}$
 - Can't ignore Static Power (aka. Leakage power)
- Propagation Delay
 - Average Current Model
 - Differential Equation Model
 - 1st Order Model

Admin

- HW 4 due Thursday, 2/16